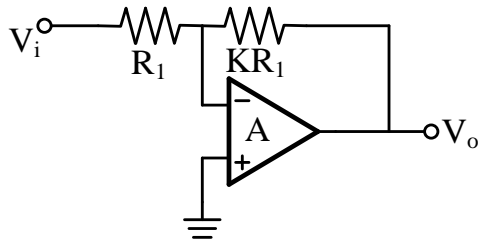



### BONUS EXAM 457 (5 POINTS)

Problem. 1. i) Determine the value of  $A_o$  to yield a maximum gain error of  $\pm 5\%$  when  $K=3$ .




ii) For  $GB/s=A(s)$  and  $GB=10^6$  Hz determine the error gain at  $\omega = 2\pi \times 250$  Kr/s.

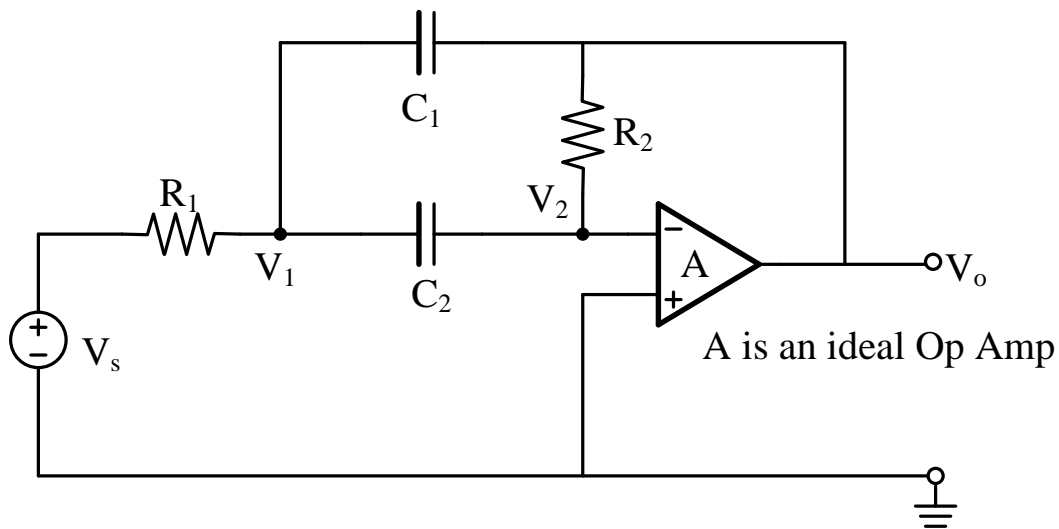Problem 2. i) Write the nodal analysis for the circuit shown below:



ii) Determine the transfer function  $H(s) = \frac{V_o(s)}{V_s(s)}$

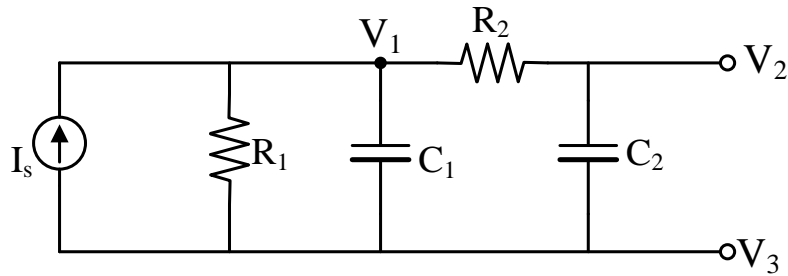Problem 3. i) Write the admittance matrix nodal equations  $YV=I$ .



ii) Obtain the impedance transfer function  $Z_{in} = \frac{V_1(s)}{I(s)}$  for  $V_3 = 0$ . Write a simplified expression of  $Z_{in}$ .

iii) Plot  $Z_{in}$  for  $R_1 = R_2 = 1K\Omega$   $C_1 = C_2 = (10^{-6}/2\pi)F$  and  $\omega = 0.1$  to  $10$  Kr/s .


Problem 4. Determine if the following expressions are correct or not and why.

$$CV + RCI + I/\omega \quad (1)$$

$$\frac{1}{sC_2 + sC_1} + \frac{1}{R_1} + \frac{1}{sL} \quad (2)$$

$$sC_1 + \frac{1}{R_2} + \frac{R_2}{R_1} \frac{1}{sL} \quad (3)$$

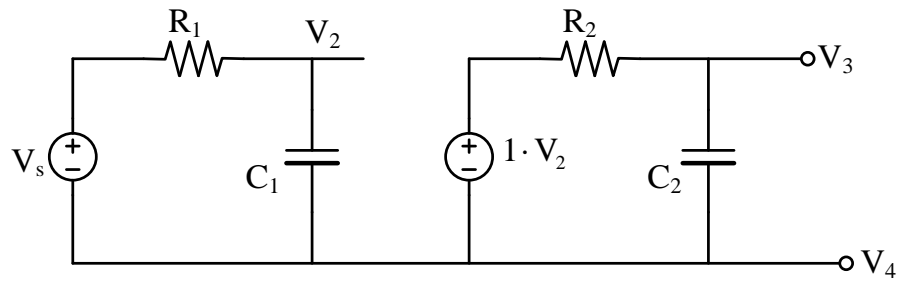Problem 5. i) Write the admittance nodal analysis  $YV=I$



ii) Obtain  $V_3(s)/V_s$  for  $V_4 = 0$

iii) Compare results from Prob. 3 ii) and the result in 5ii). Make comments.