

FALL 2013
ECEN 457 (ESS)

Name _____

EXAM #1


This is a closed book and notes exam. This exam is worth 15% of your total grade.

| Prob. | Maximum | Yours |
|--------------|----------------|--------------|
| 1 | 3 | |
| 2 | 4 | |
| 3 | 4 | |
| 4 | 4 | |
| Extra Credit | 1 | |
| Total | 16 | |

Prob. 1. (Macromodeling). Propose a macromodel of the transfer function $H(s)$ using only SPICE primitives (i.e, passive components and dependent and independent sources)


$$H(s) = K \frac{(1 + s/\omega_z)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})(1 + s/\omega_{p3})}$$

Prob. 2. (Instrumentation). Obtain the closed form of the transfer function $H(s) = \frac{V_o(s)}{V_{in}(s)}$ of the following circuit. Where $V_{in}(s) = V_1 - V_2$.

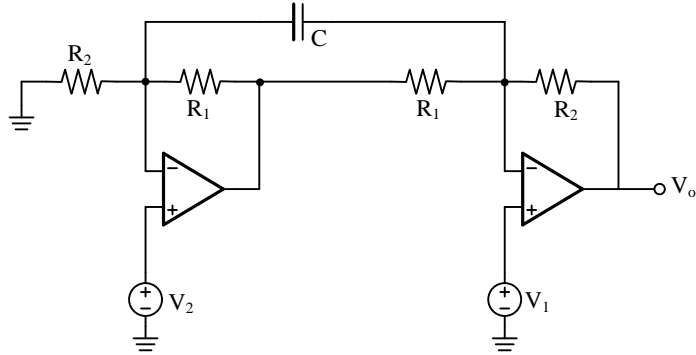

Prob. 3. (Feedback AMP)

- a) Obtain the transfer function $H = V_o/V_{in}$ assuming a finite open loop op amp gain A_o .
- b) The ideal voltage $-R_F/R_1$ is not obtained due to the finite A_o . For $R_F/R_1=9$, determine the value of A_o for a $\pm 1\%$ voltage gain deviation (ϵ).
- c) Determine the normalized sensitivity expression for $S_{A_o}^H$

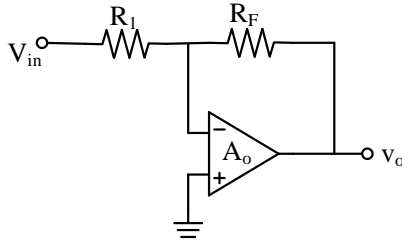


Prob. 4. (Input Offset Voltage)

Assume an op amp with an open loop gain $A_{\min} = 10^4 \text{ V/V}$,

$V_{\text{oso(max)}} = 2\text{mV}$, and a $\text{CMRR}_{\text{db(min)}} = \text{PSRR}_{\text{db(min)}} = 74\text{dB}$ is connected as a voltage follower configuration. $(\text{TC}(V_{\text{os}})_{\text{ovg}} = 3\mu\text{V}/^\circ\text{C})$, Supply = $\pm 15\text{V}$, $T = 35^\circ\text{C}$

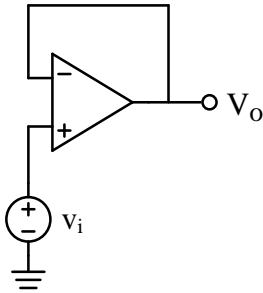- i) Estimate the worst case departure of v_o from the ideal when $v_i = 0\text{V}$
- ii) Repeat with $v_i = 10\text{V}$
- iii) Repeat the problem if the supply voltages are decreased from $\pm 15\text{V}$ to $\pm 12\text{V}$



EXTRA CREDIT (No partial credit)

Describe the conditions of resistors (conductances) that allow the output V_o to be written as

