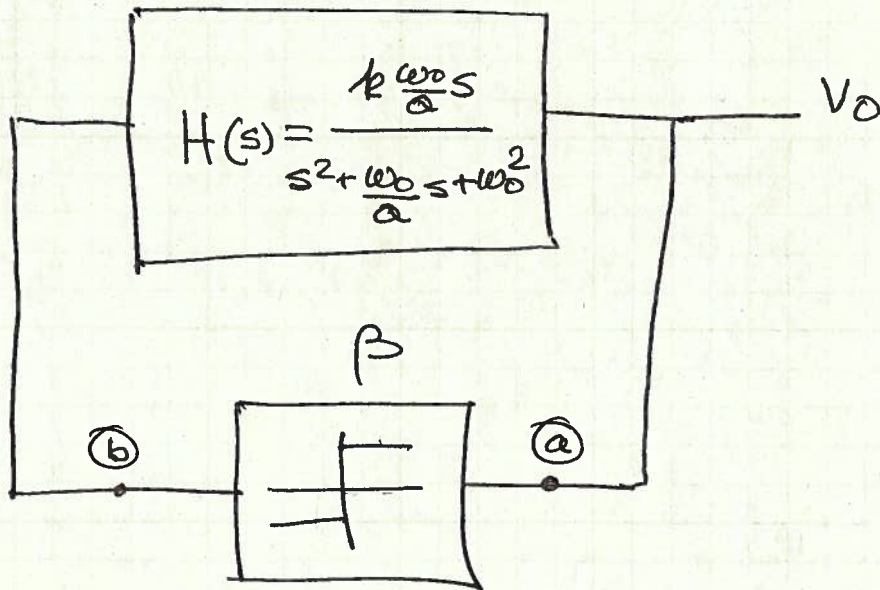


SIGNAL GENERATORS

- SINUSOIDAL
 - BP (TWO INTEGRATOR) BASED
 - ONE OP AMP (WIEN-BRIDGE)
- TRIANGULAR AND SQUARE WAVE
- SAWTOOTH
- V-F AND F-V CONVERTERS

HOW TO MAKE A SINUSOIDAL
OSCILLATOR BASED ON FILTERS?

BAND PASS BASED OSCILLATOR



ASSUMING SMALL SIGNAL CONDITIONS, WE
CAN WRITE THE LOOP FILTER

$$1 - \beta H(s) = 0 \quad ; \quad K = k \frac{\omega_0}{Q}$$

$$1 - \frac{Ks}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} = 0 \quad \text{or} \quad \beta H(s) = 1$$

THUS THE CHARACTERISTIC EQUATION YIELDS:

$$s^2 - \left(k - \frac{\omega_0}{Q}\right)s + \omega_0^2 = 0$$

IN ORDER TO HAVE THE POLES IN THE RHP, IT IS IMPOSED THAT


$$K - \frac{\omega_0}{Q} > 0$$

OR


$$K \geq \frac{\omega_0}{Q}$$

HOWEVER TO MOVE THE POLES ON THE $j\omega$ AXIS WE REQUIRE A NON-LINEAR BLOCK IMPLEMENTATION OF β . THERE A NUMBER OF BLOCKS TO ACCOMPLISH THIS.

IMPLEMENTATION 1

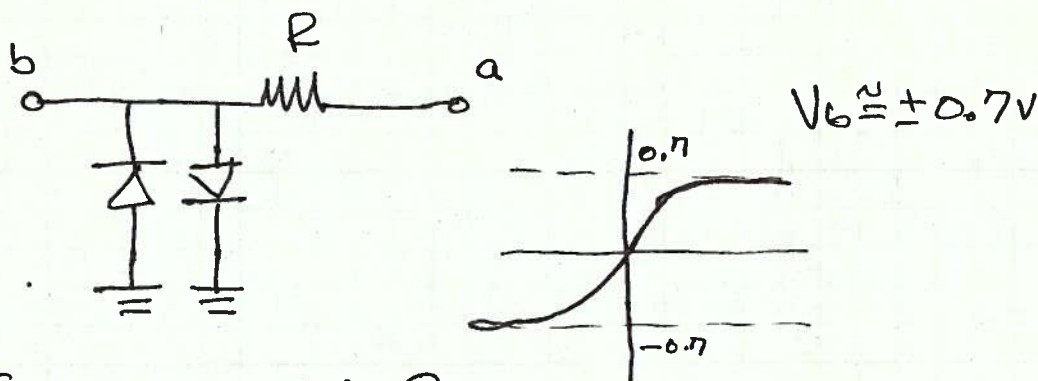


IMPLEMENTATION 2

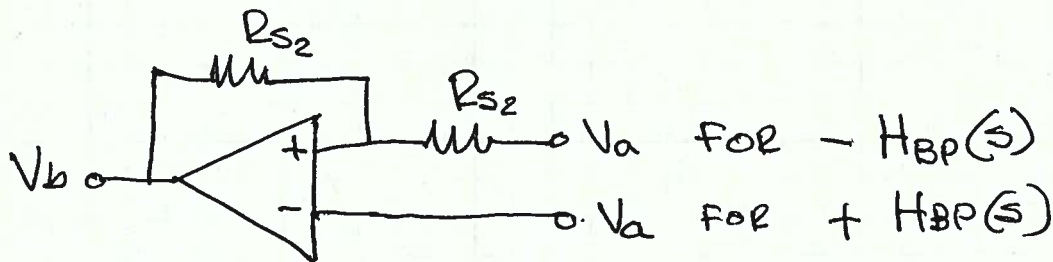


INVERTING SCHMITT TRIGGER
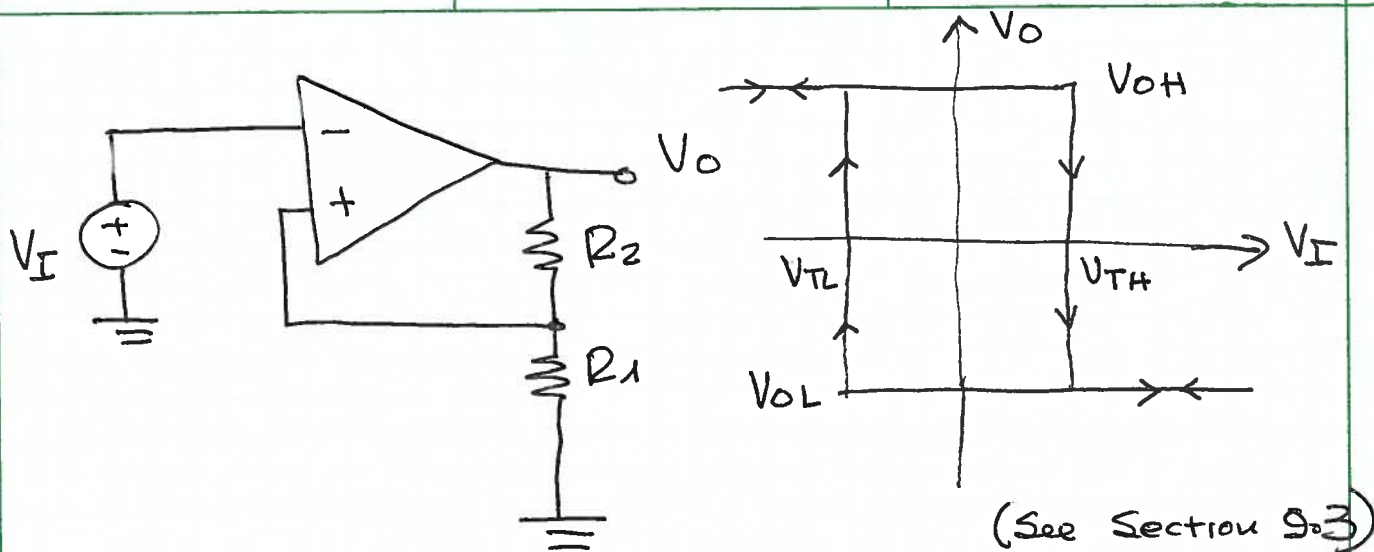
$$V_{TH} = \frac{R_{S1}}{R_{S1} + R_{S2}} V_{CC}$$



INVERTING SCHMITT TRIGGER

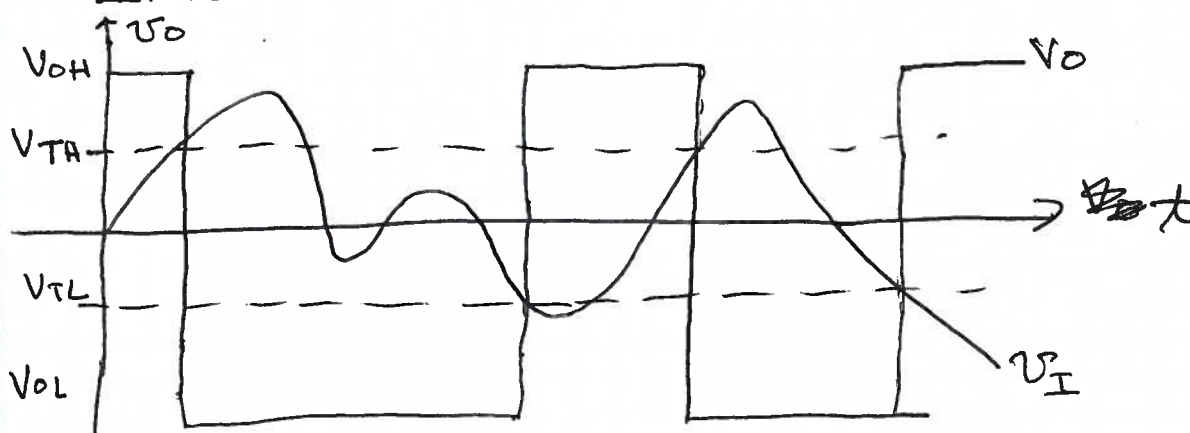

$$V_{TH} = \frac{R_1}{R_1 + R_2} V_{OH} \quad \text{OR} \quad V_{OH} = \left(1 + \frac{R_2}{R_1}\right) V_{TH}$$

$$V_{TL} = \frac{R_1}{R_1 + R_2} V_{OL} \quad \text{OR} \quad V_{OL} = \left(1 + \frac{R_2}{R_1}\right) V_{TL}$$

HYSTERISIS WIDTH:

$$\Delta V_T = V_{TH} - V_{TL} = \frac{R_1}{R_1 + R_2} (V_{OH} - V_{OL})$$

OR

$$V_{OH} - V_{OL} = \left(1 + \frac{R_2}{R_1}\right) \Delta V_T$$

NUMERICAL EXAMPLE


$$V_{OH} = 13V \quad ; \quad V_{OL} = -13V$$

FOR $R_2 = 16K\Omega$ AND $R_1 = 10K\Omega$

$$V_{TH} = \frac{13}{26} \times 10 = 5V$$

$$V_{TL} = \frac{-13}{26} \times 10 = -5V$$

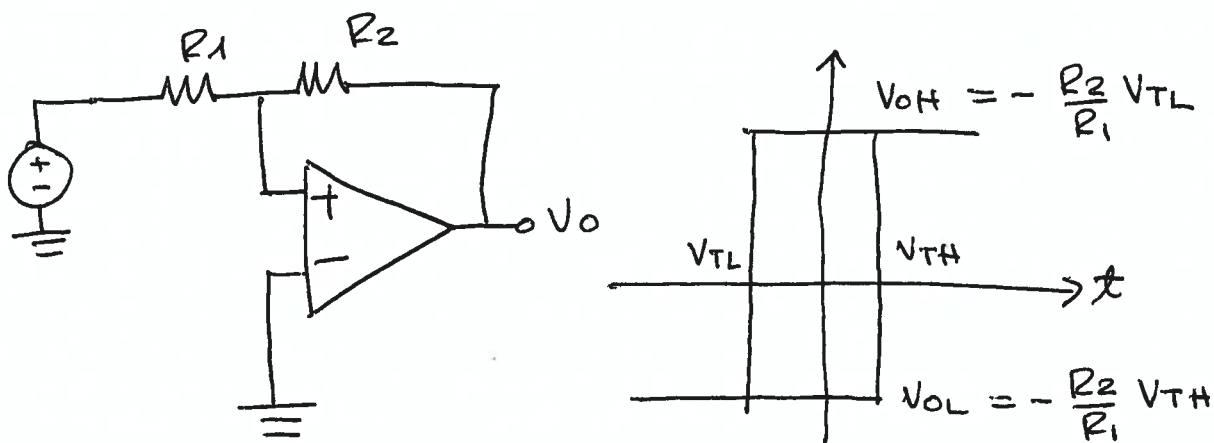LET US CONSIDER THE NON-INVERTING SCHMITT TRIGGER




$$V_{TH} = -\frac{R_1}{R_2} V_{OL} \quad \Leftarrow \quad \frac{V_{TH} - 0}{R_1} = \frac{0 - V_{OL}}{R_2}$$

$$V_{TL} = -\frac{R_1}{R_2} V_{OH}$$

$$\Delta V_T = \frac{R_1}{R_2} (V_{OH} - V_{OL}) \quad \text{HYSTERISIS WINDOW}$$

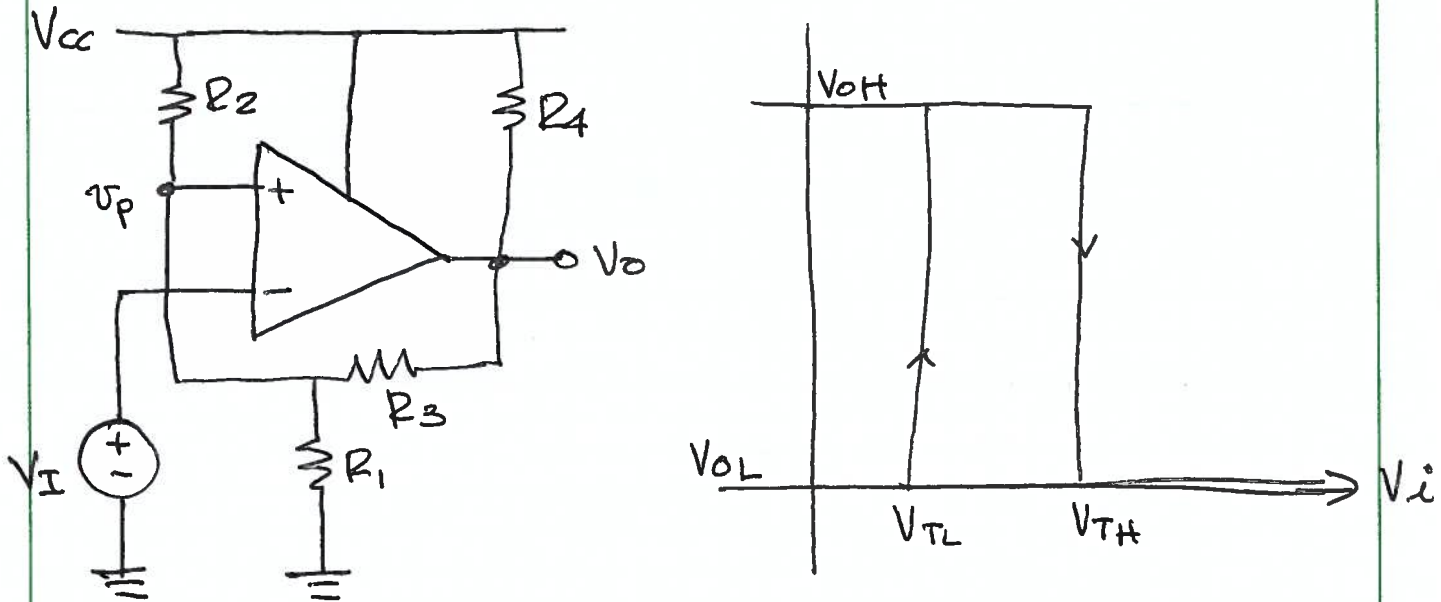SCHMITT TRIGGER IN I/O IN FIRST QUADRANT AND HAVING A SINGLE SUPPLY



USING SUPERPOSITION

$$V_p = \frac{R_{1,3}}{R_{1,3} + R_2} V_{CC} + \frac{R_{1,2}}{R_{1,2} + R_3} V_o$$

WHERE $R_{1,3} = R_1 // R_3$ & $R_{1,2} = R_1 // R_2$

IF $V_{OH} \approx V_{CC}$ AND $V_{OL} = 0$

THEN $R_4 \ll R_3 + R_{1,2}$

THUS, IMPOSING $V_p = V_{TL}$ FOR $V_o = V_{OL} = 0$
AND $V_p = V_{TH}$ FOR $V_o = V_{OH} = V_{CC}$, WE GET

$$V_{TL} = \frac{R_{1,3}}{R_{1,3} + R_2} V_{CC}; \quad V_{TH} = \frac{R_1}{R_1 + R_{2,3}} V_{CC}$$


REARRANGING TERMS AND FIX R_4 AND $R_3 \gg R_4$

$$\frac{1}{R_2} = \frac{V_{TL}}{V_{CC} - V_{TL}} \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$



$$\frac{1}{R_1} = \frac{V_{CC} - U_{TH}}{V_{TH}} \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

THUS THE TWO ABOVE EQUATIONS CAN BE SOLVED.

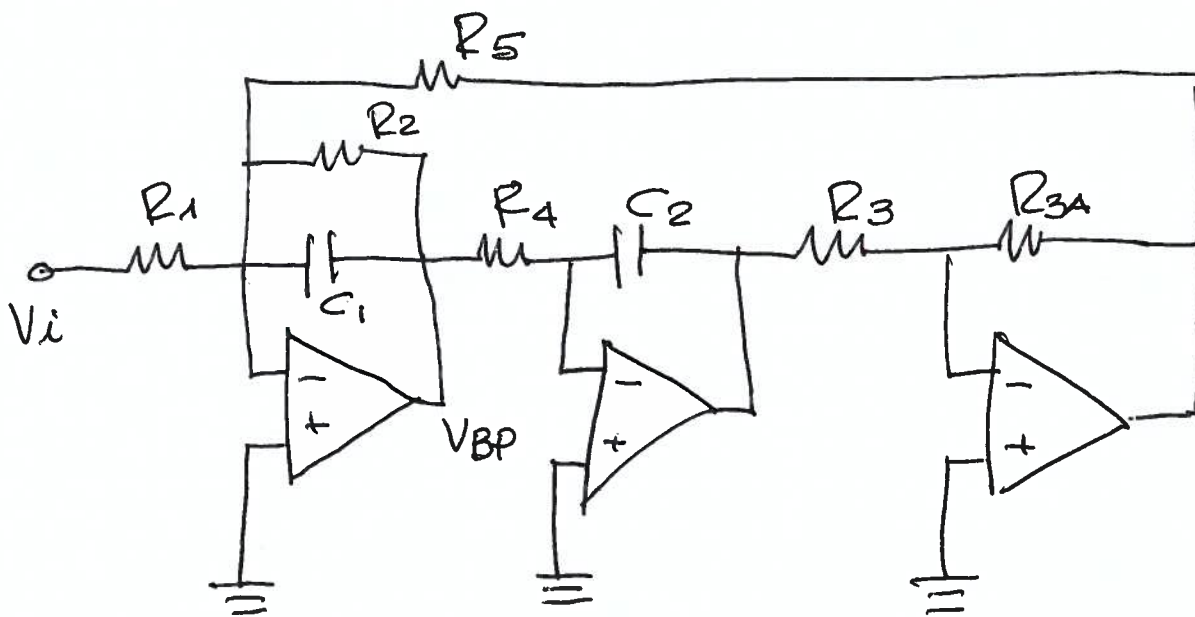THE BP CAN BE IMPLEMENTED USING THE TOW-THOMAS



WIEN - BRIDGE

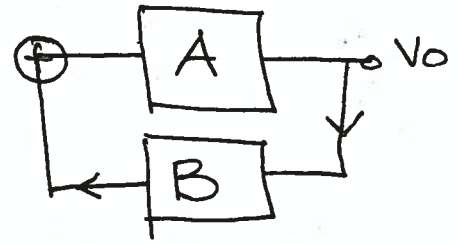
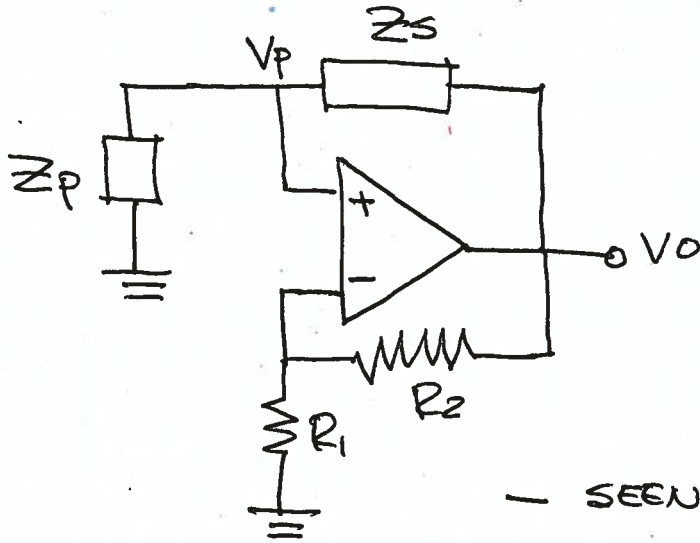


— SEEN AS NON-INVERTER


$$A = \frac{V_o}{V_p} = 1 + \frac{R_2}{R_1}$$

FURTHERMORE WE CAN SEE AS A VOLTAGE DIVIDER

$$\frac{Z_p}{Z_p + Z_s} V_o = V_p$$

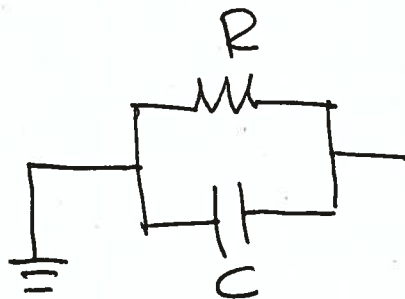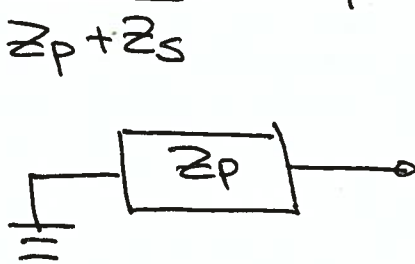

$$Z_p = \frac{R}{1 + sRC}$$

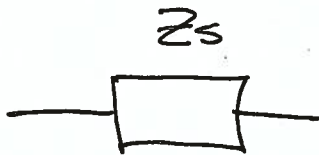

$$Z_s = \frac{1 + sRC}{sC}$$

THUS

$$\frac{V_o}{V_p} = \frac{Z_p + Z_s}{Z_p}$$

$$B = \frac{V_p}{V_o} = \frac{Z_p}{Z_p + Z_s} = \frac{1}{1 + \frac{Z_s}{Z_p}} = \frac{1}{1 + \frac{R \cdot sC}{1 + sRC}} = \frac{1 + sRC}{1 + sRC + sRC}$$

$$B = \frac{1}{1 + \frac{Z_s}{Z_p}} = \frac{1}{1 + \frac{(1+sRC)^2}{sRC}}$$

$$B = \frac{sRC}{(sRC)^2 + 3sRC + 1} \Rightarrow \text{BAND PASS FILTER}$$

CHARACTERISTIC EQUATION

$$1 - AB = 1 - T$$

$$T = AB = \frac{(1 + \frac{R_2}{R_1})sRC}{(sRC)^2 + 3sRC + 1}$$

$$T = \frac{1 + \frac{R_2}{R_1}}{sRC + 3 + \frac{1}{sRC}}$$

$$\text{IF } RC = \frac{1}{\omega_0}$$

$$T(j\omega) = \frac{1 + \frac{R_2}{R_1}}{j\omega/\omega_0 - \frac{j}{\omega/\omega_0} + 3} = \frac{1 + \frac{R_2}{R_1}}{3 + j\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$


$$T(j\omega_0) = \frac{1 + R_2/R_1}{3}$$

TO ~~AV~~ FORCE OSCILLATION



$$T(j\omega_0) > 3 \quad \text{i.e.} \quad \frac{R_2}{R_1} > 2$$

$$\frac{R_2}{R_1} = 2 + \epsilon$$

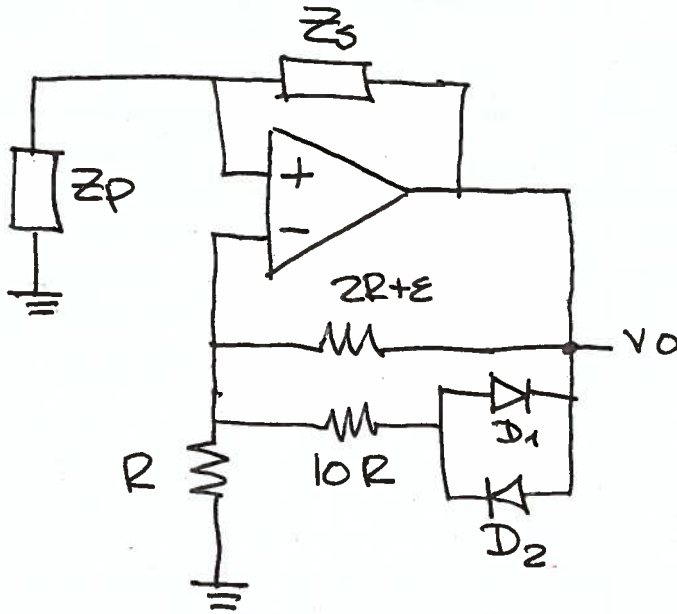THE NON-LINEAR PART OF THE OSCILLATOR
MUST BE ADDED





SQUARE WAVE OSCILLATOR

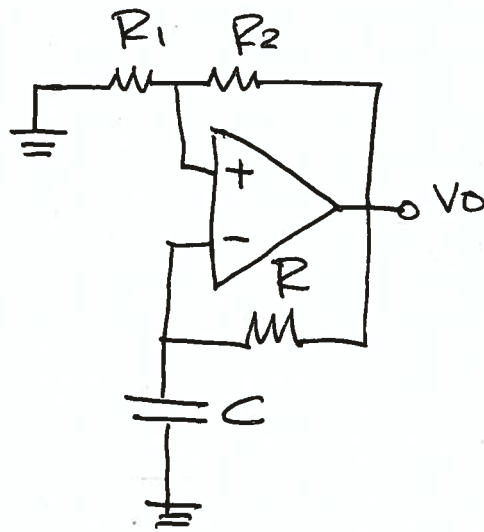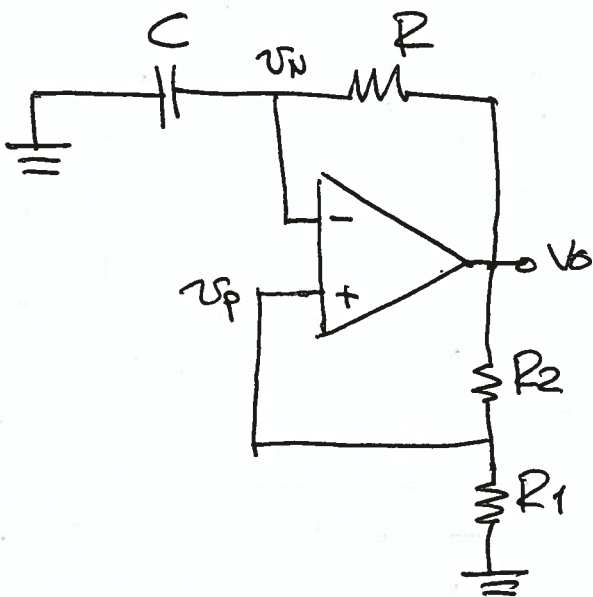

LET US LOOK CLOSER TO THE

SCHMITT TRIGGER

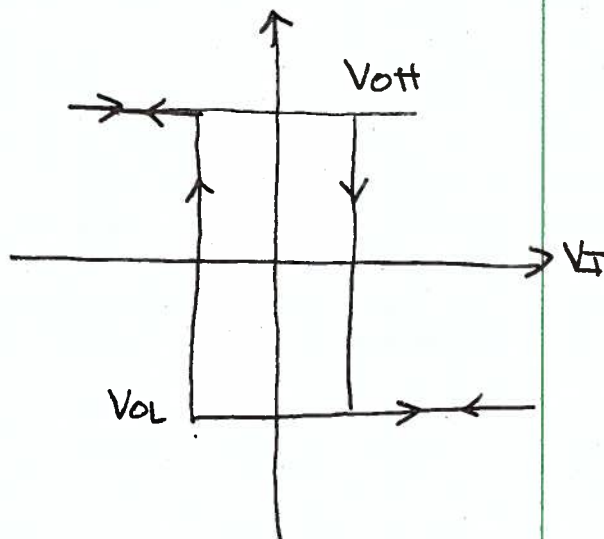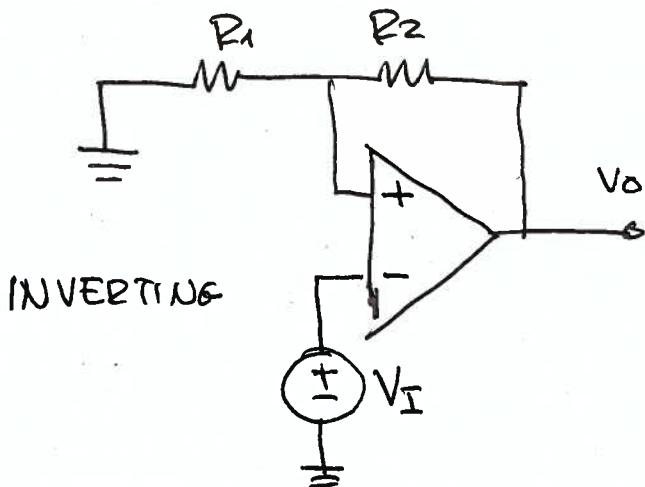


$$V_{TH} = \frac{R_1}{R_1 + R_2} V_{OH}$$


$$V_{TL} = \frac{R_1}{R_1 + R_2} V_{OL}$$

$$\Delta V_T = V_{TH} - V_{TL} = \frac{R_1}{R_1 + R_2} (V_{OH} - V_{OL})$$
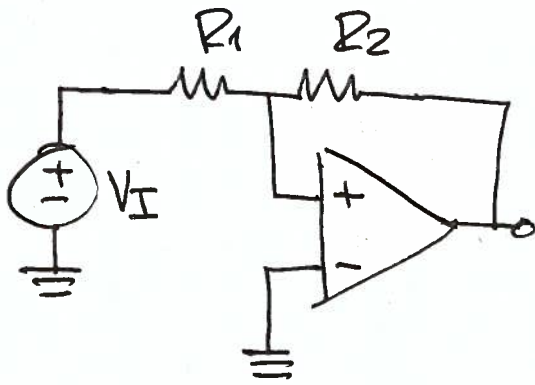
$$\Delta V_T = \frac{1}{1 + \frac{R_2}{R_1}} (V_{OH} - V_{OL})$$



NON-INVERTING
SCHMITT TRIGGER

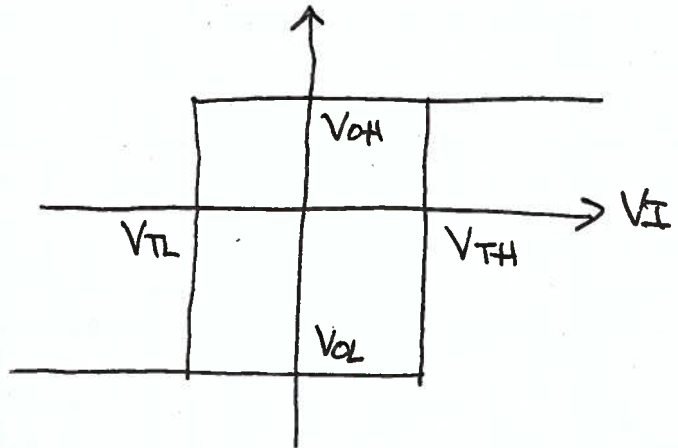

$$\frac{V_{TH} - 0}{R_1} = \frac{0 - V_{OL}}{R_2}$$

$$V_{TH} = -\frac{R_1}{R_2} V_{OL}$$

TRIPPING VOLTAGE V_{TL} BECOMES


$$\frac{V_{OH} - 0}{R_2} = \frac{0 - V_{TL}}{R_1}$$

OR


$$V_{TL} = -\frac{R_1}{R_2} V_{OH}$$

$$\Delta V_T = \frac{R_1}{R_2} (V_{OH} - V_{OL})$$
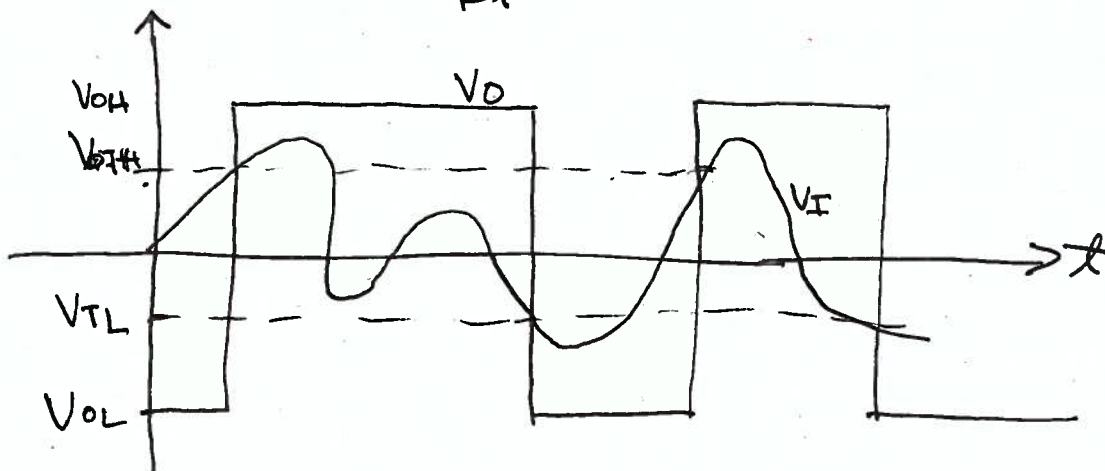
$$\Delta V_T = \frac{1}{\frac{R_2}{R_1}} (V_{OH} - V_{OL})$$




NOTES ON RELAXATION OSCILLATORS

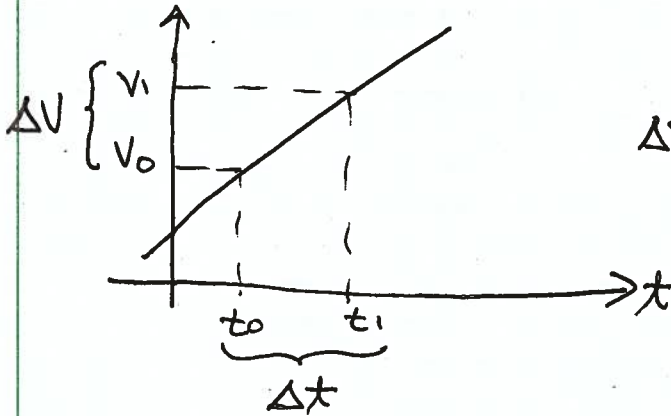

LINEAR

$$C \Delta V = I \Delta t$$

$$\Delta t = \frac{C}{I} \Delta V$$

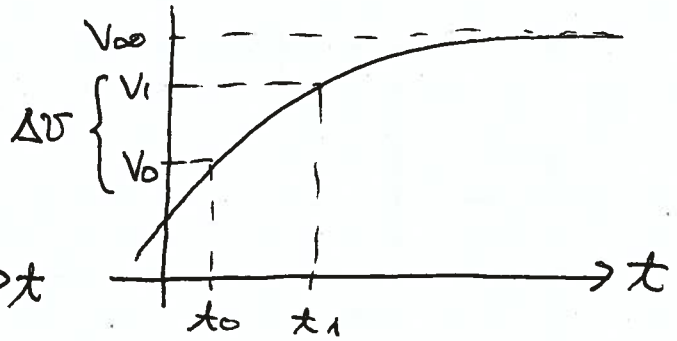

EXPONENTIAL

$$v(t) = V_{\infty} + (V_0 - V_{\infty}) e^{-\frac{t-t_0}{\tau}}$$

$$\tau = RC$$

$$V_1 = V_{\infty} + (V_0 - V_{\infty}) e^{-\frac{t_1-t_0}{\tau}}$$

$$\Delta t = t_1 - t_0 = \tau \ln \frac{V_{\infty} - V_0}{V_{\infty} - V_1}$$


THUS FOR THE BASIC-FREE-RUNNING OSCILLATOR

$$\frac{T}{2} = RC \ln \frac{V_{sat} + V_T}{V_{sat} - V_T}$$

$$V_T = \frac{V_{sat}}{1 + \frac{R_2}{R_1}}$$


THEN
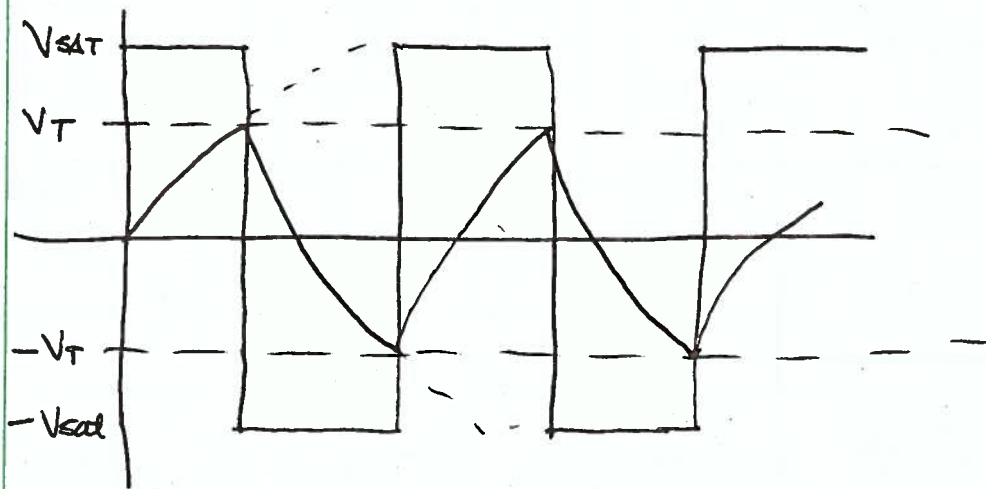
$$f_0 = \frac{1}{T} = \frac{1}{2RC \ln \left(1 + \frac{R_2}{R_1}\right)}$$



$$f_0 \neq f(V_T, V_{SAT})$$

SQUARE WAVE GENERATOR

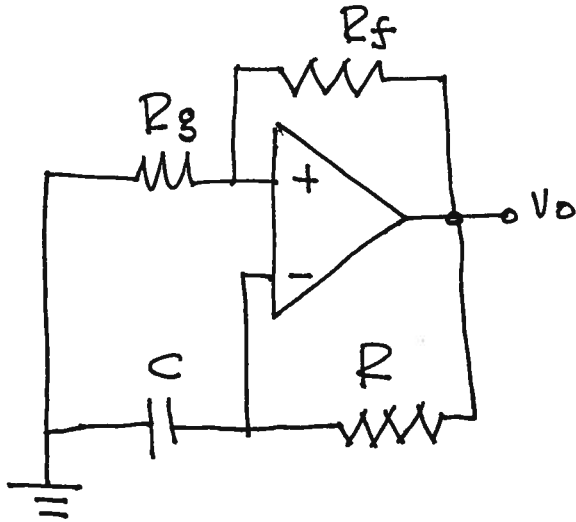

$$V_{TH} = \frac{R_f}{R_g + R_f} V_{OH}$$

OR

$$V_{TL} = \frac{R_g}{R_g + R_f} V_{OL}$$

HIGH TO LOW. —

ASSUME THE OUTPUT VOLTAGE IS AT V_{OH} , THEN THE NON-INVERTING INPUT IS AT V_{TH} , AND THE INVERTING IS IN EXPONENTIAL TRANSITION FROM ITS INITIAL VALUE V_{TL} TOWARD V_{OH} . THUS

$$V^-(t) = V_{OH} - (V_{OH} - V_{TL}^-) e^{-t/RC}$$

OR EQUIVALENT

$$V^-(s) = \frac{V_{OH}}{s} - \frac{(V_{OH} - V_{TL}^-)}{1 + s/RC}$$


THE TOTAL EXPONENTIAL TRANSITION TIME IS THE SOLUTION TO THE EQUALITY

$$V^-(t) = \cancel{V_{OH}} V_{TH}^+$$

OR

$$V_{OH} - \left(V_{OH} - \frac{R_g}{R_g + R_f} V_{OL} \right) e^{-t/RC} = \frac{R_f}{R_g + R_f} V_{OH}$$

NOTE. — SEE SECTION 10.2 TEXT

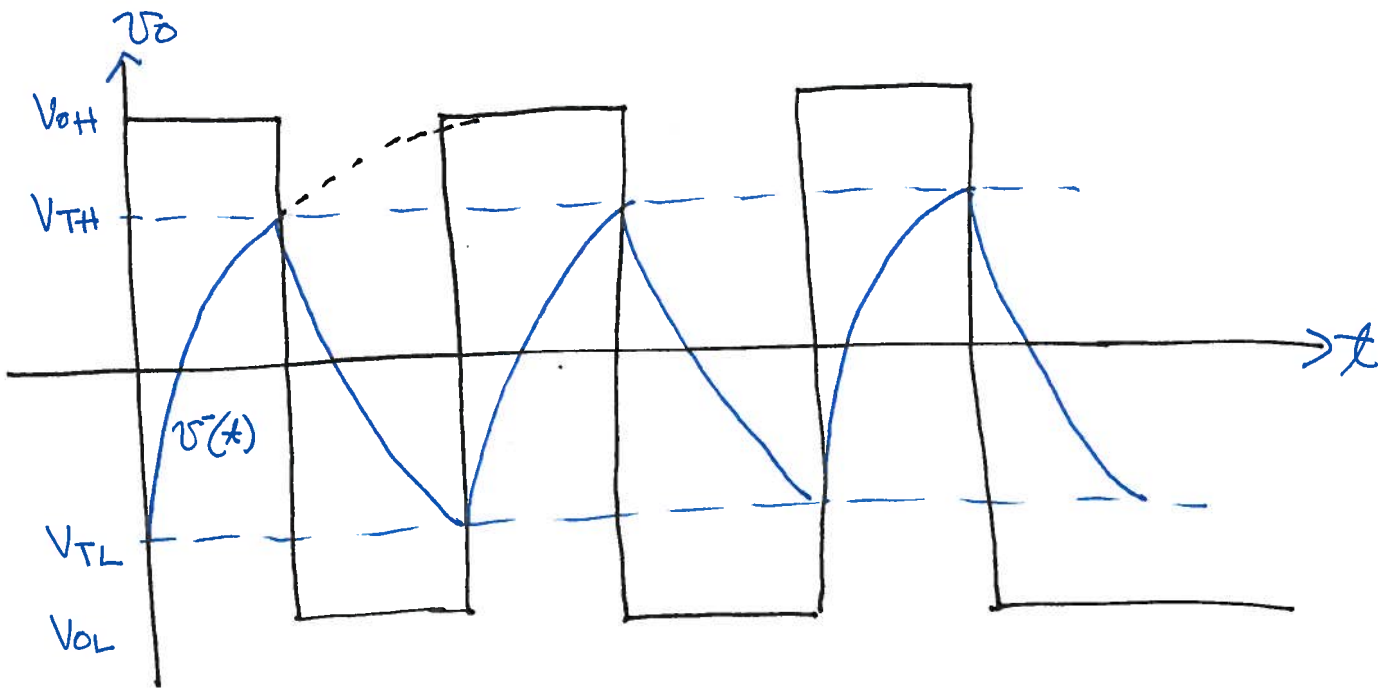

THEN

$$V_{OH} \left(1 - \frac{R_B}{R_B + R_F} \right) = \left(V_{OH} - \frac{R_B}{R_B + R_F} V_{OL} \right) e^{-t/RC}$$

THE TRANSITION TIME IS GIVEN BY

$$t_{HL} = RC \ln \left[\frac{(R_B + R_F) V_{OH} - R_B V_{OL}}{R_F V_{OH}} \right]$$

$$t_{HL} = RC \ln \left(1 + \frac{R_B (V_{TH} - V_{OL})}{R_F V_{OH}} \right)$$

$$t_{HL} = RC \ln \left(1 + \frac{\Delta V_T}{V_{OH}} \right)$$

LOW TO HIGH

SAME AS BEFORE BY INTERCHANGING V_{OH} AND V_{OL} .
THEN THE DUTY CYCLE IS DETERMINED BY
THE SUM OF THE TRANSITION TIMES:

$$\tau = RC \left[\ln \left(1 + \frac{R_g (V_{OH} - V_{OL})}{R_f V_{OH}} \right) + \ln \left(1 + \frac{R_g (V_{OL} - V_{OH})}{R_f V_{OL}} \right) \right]$$

$$\tau = RC \left[\ln \left(1 + \frac{\Delta V_T}{V_{OH}} \right) + \ln \left(1 - \frac{\Delta V_T}{V_{OL}} \right) \right]$$

FOR 50% DUTY CYCLE $V_{OL} = -V_{OH}$ YIELDS

$$t_{HL} = t_{LH} = RC \ln \left(1 + \frac{2R_g}{R_f} \right)$$

THEN THE PERIOD IS GIVEN BY


$$T = 2t_{HL} = 2RC \ln \left(1 + 2 \frac{R_g}{R_f} \right)$$

T WILL BE AFFECTED BY THE SR OF THE
COMPARATOR. ALSO THE PARASITIC CAPACITANCE
ASSOCIATED TO THE "+" TERMINAL OF THE
COMPARATOR.

NOTE THAT V_{OL} AND V_{OH} CAN ^{NOT} BE EXACTLY
PREDICTED THUS A CLAMPING CIRCUIT
IS PLACED USUALLY AT THE OUTPUT.

ASTABLE, NONSYMMETRIC SQUARE-WAVE GENERATOR

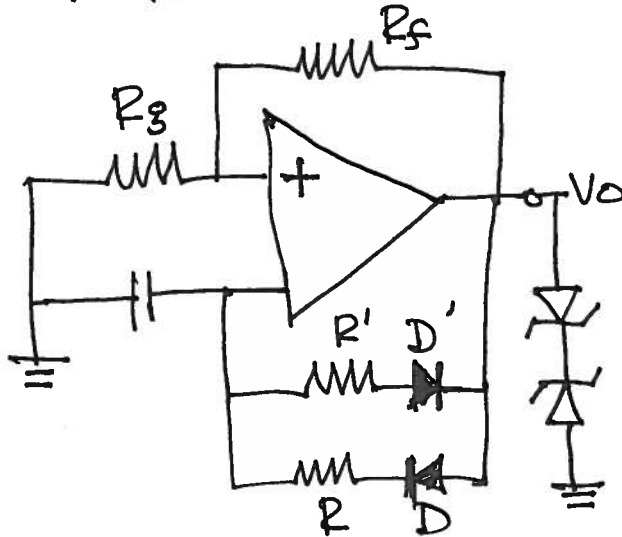- ONE OPTION IS BY MAKING $V_{OL} \neq V_{OH}$
- ANOTHER OPTION IS BY CHANGING THE EQUALITY OF RISING AND DECAYING TIMES.




THEN ONE CAN SHOW THAT

$$T = t_H + t_L$$


$$T = RC \ln \left(1 + \frac{2R_3}{R_f} \right) + R'C \ln \left(1 + \frac{2R_3}{R_f} \right)$$

$$\text{DUTY CYCLE} \triangleq \frac{t_H}{T} = \frac{R}{R+R'}$$

BASIC TRIANGULAR/SQUARE WAVE GENERATOR

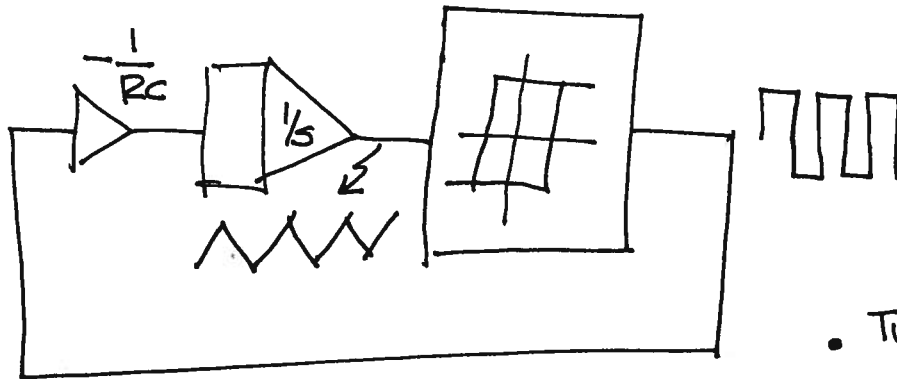

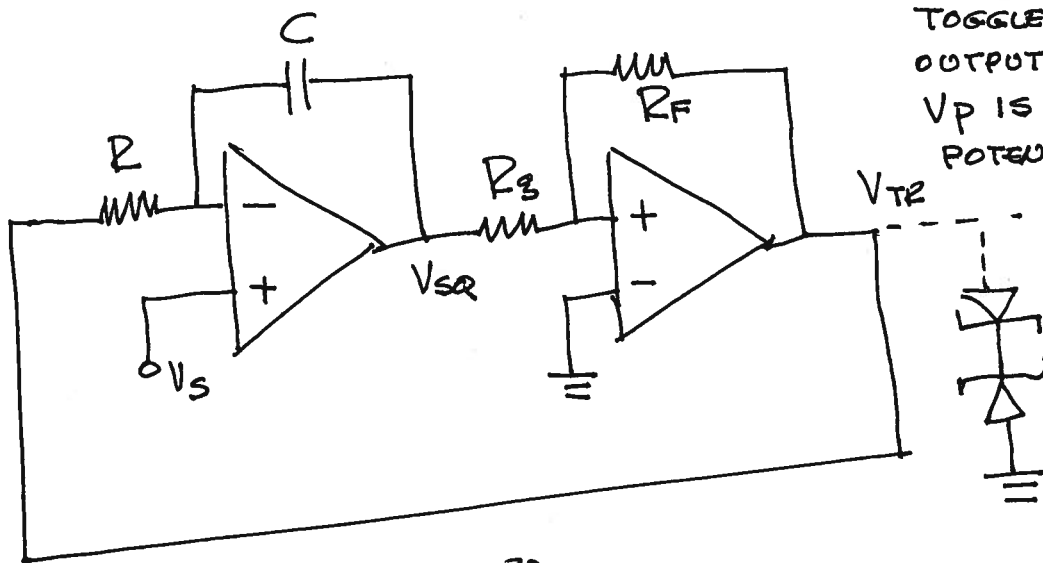- TWO QUASI-STATIC STATES - FOR V_{OH} AND V_{OL}
- THE SCHMITT TRIGGER TOGGLES BETWEEN OUTPUT STATES WHEN V_P IS AT GROUND POTENTIAL.



TRANSITION OCCURS

$$V_{TR(\text{trans})} = -\frac{R_3}{R_f} V_{sq} = +\frac{R_3}{R_f} V_{OH}$$

$$V_{TR} = -\frac{1}{RC} \int [V_{sq}(t) - V_s] dt$$

WHEN, V_{sq} IS IN THE HIGH STATE, V_{TR} IS LINEARLY DECREASING BETWEEN ITS TOGGLE VALUES:

$$V_{TR} = -\frac{1}{RC} \int (V_{OH} - V_s) dt = \frac{V_s - V_{OH}}{RC} t + V_{TR}(0^+)$$

↑ initial condition

THUS, THE ^{VOLTAGE} TRANSITION IS THE DIFFERENCES IN THRESHOLD VALUES DIVIDED BY THE SLOPE OF THE LINEAR TRANSITION.


$$2 \frac{R_g}{R_f} V_{OH} = \frac{V_{OH} - V_s}{RC} t_-$$

THEREFORE

$$t_- = \frac{2R_g V_{OH} \cdot RC}{R_f (V_{OH} - V_s)}$$

NOW WHEN THE POSITIVE TRANSITION OCCURS

FOR $V_s > 0$

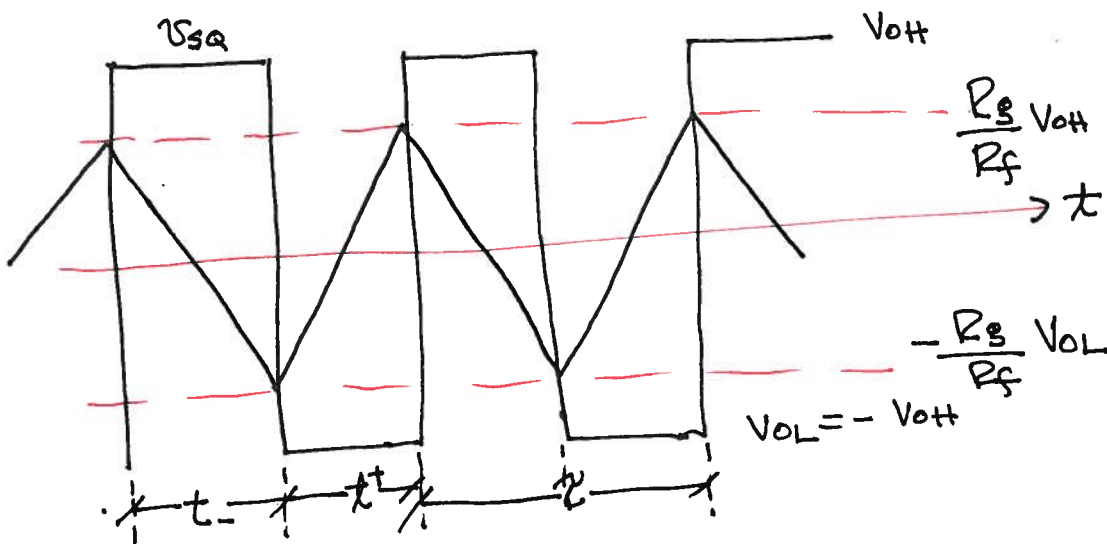

$$V_{xr} = -\frac{1}{RC} \int - (V_{OH} + V_s) dt = \frac{V_{OH} + V_s}{RC} t + V_{xr}(0^-)$$

$$2 \frac{R_g}{R_f} V_{OH} = \frac{V_{OH} + V_s}{RC} t_+ \Rightarrow t_+ = \frac{2R_g RC V_{OH}}{R_f (V_{OH} + V_s)}$$

THUS THE PERIOD BECOMES:

$$T = t_- + t_+ = 4R_g RC \frac{V_{OH}^2}{R_f (V_{OH}^2 - V_s^2)}$$

$$\text{DUTY CYCLE}^+ = \frac{t_+}{T} = \frac{1}{2} \left(1 - \frac{V_s}{V_{OH}} \right)$$