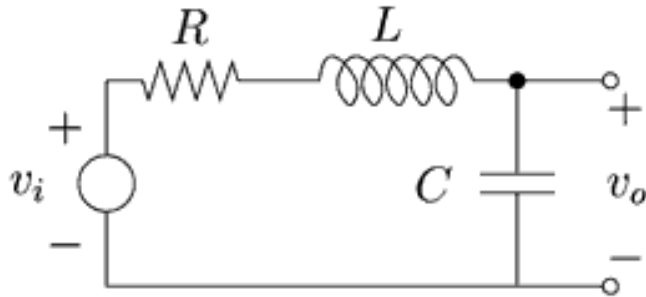


The two-integrator loop

Courtesy of Jorge Zarate

The standard form



$$\frac{v_o}{v_i} = \frac{1/sC}{R + sL + 1/sC} \rightarrow \frac{1/LC}{s^2 + R/Ls + 1/LC}$$

- IF the circuit is lossless ($R=0$), the poles:

$$s_{1,2} = \pm j \frac{1}{\sqrt{LC}} = \pm j\omega_o$$

- Similarly to the Q of an inductor:

$$Q = \frac{\omega_o L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

- Using our definitions: $\frac{v_o}{v_i} = \frac{\omega_o^2}{s^2 + \omega_o/Q s + \omega_o^2}$

The second order circuit

- With an active implementation (gain -H) and normalizing to $s_n = s/\omega_o$.

$$\frac{v_{LP}}{v_i} = \frac{-H}{s_n^2 + 1/Q s_n + 1} \rightarrow v_{LP} (s_n^2 + 1/Q s_n + 1) = -H v_i$$

- In the time domain:

$$\frac{d^2 v_{LP}(t)}{dt^2} + \frac{1}{Q} \frac{dv_{LP}(t)}{dt} + v_{LP}(t) = -H v_i(t)$$

- It is clear that we need two integrations to determine v_{LP} . To identify integration:

$$s \left(s + 1/Q \right) v_{LP} = -(H v_i + v_{LP})$$
$$s v_{LP} = - \frac{1}{\left(s + 1/Q \right)} (H v_i + v_{LP}) = v_{BP}$$

- Now, v_{LP} can be obtained if v_{BP} is integrated

$$s v_{LP} = -\frac{1}{\left(s + 1/Q\right)} (H v_i + v_{LP}) = v_{BP}$$

$$v_{LP} = \frac{1}{s} v_{BP} = \frac{1}{s} \left[-\frac{1}{\left(s + 1/Q\right)} (H v_i + v_{LP}) \right]$$

- To further simplify:

$$-(H v_i + v_{LP}) = \left(s + 1/Q\right) v_{BP}$$

$$v_{BP} = -\frac{1}{s} (H v_i + v_{LP} + 1/Q v_{BP}) = -\frac{1}{s} v_{HP}$$

- Now we can see that v_{BP} can be obtained by integrating with a sign of inversion v_{HP} .


- Where v_{HP} is nothing but the sum of three scaled voltages

$$v_{HP} = (Hv_i + v_{LP} + 1/Q v_{BP})$$

- Backing up:
 - We said we could get v_{LP} by integrating v_{BP}
 - And that v_{BP} is obtained by integrating, with a negative sign, v_{HP}
 - And v_{HP} is the summation of three scaled voltages, therefore:

$$v_{LP} = \frac{1}{s} \left[\left(-\frac{1}{s} \right) v_{HP} \right]$$

Block diagram

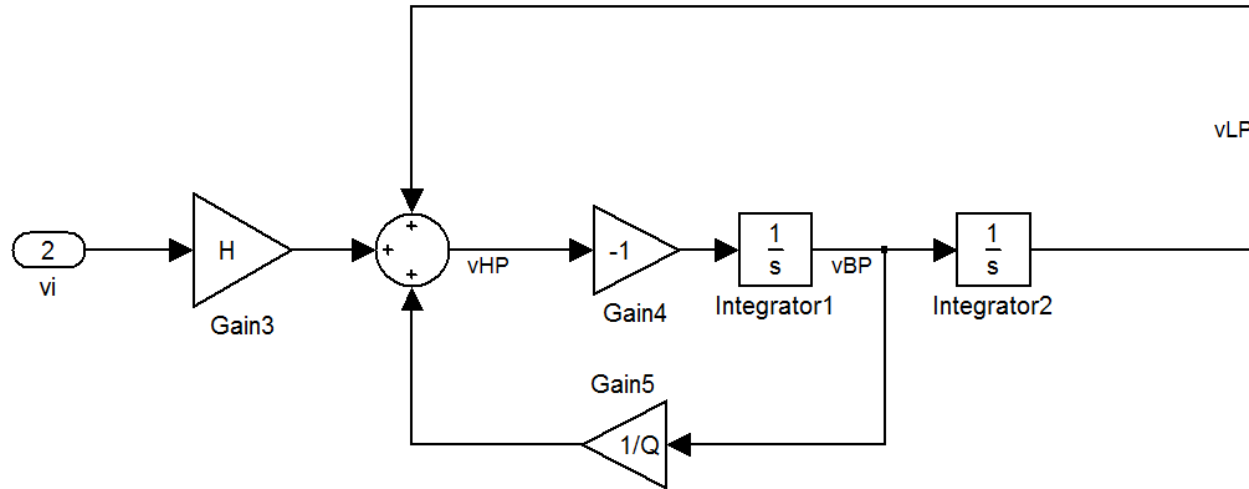


$$v_{LP} = \frac{-H}{s_n^2 + 1/Q s_n + 1} v_i$$

$$v_{BP} = \frac{-Hs}{s_n^2 + 1/Q s_n + 1} v_i$$

$$v_{HP} = \frac{Hs^2}{s_n^2 + 1/Q s_n + 1} v_i$$

Tow-Thomas

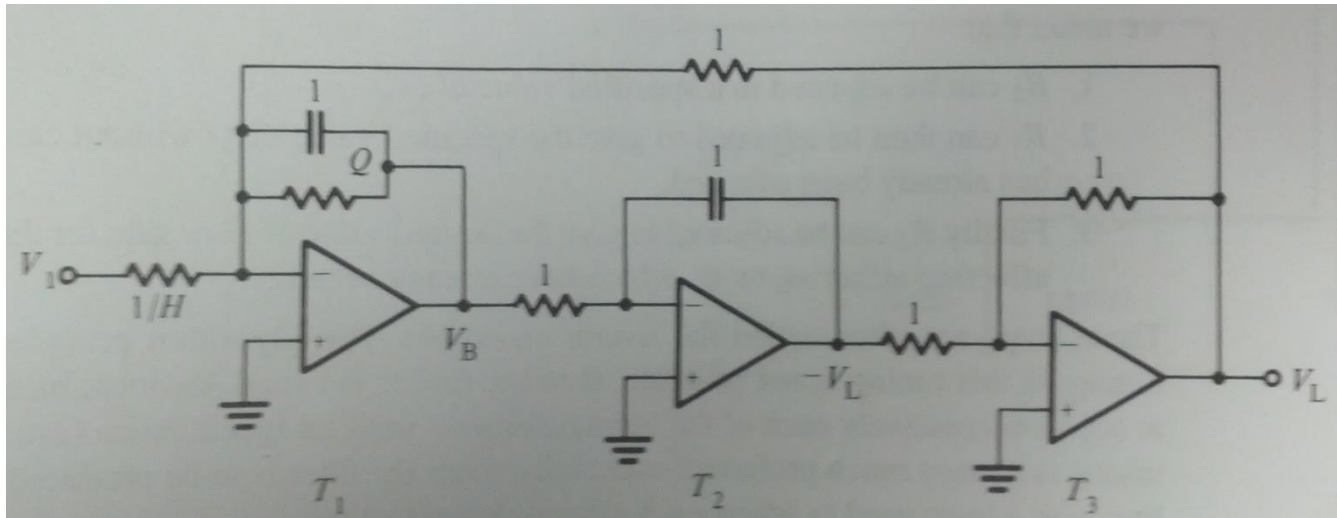
- Block diagram calls for a lossy inverting integrator and for an ideal non-inverting integrator
- Replace the ideal non-inverting for an ideal inverting + inverting amplifier



- Where is the high-pass output?

Feed-forward Tow-Thomas


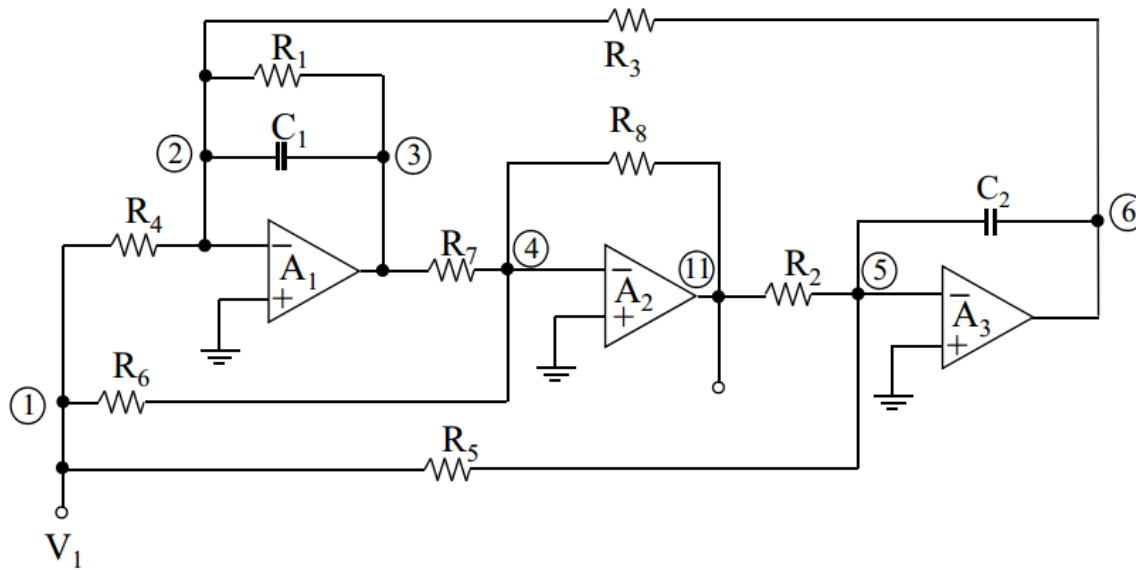
- Single-point output, multiple functions can be achieved



$$\frac{v_o}{v_i} = -\frac{R_8}{R_6} \frac{s^2 + \left(\frac{1}{R_1 C_1} - \frac{R_6}{R_4 R_7 C_1} \right) s + \frac{R_6}{R_3 R_5 R_7 C_1 C_2}}{s^2 + \left(\frac{1}{R_1 C_1} \right) s + \frac{R_8}{R_2 R_3 R_7 C_1 C_2}}$$

Simulink

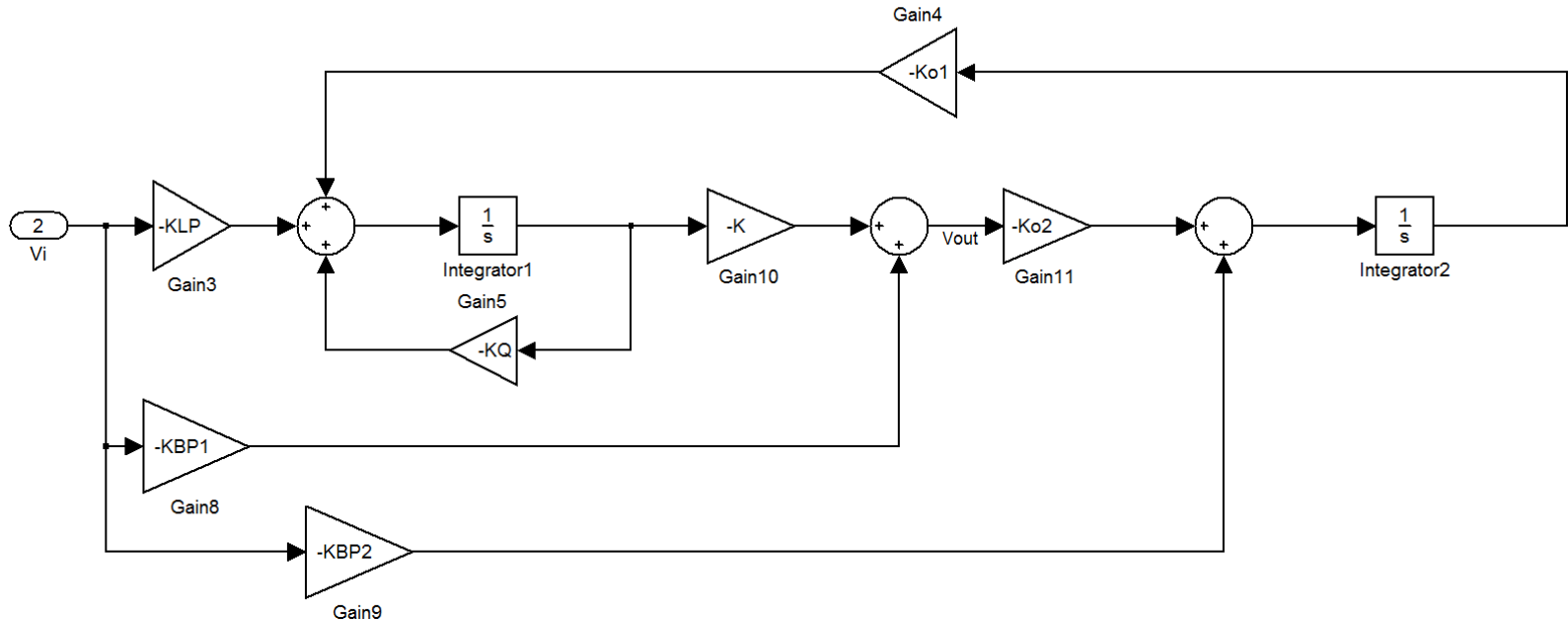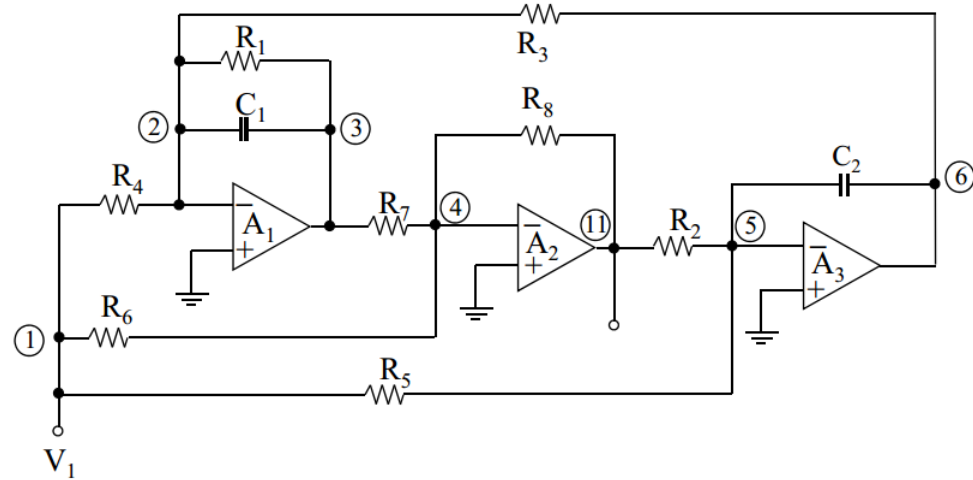- Obtain V_{out}/V_i or $(V11/V_i)$, whatever is easier for you, also, map the blocks to gain/integrators time constants



Mason's Rule

- Direct paths:


$$1) -\frac{KLP}{s} \cdot -K \qquad 2) -KBP1 \qquad 3) -KBP2 \cdot -\frac{K}{s} \cdot -\frac{Ko1}{s}$$

- Loops:

$$1) -\frac{KQ}{s} \qquad 2) \frac{-K \cdot -Ko1 \cdot -Ko2}{s^2}$$

$$\frac{v_o}{v_i} = \frac{\frac{(KLP)K}{s} - \frac{(KBP2)K(Ko1)}{s^2} - KBP1 \left(1 + \frac{KQ}{s}\right)}{1 + \frac{KQ}{s} + \frac{KKo1Ko2}{s^2}}$$
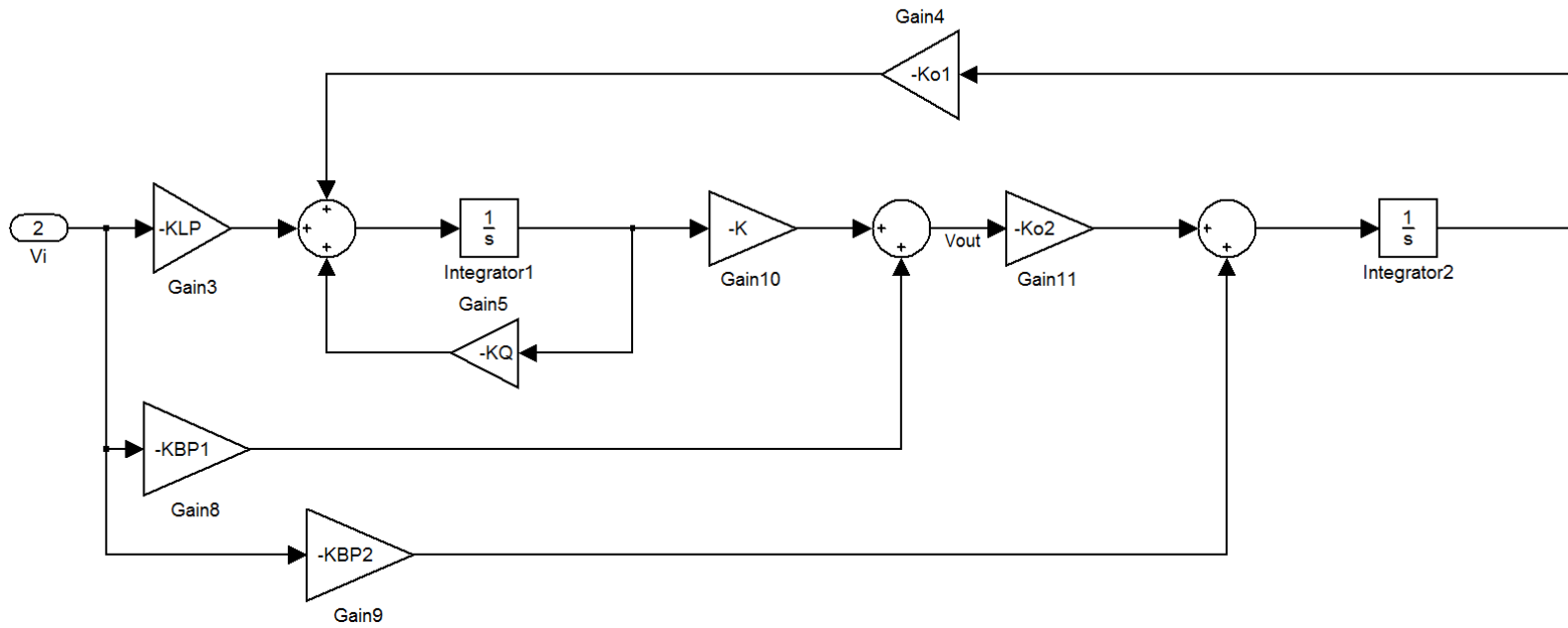
$$\frac{v_o}{v_i} = -KBP1 \frac{s^2 + \left(KQ - \frac{(KLP)K}{KBP1}\right)s + KBP2(Ko1)K}{s^2 + KQs + KKo1Ko2}$$



$$KQ = \frac{1}{R_1 C_1}$$

$$KLP = \frac{1}{R_4 C_1}$$

$$KBP1 = \frac{R_8}{R_6}$$

$$KBP2 = \frac{1}{R_5 C_2}$$

$$K = \frac{R_8}{R_7}$$

$$Ko1 = \frac{1}{R_3 C_1}$$

$$Ko2 = \frac{1}{R_2 C_2}$$

