



Voltage References/Regulators



PART 1

ECEN 457: Op-Amps and Applications
Analog & Mixed-Signal Center
Texas A&M University

Agenda

- Motivation
- Important Definitions

Voltage Regulator Market

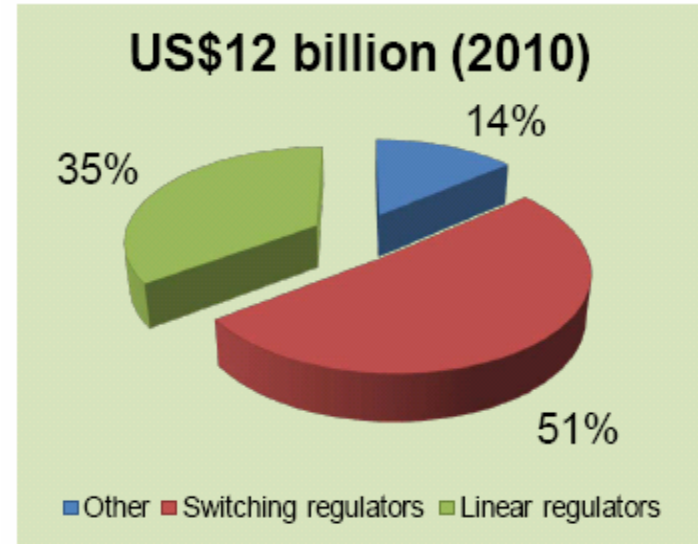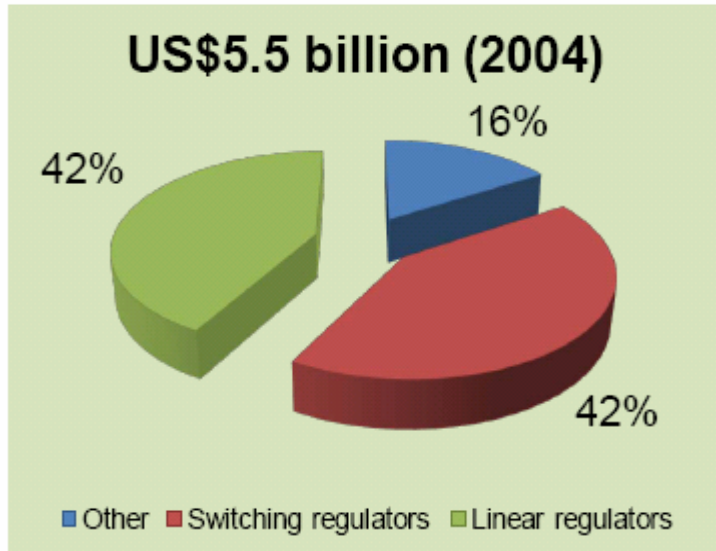


Major Companies:

- ✓ Texas Instruments
- ✓ STMicroelectronics
- ✓ Toshiba
- ✓ Maxim
- ✓ Linear Technologies

Voltage References/Regulators

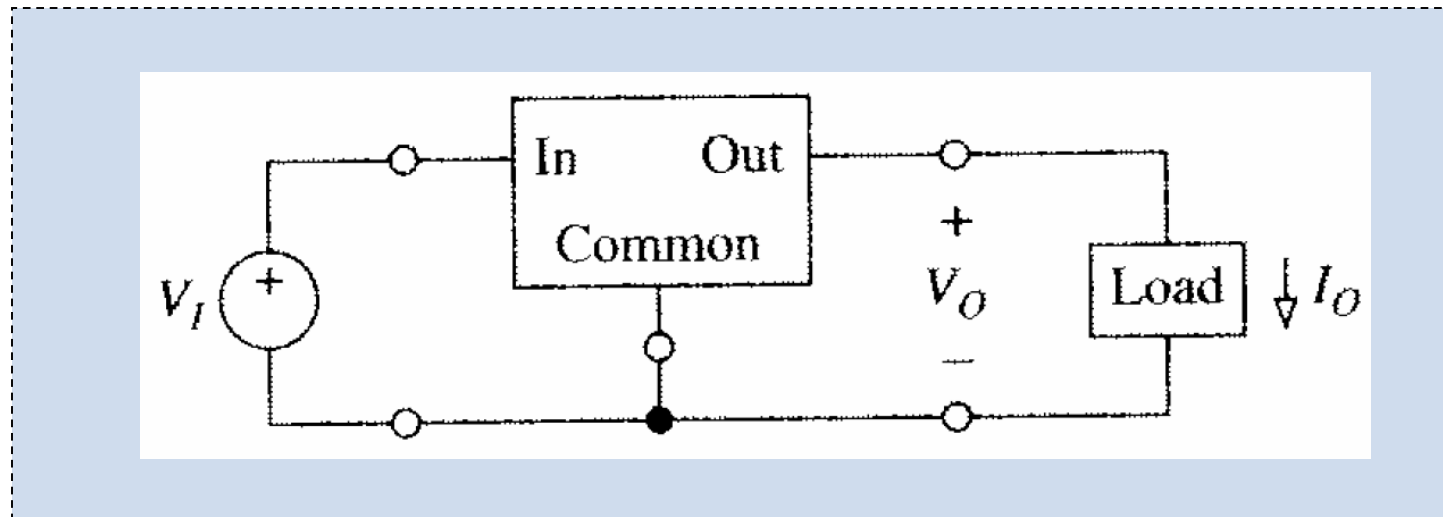- The function of a voltage reference/regulator:
 - Provide stable dc voltage V_O starting from a less stable voltage V_i



Basic connection of a voltage reference/regulator





Voltage References

- **Voltage reference:**
 - Provides an even more stable V_0 to serve as a standard for other circuits.
 - **Application:**
 - Digital multimeter: the full-scale accuracy is set by the internal voltage of suitable quality.
 - **Other applications:**
 - Power supplies
 - AD/DA converters
 - V-F / F-V converters
 - **Main requirements:**
 - Accuracy
 - Stability
 - **To minimize errors due to self-heating:**
 - Modest output-capabilities (few mA)



Voltage Regulators

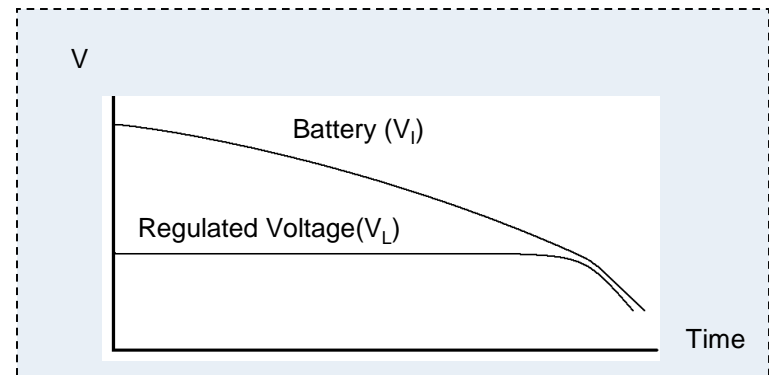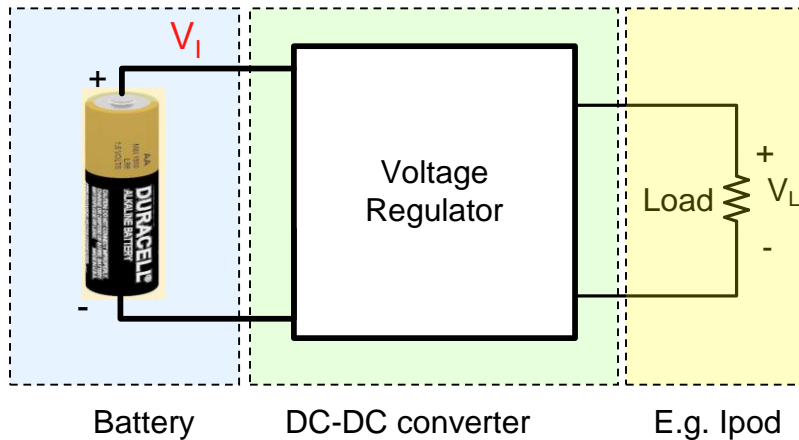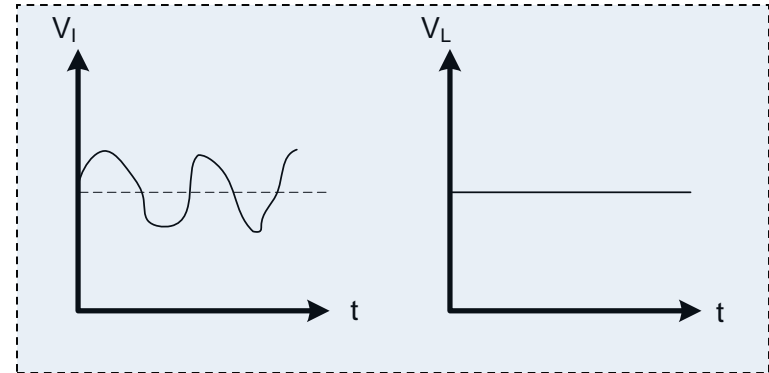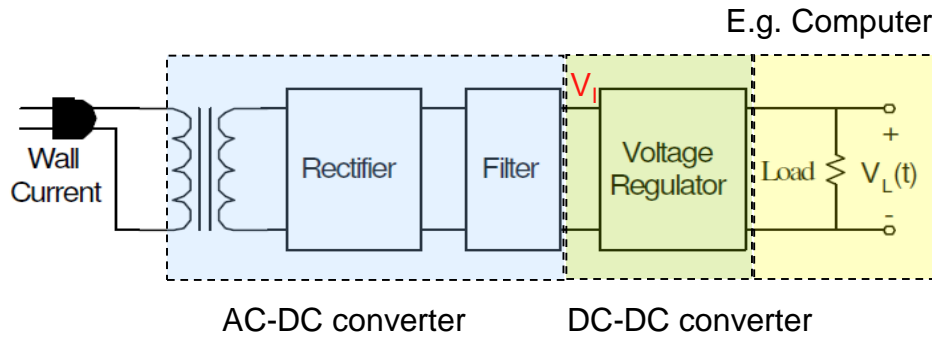- V_I is usually a poorly specified voltage



Requirements:


- Similar to voltage references but less stringent
- Output current capabilities are much higher (100mA-10A)

Voltage Regulators

– Two Types:


- **Linear regulators**

- Simple
- Low noise
- Poor Efficiency

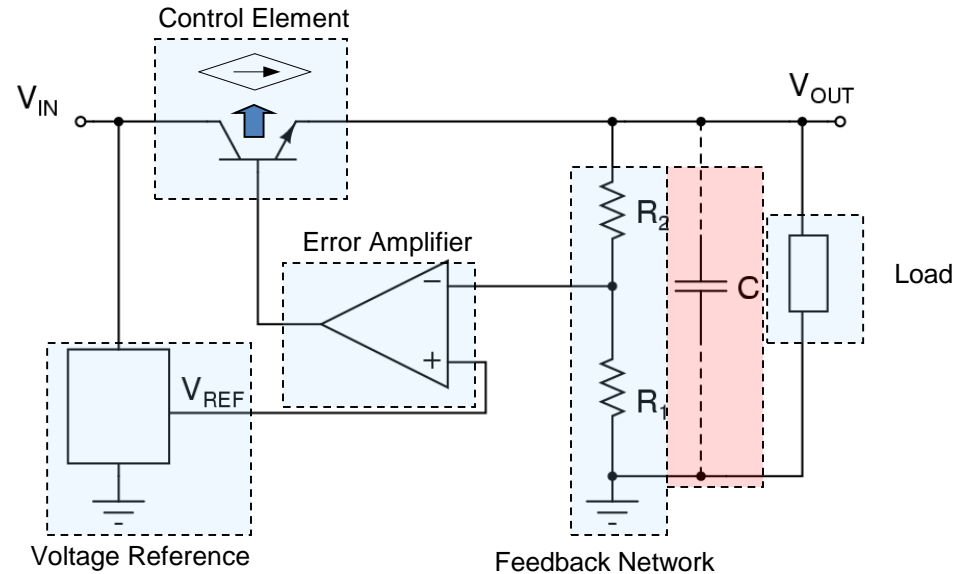

- **Switching regulators**

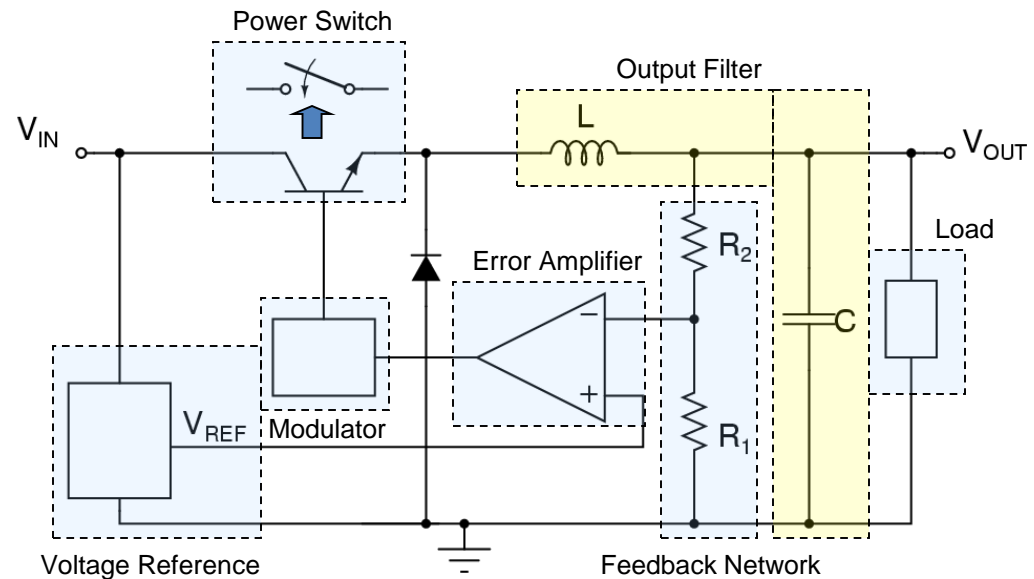- High efficiency
- Output voltage can be:
 - » Negative
 - » Higher than V_I
- Complex
- Require inductors
- Noisier




Important Definitions

- Line Regulation:

$$\text{Line - regulation} = \frac{\Delta V_o}{\Delta V_I}$$

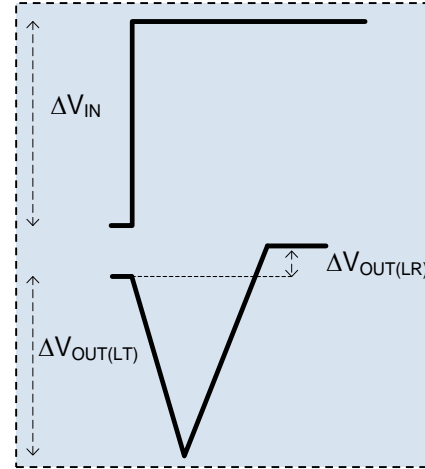
$$\text{Line - regulation}(\%) = \frac{\Delta V_o}{\Delta V_I} \cdot \frac{100}{V_o}$$



- Load Regulation:

$$\text{Load - regulation} = \frac{\Delta V_o}{\Delta I_o}$$
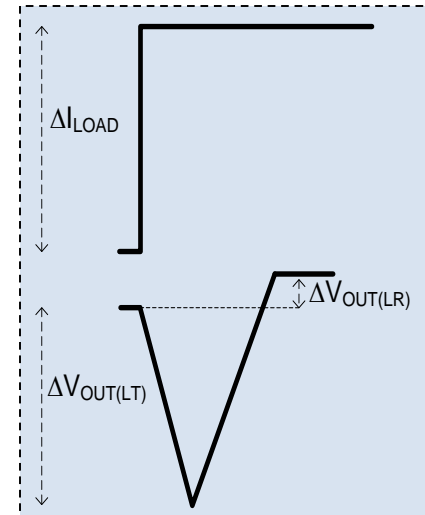
$$\text{Load - regulation}(\%) = 100 \frac{\Delta V_o / V_o}{\Delta I_o}$$



More Definitions

- Ripple (**power supply**) rejection ratio (RRR) (**PSR**):

$$RRR_{dB} = 20 \log_{10} \left(\frac{\Delta V_{ri}}{\Delta V_{ro}} \right)$$

- Dropout Voltage:
 - The minimum difference between V_i and V_o for which the circuit still operates properly.

Example 11.1

- The data sheets of the uA7805 5-V voltage regulator (Fairchild) indicate that V_o typically changes by 3mV when V_i is varied from 7 V to 25 V, and by 5 mV when I_o is varied from 0.25 A to 0.75 A. Moreover, $RRR_{dB} = 78dB$ at 120 Hz.
 - Estimate the typical line and load regulation of this device. What is the output impedance of the regulator?

$$\frac{\Delta V_o}{\Delta V_i} = \frac{3 \times 10^{-3}}{(25 - 7)} = 0.17 \text{ mV/V} \quad \frac{\Delta V_o}{\Delta V_i} (\%) = \frac{0.17 \text{ mV/V}}{5 \text{ V}} \times 100 = 0.0033\% / \text{V}$$

$$\frac{\Delta V_o}{\Delta I_o} = \frac{5 \times 10^{-3}}{(0.75 - 0.25)} = 10 \text{ mV/A}$$

- Estimate the amount of output ripple V_{ro} for every volt of V_{ri} .

$$V_{ro} = \frac{V_{ri}}{10^{(78/20)}} = 0.126 \times 10^{-3} \times V_{ri}$$

For 1-V at 120Hz ripple at the input: $V_{ro} = 0.126 \times 10^{-3} \times 1 = 126 \text{ mV}$

More Definitions

- Thermal Coefficient of V_o :

$$TC(V_o) = \frac{\Delta V_o}{\Delta T}$$

$$TC(V_o)(\%) = \frac{\Delta V_o}{\Delta T} \cdot \frac{100}{V_o}$$

$$TC(V_o) - \text{in} - \text{ppm} = \frac{\Delta V_o}{\Delta T} \cdot \frac{10^6}{V_o}$$

ppm = parts per million

Example 11.2

- The data sheets of the REF101KM 10-V precision voltage reference (Burr-Brown) give a typical line regulation of 0.001%/V, a typical load regulation of 0.001%/mA, and a maximum TC of 1 ppm/C. Find the variation in V_o brought about by: (a) a change of V_i from 13.5 V to 35V; (b) a ± 10 mA change in I_o ; (c) a temperature change from 0 C to 70 C.

– (a)
$$0.001\%/V = \frac{100}{(35-13.5)} \left(\frac{\Delta V_o}{10} \right)$$

$$\Delta V_o = 2.15mV$$

– (b)
$$0.001\%/mA = \frac{100}{(\pm 10mA)} \left(\frac{\Delta V_o}{10} \right)$$

$$\Delta V_o = \pm 1mV$$

– (c)

$$1ppm/C = \frac{10^6}{(70^\circ C)} \left(\frac{\Delta V_o}{10} \right)$$

$$\Delta V_o = 0.7mV$$

More Definitions

- Efficiency

$$\eta \equiv \frac{P_{OUT}}{P_{IN}} = \frac{V_{OUT} I_{OUT}}{V_{IN} (I_Q + I_{OUT})}$$

If $I_Q \ll I_{LOAD}$

$$\eta \approx \frac{V_{OUT}}{V_{IN}} = \frac{V_{IN} - V_{DO}}{V_{IN}} = 1 - \frac{V_{DO}}{V_{IN}}$$

Example: A 3.3 V linear regulator with $3.7 \text{ V} < V_{IN} < 4.7 \text{ V}$, $I_Q = 100 \mu\text{A}$
 $1 \text{ mA} < I_o < 100 \text{ mA}$. What is the minimum drop-out voltage? What is the maximum efficiency? What is the minimum efficiency?

$$\eta_{\max} = \frac{100\text{mA} \times 3.3}{(100\text{mA} + 100\mu\text{A}) \times 3.7} \times 100 = 89.1\% \quad \text{or} \quad \eta_{\max} \approx \left(1 - \frac{0.4\text{V}}{3.7}\right) \times 100 = 89.2\%$$

$$\eta_{\min} = \frac{1\text{mA} \times 3.3}{(1\text{mA} + 100\mu\text{A}) \times 4.7} \times 100 \cong 63.8\%$$

Next Class

- Bandgap voltage reference
- Voltage regulators
 - Shunt voltage regulators
 - Linear regulators