

## SECOND-ORDER FILTER TYPES

- Using a number of first – order and second – order filter blocks, of any type of approximation. one can built higher – order filters.
- We will focus here in the analysis of second-order filters also known as biquads.
- A design procedure for a biquad filter named Tow- Thomas will be presented.

## SECOND-ORDER FILTER TYPES

Second-order blocks are important building blocks since with a combination of them allows the implementation of higher-order filters. The general order transfer function in the s-plane has the form:

$$H(s) = \frac{K_1 s^2 + K_2 s + K_3}{s^2 + \frac{\omega_o s}{Q} + \omega_p^2}$$

Particular conventional cases are:

Lowpass i.e.,  $K_1 = K_2 = 0$

Bandpass i.e.,  $K_1 = K_3 = 0$

Highpass i.e.,  $K_2 = K_3 = 0$

(Notch) Band-Elimination i.e.,  $K_2 = 0$

Allpass i.e.,  $K_1 = 1$ ,  $K_2 = -\frac{\omega_o}{Q}$  and  $K_3 = \omega_o^2$


One interesting case used for amplitude equalization is the “equalizer” sometimes referred to as Bump (DIP) Equalizer. In this case,  $K_1 = 1$   $K_3 = \omega_0^2$  and  $K_2 = \pm k \frac{\omega_0}{Q}$

Specific structures have different properties. Some structures have enough degrees of freedom to allow them to change independently  $\omega_0$ ,  $Q$  (or BW) and a particular gain  $|H(\omega_p)|$  where  $\omega_p$  is a particular frequency, i.e.,  $\omega_p = 0, \omega_0, \infty$  for the LP, BP and HP cases. Furthermore, some structures have the property to have constant  $Q$  or BW while varying  $f_o$ .

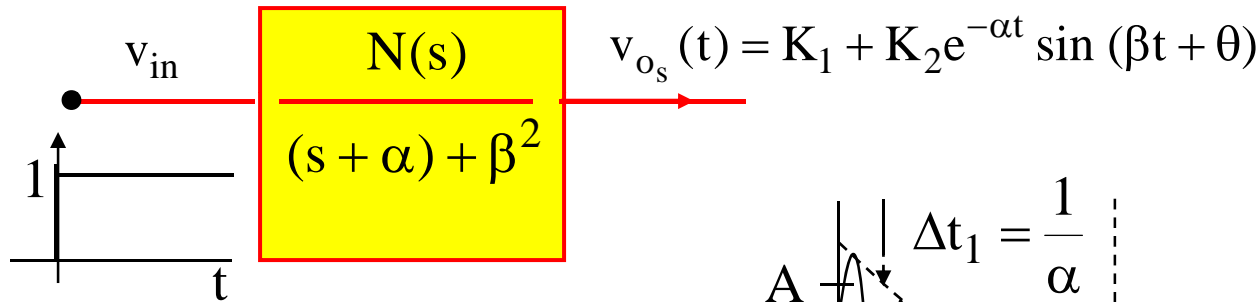
# Properties of Second-Order Systems

$$s^2 + \frac{\omega_o}{Q}s + \omega_o^2 = (s + \alpha)^2 + \beta^2 = s^2 + 2\alpha s + \omega_o^2$$


where  $\alpha = \frac{\omega_o}{2Q}$ ,  $\beta = \omega_o \sqrt{1 - \frac{1}{4Q^2}}$



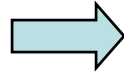How to determine the pole location from a step response?



$$K_1, K_2 = f(N(s))$$




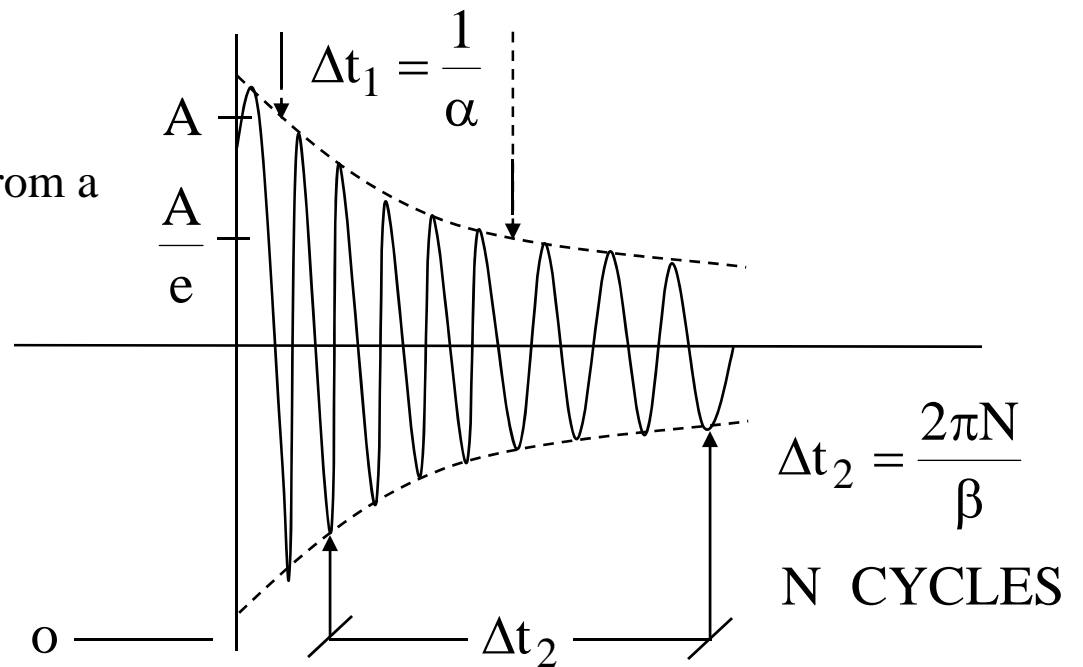


# Pole locations and properties

$$\alpha = \frac{1}{\Delta t_1}$$

and


$$\beta = N \frac{2\pi}{\Delta t_2}$$

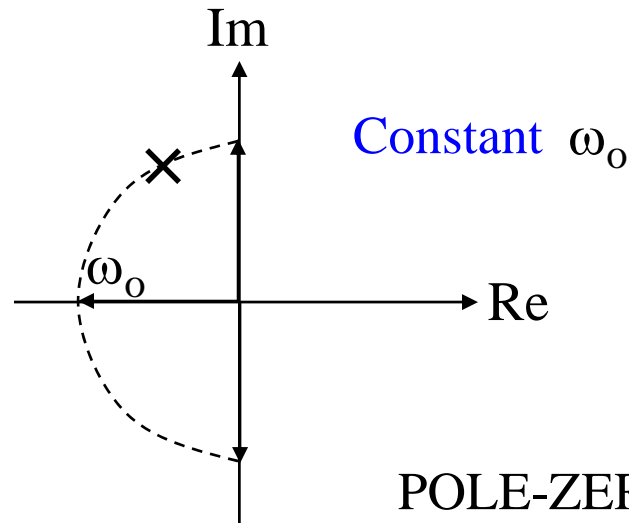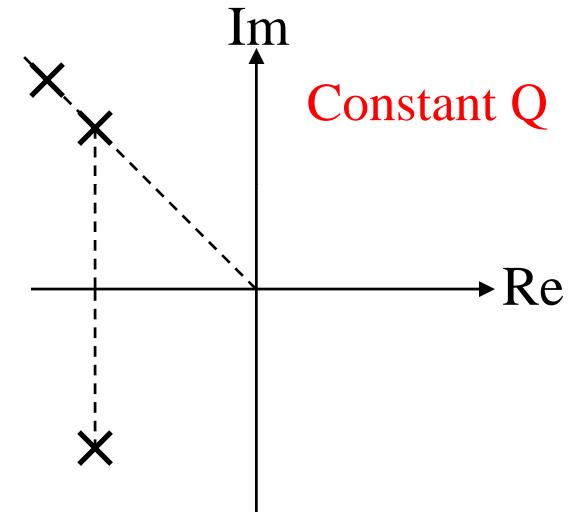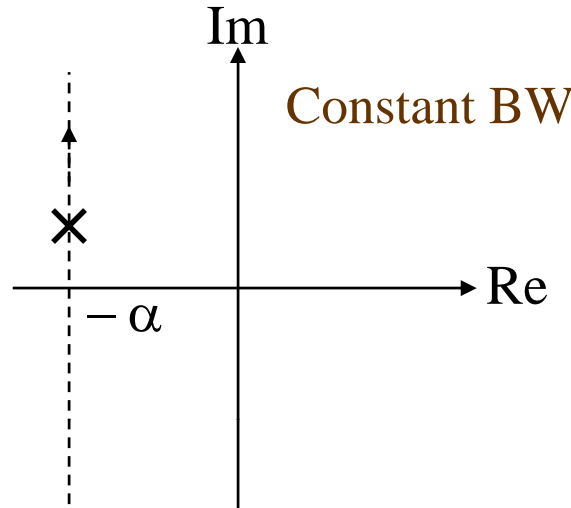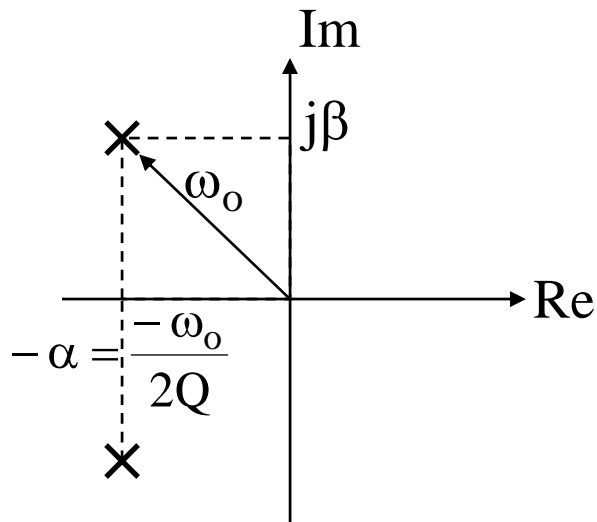

POLE-ZERO LOCI
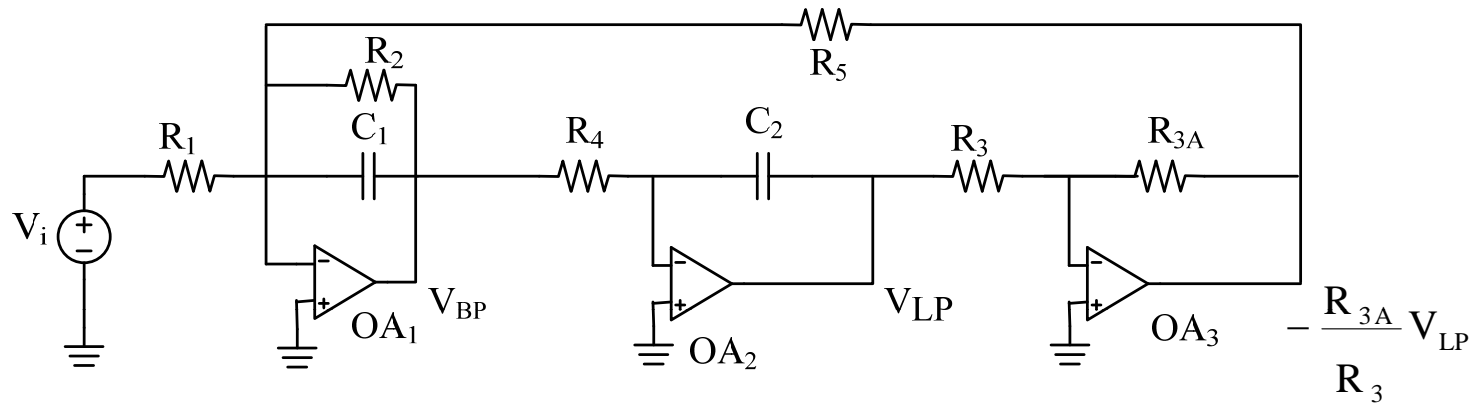
## The Biquad Filter

This is a two integrator loop that can implement two real or complex poles. Zeros can be also achieved if an additional summer is added.



Using KCL at the inverting  $-$  input of  $OA_1$  can write

$$\frac{V_i}{R_1} + V_{BP} \left( \frac{1}{R_2} + sC_1 \right) - \frac{\frac{R_{3A}}{R_3} V_{LP}}{R_5} = 0 \quad (1)$$

$$V_{LP} = -V_{BP} \frac{1}{sC_2 R_4} \quad (2)$$

Solving (1) and (2) yields:

$$H_{BP} = \frac{-Ks}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2} \quad (3)$$

Where

$$K = 1/C_1R_1$$

$$\frac{\omega_o}{Q} = \frac{1}{C_1R_2} \quad \text{or} \quad Q = R_2 \sqrt{\frac{R_{3A}C_1}{R_3C_2R_4R_5}}$$

$$\omega_o^2 = \frac{(R_{3A}/R_3)}{C_1C_2R_4R_5}$$


Using (3) and (2) becomes

$$H_{LP}(s) = \frac{V_{LP}(s)}{V_i(s)} = \frac{-K_s}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2} = \frac{1}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$$

$$H_{LP}(0) = \frac{R_5}{R_1(R_{3A}/R_3)}$$

$$H_{BP}(\omega_o) = -\frac{R_2}{R_1}$$
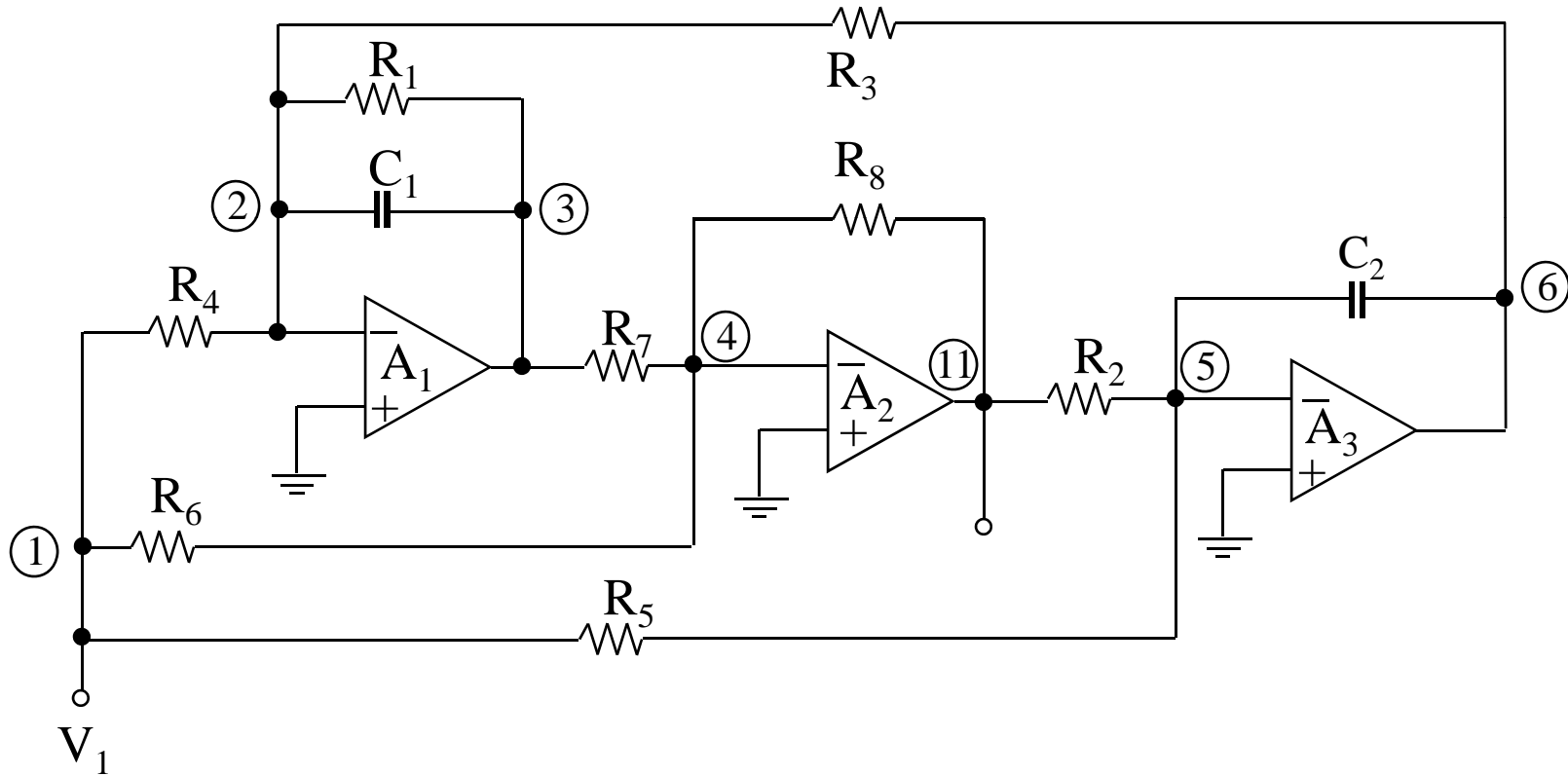
## *Feedforward Tow-Thomas Biquad Circuit*



Analysis using KCL at the input of A1 plus the simple relations of  $V_{11}/V_3$  and  $V_6/V_{11}$  yields the following transfer function.



## Description of the Parameters for the Tow-Thomas Filter

General Transfer Function

$$T(s) = -\frac{R_8}{R_6} \frac{s^2 + \left( \frac{1}{R_1 C_9} - \frac{1}{R_4 C_9} \frac{R_6}{R_7} \right) + \frac{R_6}{R_7} \frac{1}{R_3 R_5 C_9 C_{10}}}{s^2 + s \left( \frac{1}{R_1 C_9} \right) + \frac{R_8}{R_7} \frac{1}{R_3 R_2 C_9 C_{10}}}$$

where

$$\omega_p^2 = \frac{R_8}{R_7 R_2 R_3 C_9 C_{10}}, \quad \omega_z^2 = \frac{R_6}{R_3 R_5 R_7 C_9 C_{10}}$$

$$Q_p = R_1 \sqrt{\frac{R_8 C_9}{R_2 R_3 R_7 C_{10}}}, \quad Q_z = \sqrt{\frac{R_6 C_9}{R_3 R_5 R_7 C_{10}}} / \left( \frac{1}{R_1} - \frac{R_6}{R_4 R_7} \right)$$

and

$$|H_{HP}| = \frac{R_8}{R_6}, \quad \text{for} \quad R_1 = \frac{R_4 R_7}{R_6}, \quad R_5 \rightarrow \infty$$

$$|H_{BP}| = \frac{R_1 R_8}{R_4 R_7}, \quad \text{for} \quad R_5, R_6 \rightarrow \infty$$

$$|H_{LP}| = \frac{R_2}{R_5}, \quad \text{for} \quad R_4, R_6 \rightarrow \infty$$

For the bandstop (notch)

$$|H_{notch}| = \frac{R_8}{R_6}, \quad \text{for} \quad R_1 = \frac{R_4 R_7}{R_6}, \quad R_5 = \frac{R_6 R_2}{R_8}$$

## Design Equations for the Tow-Thomas Filter

Let

$$R_3 = R$$

$$R_2 = a^2 R_3$$

$$R_7 = R_8 = R'$$

$$C_1 = C_2 = C$$

$$\omega_p = \frac{1}{aRC}, \quad \omega = \frac{1}{C} \sqrt{\frac{R_6}{R_5 R R'}}$$

$$Q_p = \frac{R_1}{aR}, \quad Q_z = \sqrt{\frac{R_6}{R_5 R R'}} \left/ \left( \frac{1}{R_1} - \frac{R_6}{R_4 R'} \right) \right.$$

$$|H_{HP}| = \frac{R'}{R_6}, \quad \text{for} \quad R_1 = \frac{R_4 R'}{R_6} = R_4 |H_{HP}|, \quad R_5 \rightarrow \infty$$

$$|H_{HP}| = \frac{R_1}{R_4}, \quad \text{for} \quad R_5, R_6 \rightarrow \infty$$

$$|H_{LP}| = \frac{a^2 R}{R_5}, \quad \text{for} \quad R_4, R_6 \rightarrow \infty$$

$$|H_{\text{notch}}| = \frac{R'}{R_6}, \quad \text{for} \quad R_1 = \frac{R_4 R'}{R_6}, \quad R_5 = \frac{a^2 R R_6}{R'}$$

## PSPICE Input file of Tow Thomas Filter

```
Tow - Thomas Biquad
** Description of the passive components
r1      2      3      1596698
r2     11      5      100000
r3      6      2      100000
r4      2      1      1596698
r7      3      4      100000
r8      4     11      100000
c1      2      3      9.7491D-11
c2      5      6      9.7491D-11
* Description of Op Amps
E1      3      0      0      2      2D5
E2     11      0      0      4      2D5
E3      6      0      0      5      2D5
*
VIN     1      0      AC      1
*
.AC LIN 100 6000      20000
.PLOT AC VDB(11) VP(11)
.PROBE
.END
```

1.0V

```
Tow - Thomas Biquad
** Description of the passive components
r1      2      3      1596698
r2     11      5      100000
r3      6      2      100000
r4      2      1      1596698
r7      3      4      100000
r8      4     11      100000
c1      2      3      9.7491D-11
c2      5      6      9.7491D-11
* Description of Op Amps
E1      3      0      0      2      2D5
E2     11      0      0      4      2D5
E3      6      0      0      5      2D5
*
VIN     1      0      AC      1
*
.AC LIN 100 6000      20000
.PLOT AC VDB(11) VP(11)
.PROBE
.END
```

0.5V

0V

6.0KHz

10KHz

20KHz

□ U(11) ♦ U(6)

Frequency

