

ECEN325: Electronics Summer 2012

Bode Plot Example




Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

RC Transfer Function

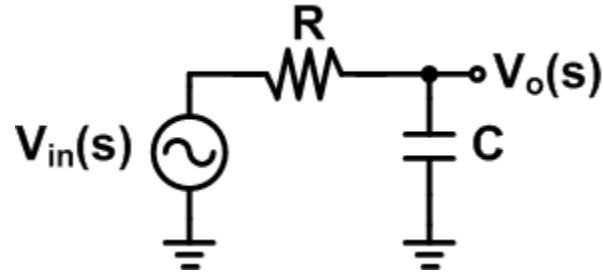

$$V_o(s) = \frac{Z_C}{Z_R + Z_C} V_{in}(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_{in}(s) = \frac{1}{1 + sRC} V_{in}(s)$$

AC Transfer Function, F(S)

$$F(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{1 + sRC}$$

where $s = j\omega = j2\pi f$

Bode Plots


- Technique to plot the **Magnitude** (squared) and **Phase** response of a transfer function
 - Magnitude is plotted in Decibels (dB), which is a power ratio unit

$$|F(j\omega)|^2 \stackrel{dB}{\Rightarrow} 10 \log_{10}(|F(j\omega)|^2) (\text{dB}) = 20 \log_{10}(|F(j\omega)|) (\text{dB})$$

- Phase is typically plotted in degrees

$$\text{Phase}(F(j\omega)) = \tan^{-1} \left(\frac{\text{Im}(F(j\omega))}{\text{Re}(F(j\omega))} \right)$$

RC Bode Plot Example

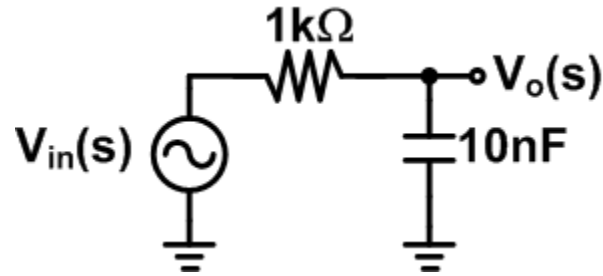

$$F(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{1 + sRC} = \frac{1}{1 + s10^{-5}} = \frac{1}{1 + j\omega 10^{-5}}$$


$$F(s) = \frac{1}{1 + j\omega 10^{-5}} = \frac{1}{1 - \frac{j\omega}{p_1}}, \text{ where } p_1 = -10^5 \text{ rad/s}$$

Magnitude Squared (dB):

$$20 \log_{10} |F(j\omega)| = 20 \log_{10} \left| \frac{1}{\sqrt{1 + (\omega 10^{-5})^2}} \right| = 20 \log_{10}(1) - 20 \log_{10} \left(\sqrt{1 + (\omega 10^{-5})^2} \right)$$

Phase: $\text{Phase}(F(j\omega)) = -\tan^{-1}(\omega 10^{-5})$

RC Bode Plot Example

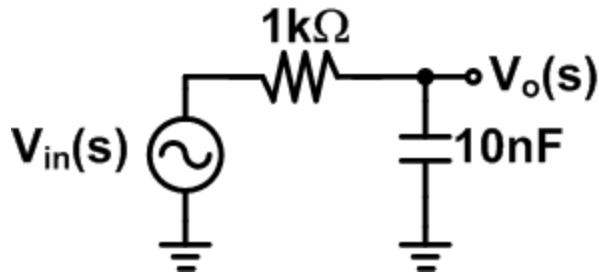

Magnitude:

$$20\log_{10}|F(j\omega)| = 20\log_{10}\left|\frac{1}{\sqrt{1+(\omega 10^{-5})^2}}\right| = 20\log_{10}(1) - 20\log_{10}\left(\sqrt{1+(\omega 10^{-5})^2}\right)$$

Phase: $\text{Phase}(F(j\omega)) = -\tan^{-1}(\omega 10^{-5})$


ω (rad/s)	$ F(j\omega) $	$ F(j\omega) ^2$	$20\log_{10} F(j\omega) $ (dB)	Phase ($F(j\omega)$) (°)
10^3	0.9999	0.9999	~0	~0
10^4	0.995	0.990	-0.043	-5.71
5×10^4	0.894	0.800	-0.969	-26.6
10^5	0.707	0.500	-3.01	-45.0
5×10^5	0.196	0.039	-14.2	-78.7
10^6	0.100	0.010	-20.0	-84.3
10^7	10^{-2}	10^{-4}	-40.0	-89.4
10^8	10^{-3}	10^{-6}	-60.0	-89.9

$\sim 20\log_{10}(1)$
= 0dB

-45°/dec


$\sim -20\log_{10}(\omega 10^{-5})$
= -20dB/dec

RC Bode Plot Example

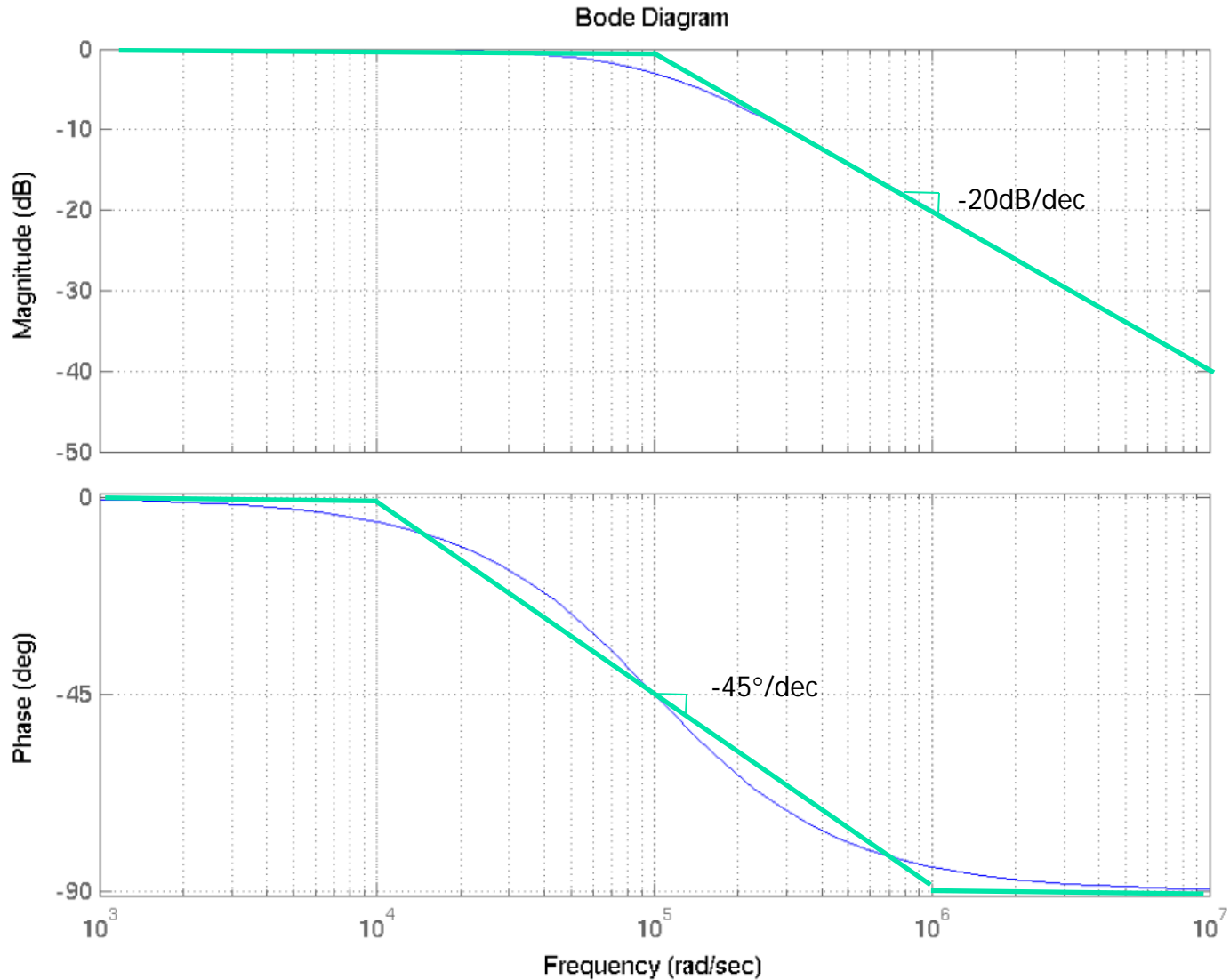


Transient Response

$$\omega = 10^3 \text{ rad/s}$$

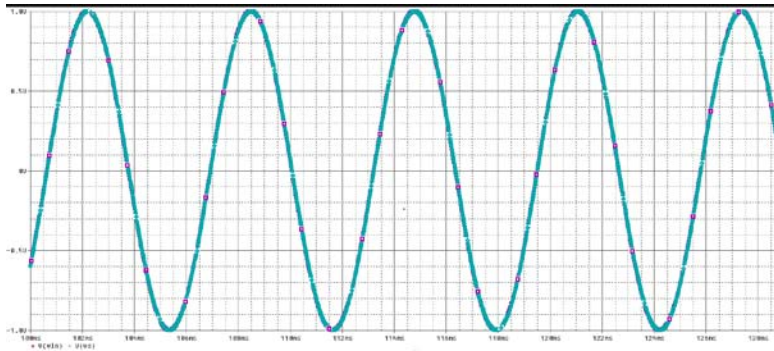

$$\omega = 10^5 \text{ rad/s}$$

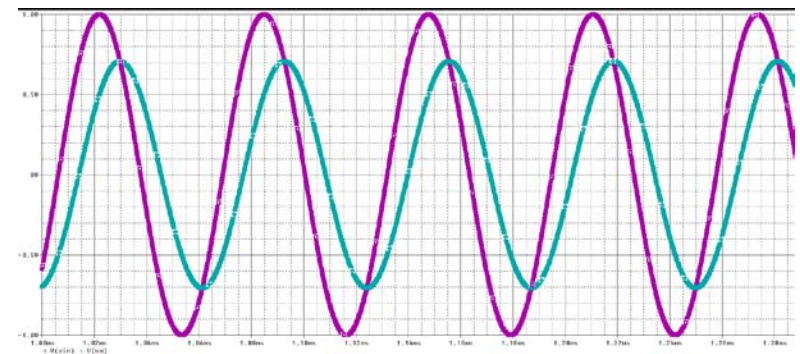

$$\omega = 10^6 \text{ rad/s}$$

