### Texas A&M University Electrical Engineering Department

# ELEN 665 RF Communication Circuits – Laboratory Fall 2010

# Laboratory #6: Analysis and Simulation of a CMOS VCO

**Objectives:** To learn the use of periodic steady state (pss) simulation tools in spectre (cadence) in the characterization of a VCO including its phase noise. To understand the operation of a CMOS LC VCO and analyze its performance trade-offs.

### 1. Schematic setup

Using a library for CMOS 0.5um technology in cadence, create the schematic shown in figure 1. This is an LC-based CMOS voltage controlled oscillator (VCO) which is designed to operate around 1.9GHz. The component values are shown in tables 1-2. The LC tank is formed by inductors L1 and L0 (with a Q factor of around 5 at the resonance frequency of the tank determined by resistors R2, R3), and the varactors implemented with pmos transistors P0 and P1. C0 and C1 represent a load parasitic capacitance. The negative conductance necessary to start and sustain the oscillations is implemented with the cross coupled nmos transistors N0 and N1.



Figure 1. VCO circuit schematic

Transistor	W [um]	L [um]	Multiplicity
N0, N1	9	0.6	8
P0, P1	15	1.2	12
P3, P4	30	1.8	16

#### Table 1. Transistor parameters

#### Table 2. Component values

Component	Value
L0, L1	8n
R2, R3	20ohms
C0, C1	200fF
IBIAS	1mA
VC	2V
VDD	3V

#### 2. Transient simulation

A transient simulation is a relatively fast way to verify the functionality of the VCO and estimate its settling time and output frequency. Run a conservative transient analysis for a period of around 20ns. If the oscillations do not start you may need to add an initial condition to one of the output voltages. Go to the menu Simulation -> Convergence Aids -> Initial Condition... and set one of the output nodes to be few mV higher or lower than its regular operating point.

Plot the output of the oscillator, you can measure the frequency of oscillation using the calculator. Take note of the time it takes to the VCO to have a stable amplitude since this time will be used in the PSS simulations.



Figure 2. Transient response of the VCO

# **3. PSS simulation**

PSS analysis can be used to find the oscillation frequency, spectrum and amplitude of the VCO. To obtain the phase noise, pnoise analysis must also be performed.

**2.1** Simulation setup for the VCO.

Choosing Analyses Virtuoso® Analog D 🕒 回 🛞	Choosing Analyses Virtuoso® Anal 🛛 😂 🖻 😣		
OK Cancel Defaults Apply Help	OK Cancel Defaults Apply Help		
Analysis tran dc ac noise xf sens dcmatch stb pz pz pac pnoise pxf psp qpss qpac qpnoise qpxf qpsp	Analysis       tran       dc       ac       noise         xf       sens       dcmatch       stb         pz       sp       envlp       pss         pac       poise       pxf       psp         qpss       qpac       qpac       qpnoise		
Periodic Steady State Analysis Periodic Noise Analysis			
Fundamental Tones	PSS Beat Frequency (Hz) 26		
# Name Expr Value Signal SrcId	Sweeptype default = Relative Harmonic		
Output Frequency Sweep Range (Hz)			
F1i 20i Large =   Clear/Add Delete Update From Schematic    Beat Frequency  20i   Qi Auto Calculate			
Output harmonics     Sidebands       Number of harmonics     Sideband			
Accuracy Defaults (empreset)	Output Positive Output Node /net080 Select		
Additional Time for Stabilization (tstab) 20rř	Negative Output Node /net04g Select		
Save Initial Transient Results (saveinit) _ no _ yes Input Source			
Oscillator Mode /net080 Select Reference node /net049 Select	Noise Type sources = sources: single sideband (SSB) noise analysis		
Enabled Detions	Enabled Options		

Figure 3. PSS and phoise simulation setups

# NOTE:

- The positive and negative output nodes are the drain/gate terminals of transistors N0 and N1.
- It is very important to choose a conservative analysis to obtain accurate phase noise simulation results. Choosing moderate analysis can change the results by a number of dBs.
- Choose the time for stabilization according to the results of your transient simulation.
- The fundamental frequency in this case is just a starting assumption. PSS will accurately find the actual period of the oscillations.

When the simulation is finished, configure the results window as shown in figure 3.

Direct Plot Form	Direct Plot Form 🕞 🗐 😣
OK Cancel Help	OK Cancel Help
Plotting Mode Append =	Plotting Mode Append =
Analysis	Analysis
◆ pss ◇ pnoise	◇ pss ◆ pnoise
Function	Function
Voltage Current     Dower Voltage Cain	🔷 Output Noise 🔷 Input Noise
Current Gain	🔷 Noise Figure 🔷 Noise Factor
	♦ NFdsb
Compression Point IPN Curves	A Phase Noise     Transfer Function
✓ Power Contours ✓ Reflection Contours ✓ Harmonic Frequency  ✓ Power Added Eff.	
♦ Power Gain Vs Pout ♦ Comp. Vs Pout	Add To Outputs 🗌 Plot
$\diamond$ Node Complex Imp. $\diamond$ THD	> Press plot button on this form
Select Net	
Sweep	
◆ spectrum ◇ time	
Signal Level 🔺 peak 🔷 rms	
Modifier	
♦ Magnitude ♦ Phase ♦ dB20	
🔷 Real 🔷 Imaginary	
Add To Outputs 🗌 Replot	
> Select Net on schematic	

Figure 4. PSS results setup

Select one of the differential outputs to plot the single ended output voltage as shown below.



Periodic Steady State Response

#### 4. Parametric simulation

To observe the behavior of the VCO with respect to the tuning voltage, a parametric simulation can be used. Set the control voltage as a variable and sweep in the range shown in figure 7. Keep both, the transient and the PSS simulations active with the same settings as in sections 2 and 3. The simulation results (output waveform and phase noise) will show multiple curves. To obtain parametric plots like the ones shown in figures 7 to 9, use the calculator and select the curves with the button 'family'. Then apply the corresponding command: 'frequency', 'ymax' and 'value' interpolated at 1M (for the phase noise).



Figure 7. Frequency of oscillation Vs. VC







Figure 9. Phase noise Vs. VC

# 5. VCO analysis

5.1 Explain the role of varactors on VCO performance such as tuning range, quality factor, linearity of gain, etc.

5.2 Explain how each of the main design variables (bias current, gm of the cross-coupled transistors and Q factor of the LC tank) affect the oscillation amplitude and the phase noise. For a given bias current, what are the trade-offs involved in the choice of the W/L for the nmos transistors?

5.3 Change the Q factor of the modeled inductor from 5 to 9 and obtain parametric plots like the ones shown in section 4. How much does the phase noise change? By how much do you need to change the bias current to obtain the same phase noise as with a Q of 5?

5.4 Measure the Q of the tank. From the measured Q and the gm, and bias current obtained from a DC simulation, estimate the phase noise @1MHz offset. How does this estimation compare with the simulation results?

5.5 Using ASITIC design an inductor for the 1.9GHz VCO. Use the extracted model, measure the new Q of the tank and re-design the VCO to obtain a phase noise of -119dBc at 1MHz for a 1.9GHz output frequency. Show a complete characterization of your re-designed VCO.

# **Final Remarks:**

The due date for your report submission is the beginning of next week's lab.