 


## Homework #3 Problem 2 Solution

### Divide-by-31/32



$MC=1 \rightarrow \div 32$

The circuit is not sensitive to the  $MF$  signal and the first synchronous divider always divides by 4.

$MC=0 \rightarrow \div 31$

The circuit is now sensitive to the  $MF$  signal, which will go low 1 out of every 8 cycles due to the asynchronous divide-by-8 second stage. This causes the first synchronous stage to divide by 4 seven times and 3 once, resulting in an overall divide-by-31 operation.

