## ECEN 620

Homework #4

Due: 11-7-2023, 11:59PM Homeworks will not be received after due. Instructor: Sam Palermo

1. Let's consider a second-order digital PLL that utilizes the PI filter from Lecture 9.

 $F_{ref}$ =156.25MHz

N=16

 $\Delta_t\!\!=\!\!10ps$ 

 $(V_{FS}/2^B)K_{VCO}=2\pi*5MHz/LSB$ 

- Follow the Lecture 9 design procedure and find the loop filter parameters  $\alpha$  and  $\beta$  for f<sub>u</sub>=5MHz and  $\Phi_m$ =60°.
- Implement a linear macromodel (MATLAB, etc.) for the closed-loop system.
  - Plot the open-loop gain magnitude and phase and find the phase margin.
  - Plot the output phase transfer function (magnitude only) from 10kHz to 1GHz.