

ECEN620: Network Theory Broadband Circuit Design Fall 2023

Lecture 4: Phase Detector Circuits



Sam Palermo
Analog & Mixed-Signal Center
Texas A&M University



Agenda

- Phase Detector Circuits
 - Mixer PD
 - XOR PD
 - J-K Flip-Flop PD
 - Phase-Frequency Detector (PFD)

References


- *RF Microelectronics*, B. Razavi, Prentice Hall, 1998.
- *Design of Integrated Circuits for Optical Communications*, B. Razavi, McGraw-Hill, 2003.
- *Monolithic Phase-Locked Loops and Clock Recovery Circuits*, B. Razavi, Wiley, 1996.
- M. Perrott, *High Speed Communication Circuits and Systems Course*, MIT Open Courseware

Phase Detector

 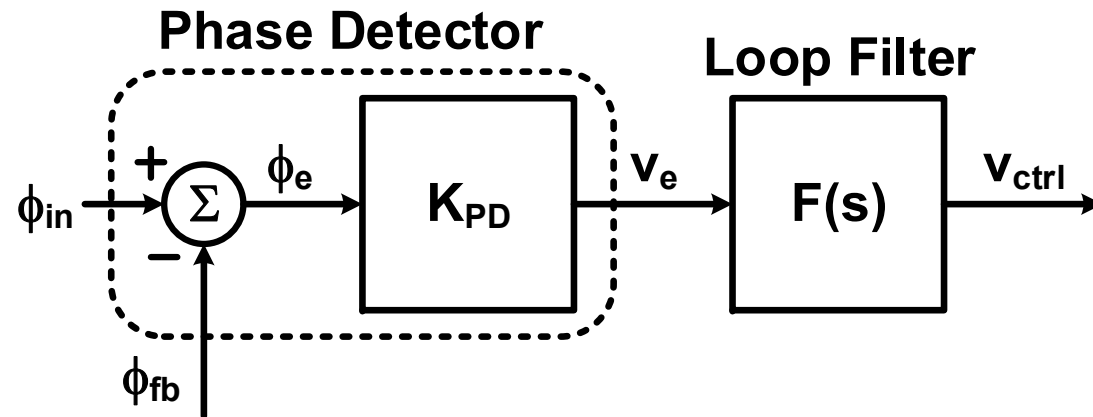

$$\text{avg}\{v_e(t)\} = K_{PD}\Delta\phi$$

 - Detects phase difference between feedback clock and reference clock
- The loop filter will filter the phase detector output, thus to characterize phase detector gain, extract average output voltage
- The K_{PD} factor can change depending on the specific phase detector circuit




K_{PD} units are V/rad when used with a dimension - less filter

K_{PD} units are rad^{-1} (averaged) or A/rad when combined with the charge - pump

when used with a impedance filter


Analog Multiplier Phase Detector

 

- If $\omega_1 = \omega_2$ and filtering out high-frequency term

$$\overline{y(t)} = \frac{\alpha A_1 A_2}{2} \cos \Delta\phi$$

 - Near $\Delta\phi$ lock region of $\pi/2$: $\overline{y(t)} \approx \frac{\alpha A_1 A_2}{2} \left(\frac{\pi}{2} - \Delta\phi \right)$



[Razavi]

Analog Mixer PD Properties

- The nominal lock point (zero frequency offset or Type-2) with a mixer PD is a 90° static phase shift
 - For many applications this is unimportant or can be cancelled elsewhere
- The mixer cannot serve as a frequency detector, as on average the output will be zero for a frequency difference
- K_{PD} is a function of the input amplitude, which is not desired

Mixer Circuits

Active Mixers



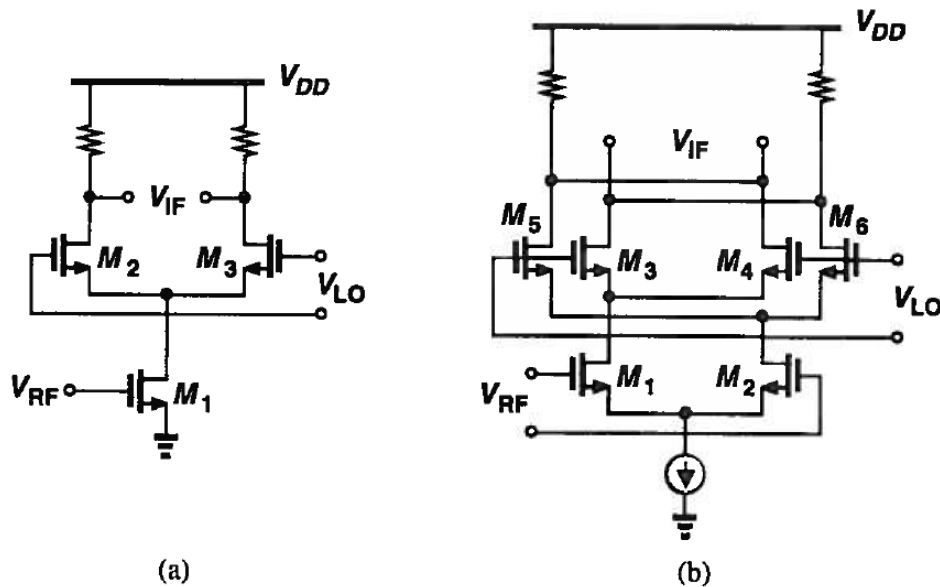


Figure 6.19 (a) Single-balanced mixer, (b) double-balanced mixer.

Passive Mixer

 



XOR Phase Detector

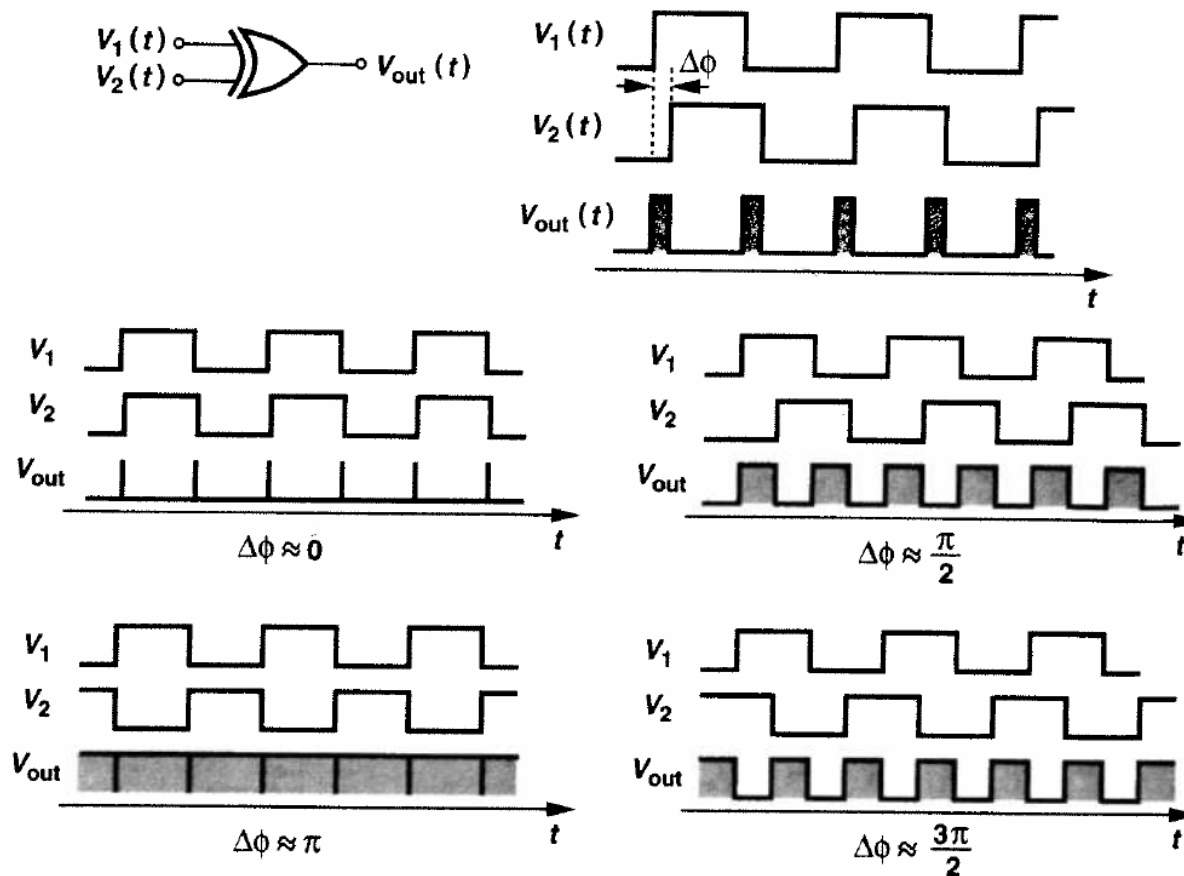

[Razavi]


- Assuming logic 1="+1" and 0="-1", the XOR PD will lock when the average output is 0
 - Generally, $\pi/2$ is a stable lock point and $-\pi/2$ is a metastable point
- Sensitive to clock duty cycle

XOR Phase Detector

  


**Width is same for both
leading and lagging
phase difference!**

[Perrott]

 


Stable vs Metastable Lock Point

 


- The PLL should be configured in negative feedback based on the phase detector gain
- However, the phase detector gain varies as a function of the phase error
- Generally, the PLL is designed to have a stable lock point with a $\pi/2$ phase offset
 - $-\pi/2$ is a metastable lock point because it is in a positive feedback operation range

Cycle Slipping

 - If there is a frequency difference between the input reference and PLL feedback signals the phase detector can jump between regions of different gain
 - PLL is no longer acting as a linear system



Cycle Slipping

 


[Perrott]

- If frequency difference is too large the PLL may not lock



XOR PD Properties

- The nominal lock point with an XOR PD is also a 90° static phase shift
- Unlike the analog mixer, K_{PD} is independent of input amplitude and constant over a π phase range
- The XOR PD is sensitive to input duty cycle, and will lock with a phase error if the input duty cycles are not 50%


J-K Flip-Flop Phase Detector

 


J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

  


J-K Flip-Flop Details

 

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

 

 J-K Flip-Flop Phase Detector Harmonic Locking






- Harmonic signals can display the same DC output, leading to potential locking to harmonics

J-K Flip-Flop PD Properties


- The nominal lock point with an J-K Flip-Flop PD is a 180° static phase shift
- The J-K Flip-Flop PD is not sensitive to input duty cycle
- The J-K Flip-Flop displays a constant KPD over a 2π range
- There is the potential to lock to harmonics of the reference clock

Phase Frequency Detector (PFD)

 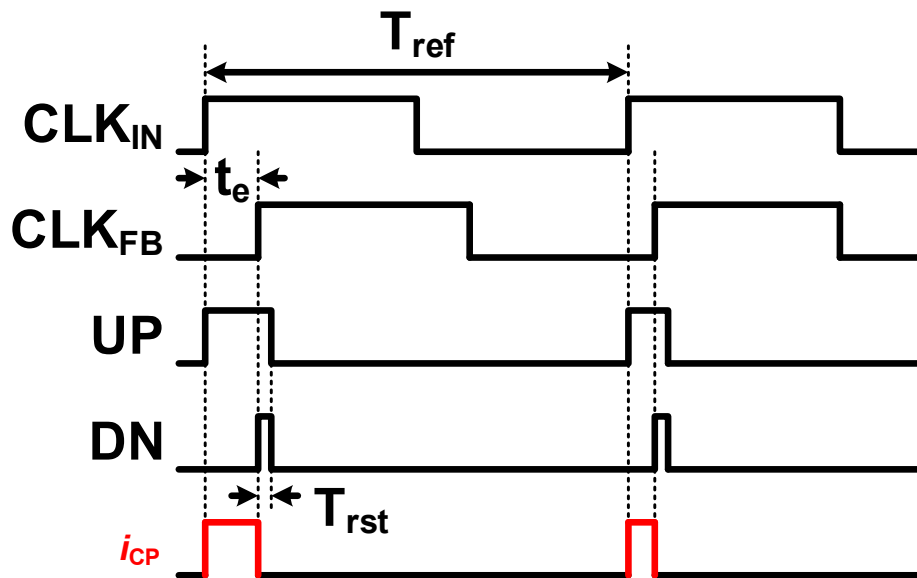 - Phase Frequency Detector allows for wide frequency locking range, potentially entire VCO tuning range
- 3-stage operation w/ UP & DN outputs
- Rising edge-triggered results in duty cycle insensitivity





Averaged PFD Transfer Characteristic

 


- Constant slope and polarity asymmetry about zero phase allows for wide frequency range operation
- The averaged PFD gain is $1/(2\pi)$ with units of rad^{-1}

PFD Deadzone

 
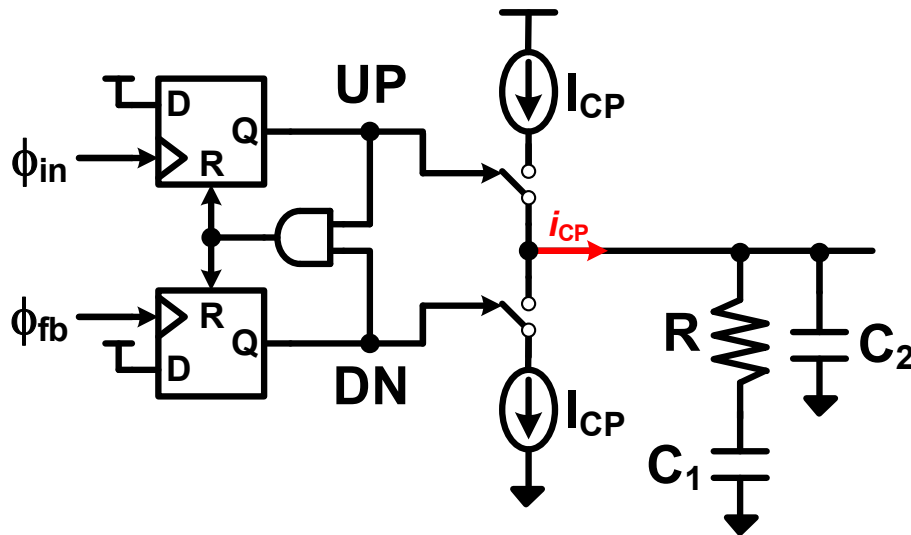


 - If phase error is small, then short output pulses are produced by PFD
- Cannot effectively propagate these pulses to switch charge pump
- Results in phase detector "dead zone" which causes low loop gain and increased jitter






PFD Operation w/ Reset Delay

  - Solution is to add delay in PFD reset path to force a minimum UP and DN pulse length
- In locked state both UP and DN current sources are on for T_{rst} , but ideally no net current is delivered to loop filter




   Problems Near 2π

- PFD cannot react to input rising edges during reset
- This can result in the next rising edge driving the loop in the wrong direction
- Reset delay can increase acquisition time and sets a max PFD operating frequency



 PFD Transfer Characteristic w/ Reset Delay



- PFD reset delay generates wrong frequency information
- If this becomes a large percentage of the reference cycle, then the PFD can fail to acquire frequency lock



$$\text{Max } T_{\text{rst}} = \frac{T_{\text{ref}}}{2}$$

$$\text{Max PFD Frequency} = \frac{1}{2T_{\text{rst}}}$$

PFD Properties

- The nominal lock point with a PFD is 0°
- The PFD is not sensitive to input duty cycle
- The PFD outputs “UP” and “DN” are not complementary and stay high until reset by the other, allowing for efficient frequency detection
- Near lock, the propagation of narrow pulses to switch the charge pump can cause a phase detector “dead zone”
 - To prevent this, extra delay is generally inserted in the PFD reset path

Detailed Optimized PFD Schematic

 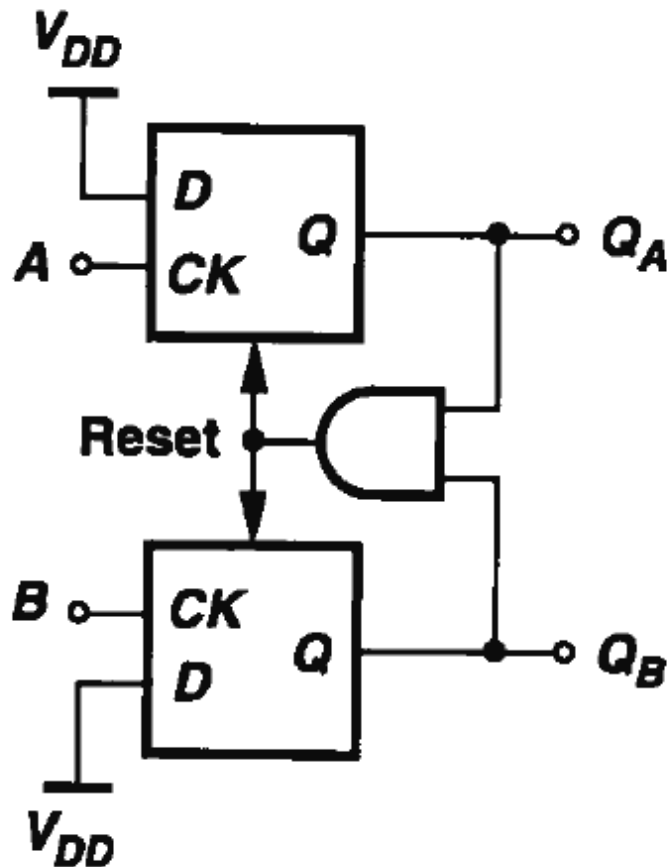

- Because the flip-flop data input is always "1", the logic can be optimized for higher speed operation

Next Time

- Charge Pump Circuits