

# ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

---

## Lecture 10: Termination & Transmitter Circuits



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements

---


- Exam 1 will be second week of March (3/8-12)
- Reading
  - Dally 11.1-11.3

# Agenda

---

- Termination Circuits
- Transmitter Circuits

# High-Speed Electrical Link System

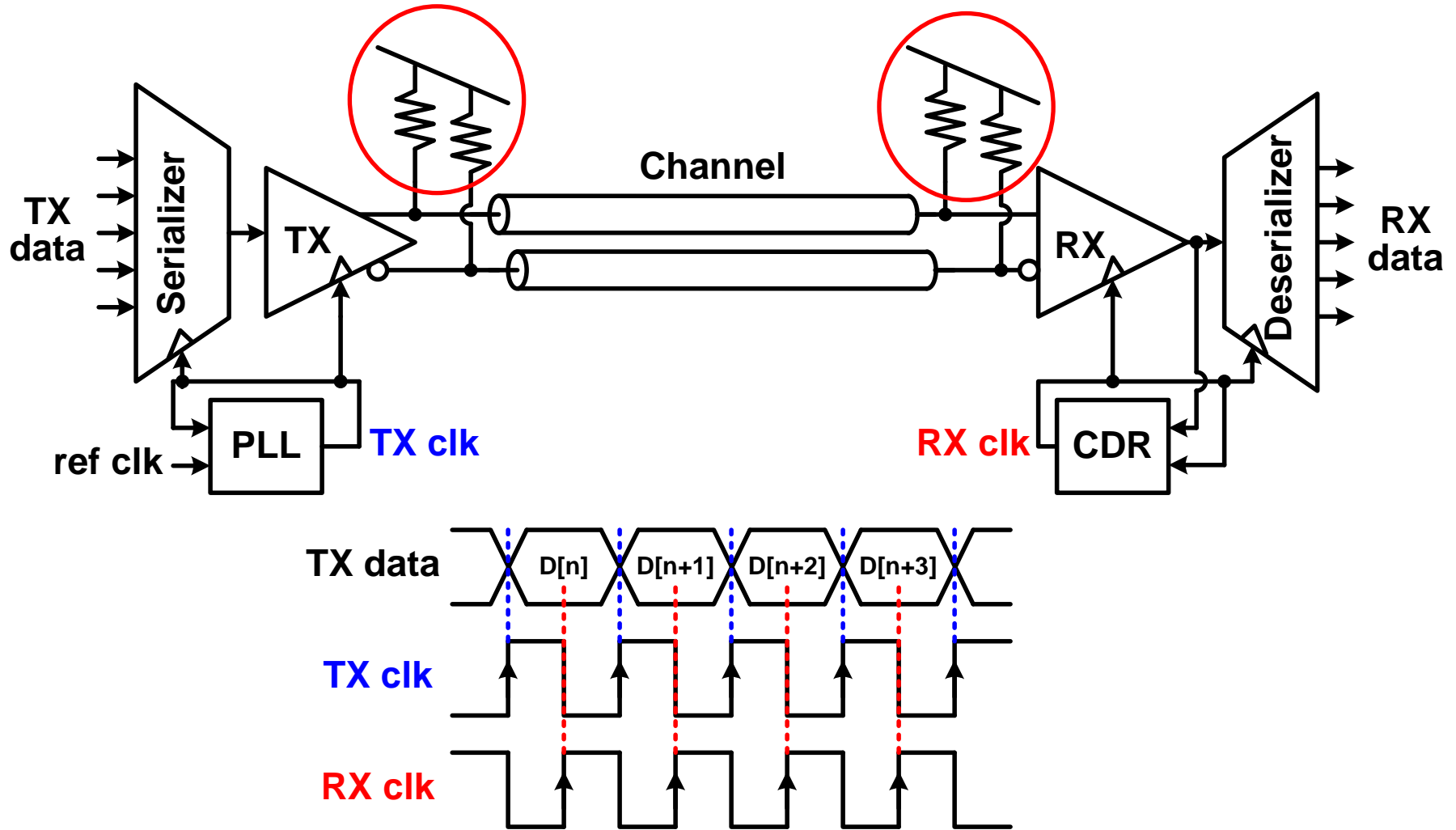


# Termination

---


- Off-chip vs on-chip
- Series vs parallel
- DC vs AC Coupling
- Termination circuits

# Off-Chip vs On-Chip Termination

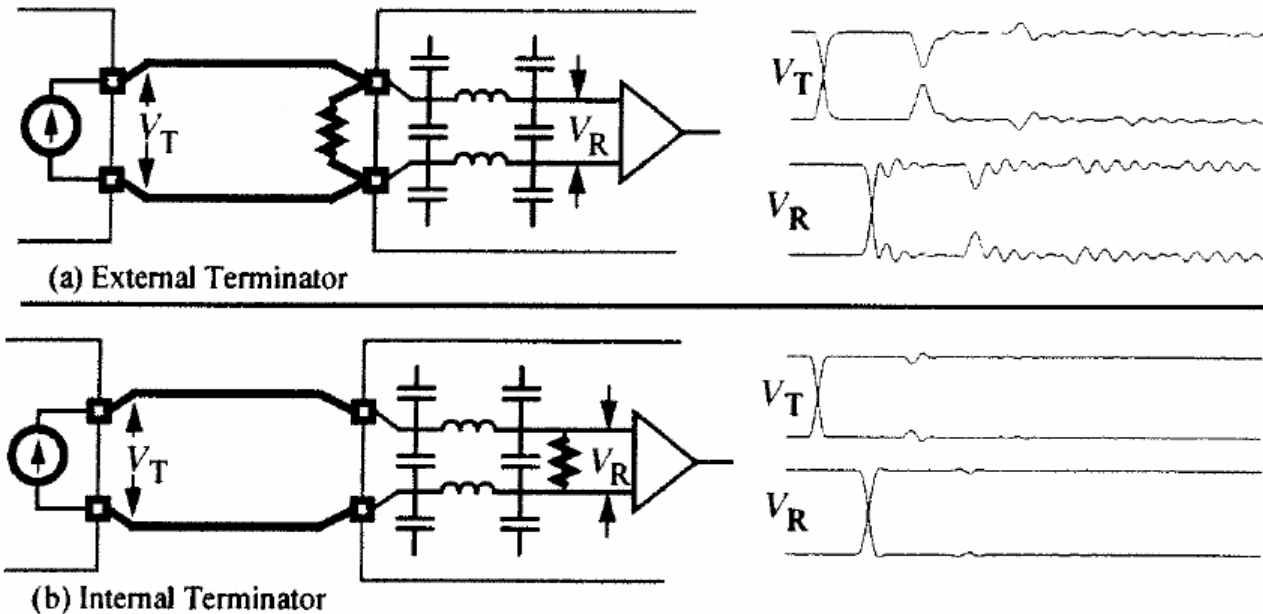

- Package parasitics act as an unterminated stub which sends reflections back onto the line
- On-chip termination makes package inductance part of transmission line



# Series vs Parallel Termination

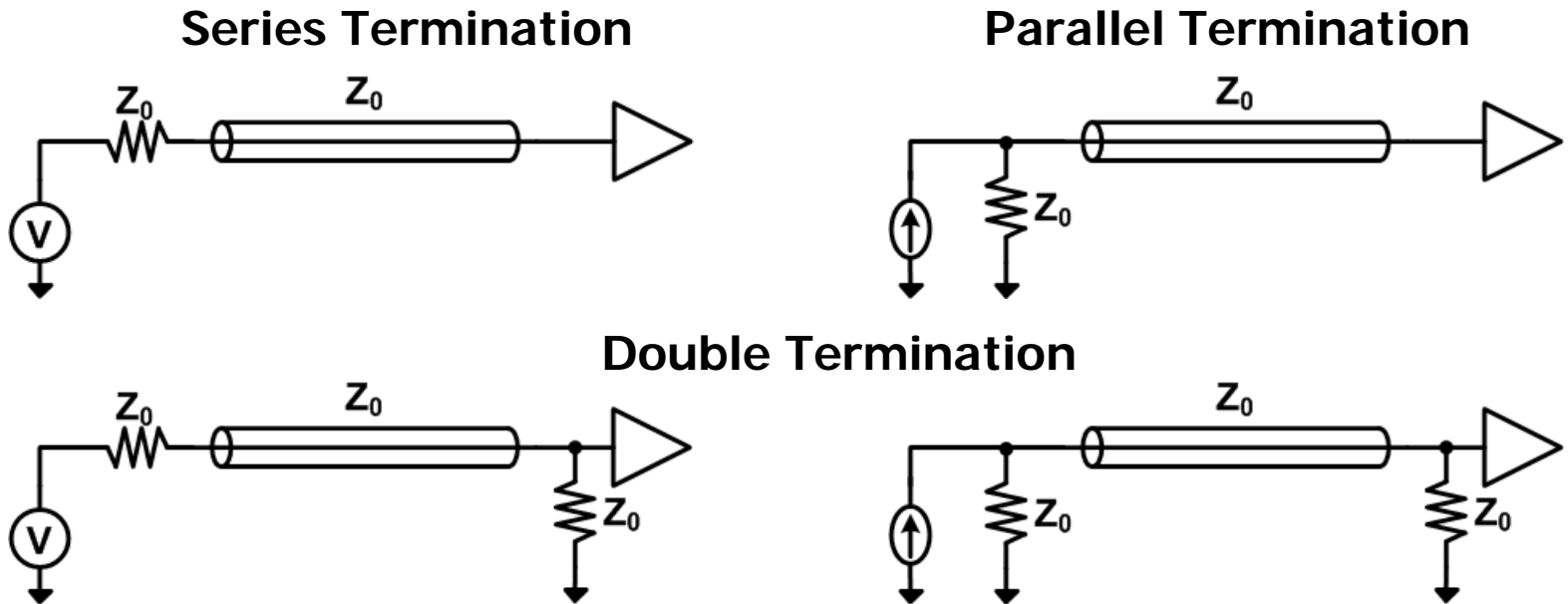

- Low impedance voltage-mode driver typically employs series termination
- High impedance current-mode driver typically employs parallel termination
- Double termination yields best signal quality
  - Done in majority of high performance serial links
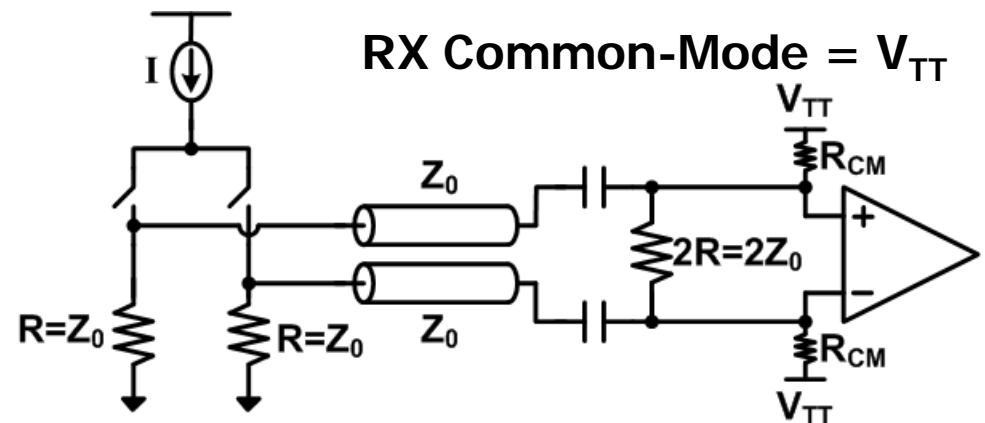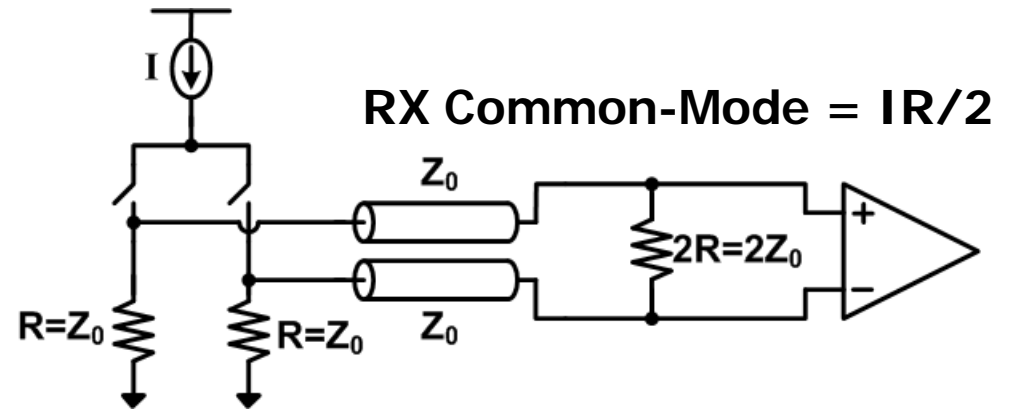
# AC vs DC Coupled Termination

- DC coupling allows for uncoded data
- RX common-mode set by transmitter signal level
- AC coupling allows for independent RX common-mode level
- Now channel has low frequency cut-off
  - Data must be coded





# Passive Termination


---

- Choice of integrated resistors involves trade-offs in manufacturing steps, sheet resistance, parasitic capacitance, linearity, and ESD tolerance
- Integrated passive termination resistors are typically realized with unalloyed poly, diffusion, or n-well resistors
- Poly resistors are typically used due to linearity and tighter tolerances, but they typically vary +/-30% over process and temperature


**Resistor Options (90nm CMOS)**

<b>Resistor</b>	<b>Poly</b>	<b>N-diffusion</b>	<b>N-well</b>
Sheet R ( $\Omega/\text{sq}$ )	90±10	300±50	450±200
VC1(V <sup>-1</sup> )	0	10 <sup>-3</sup>	8x10 <sup>-3</sup>
Parasitic Cap	2-3fF/um <sup>2</sup> (min L poly)	0.9fF/um <sup>2</sup> (area), 0.04fF/um (perimeter)	0.2fF/um <sup>2</sup> (area), 0.7fF/um (perimeter)


# Active Termination

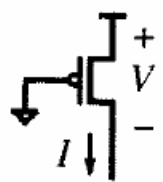


(a) Triode

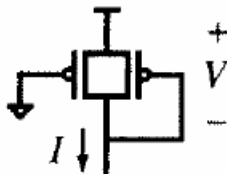

(b) Two-Element

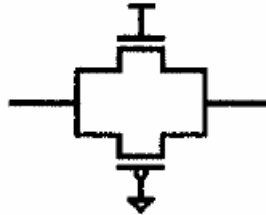


(c) Pass Gate

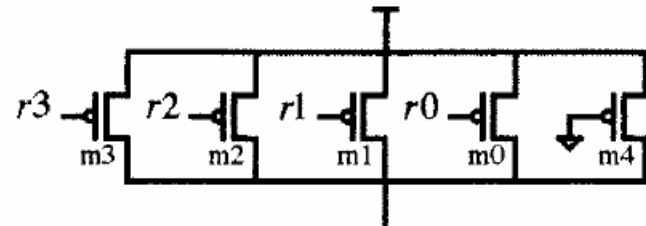

(d) Digital Trimming

- Transistors must be used for termination in CMOS processes which don't provide resistors
- Triode-biased FET works well for low-swing (<500mV)
  - Adding a diode connected FET increases linear range
- Pass-gate structure allows for differential termination


[Dally]

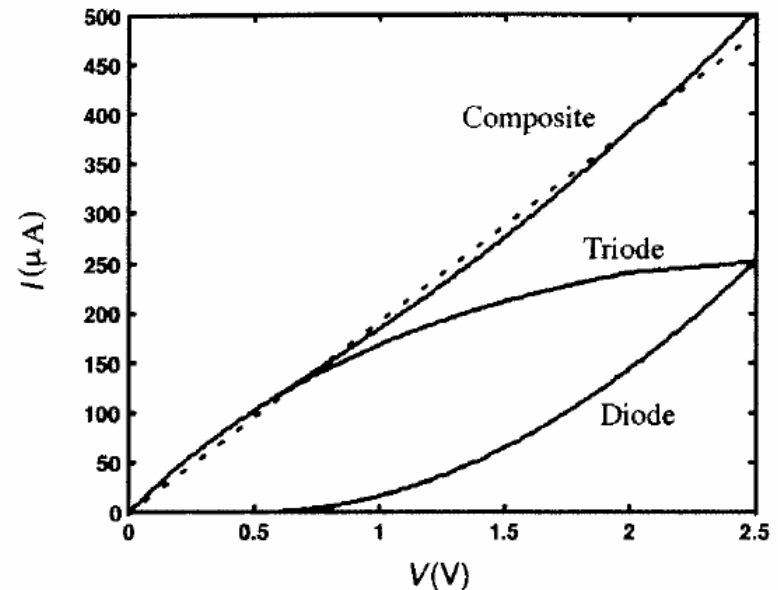
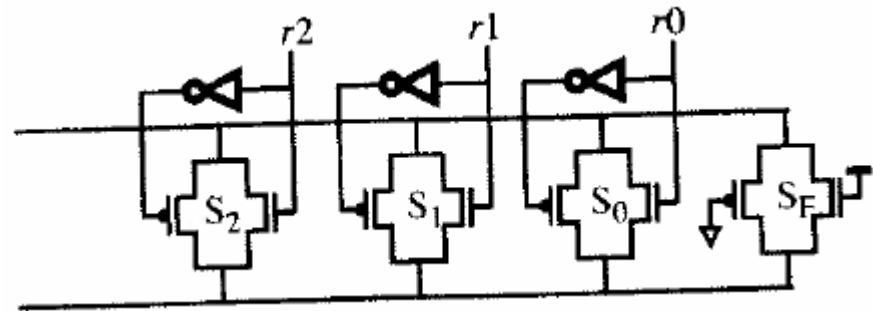
# Adjustable Termination

- FET resistance is a function of gate overdrive


$$R_{FET} = \frac{1}{\mu C_{ox} (W/L) (V_{GS} - V_t)}$$



[Dally]


- Large variance in FET threshold voltage requires adjustable termination structures
- Calibration can be done with an analog control voltage or through digital “trimming”
  - Analog control reduces  $V_{GS}$  and linear range
  - Digital control is generally preferred

# Termination Digital Control Loop

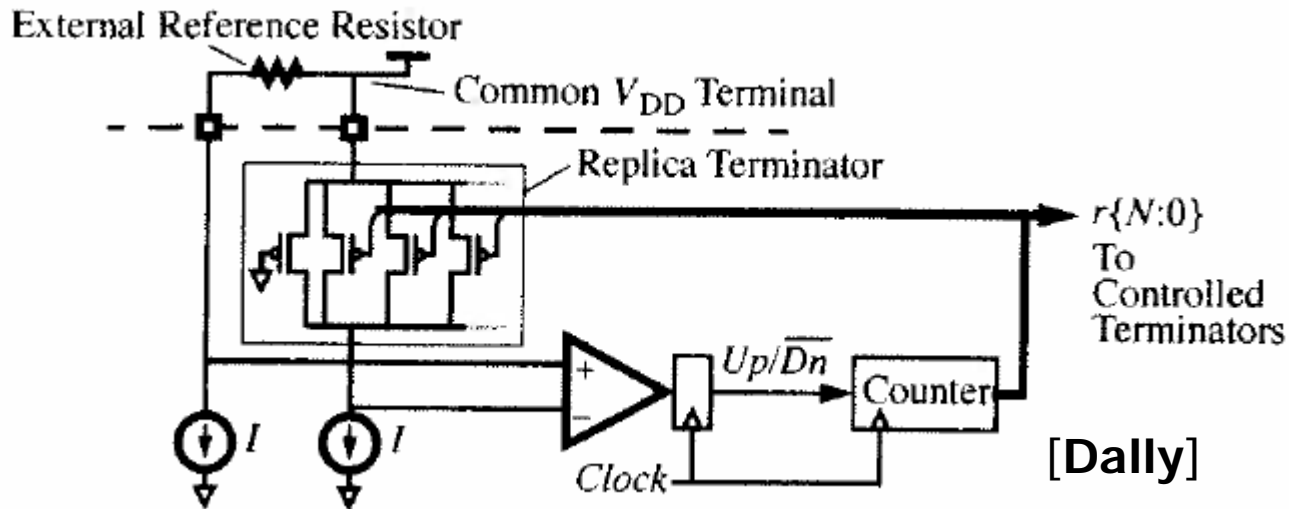

- Off-chip precision resistor is used as reference
- On-chip termination is varied until voltages are within an LSB
  - Dither filter typically used to avoid voltage noise
- Control loop may be shared among several links, but with increased nanometer CMOS variation per-channel calibration may be necessary

# High-Speed Electrical Link System

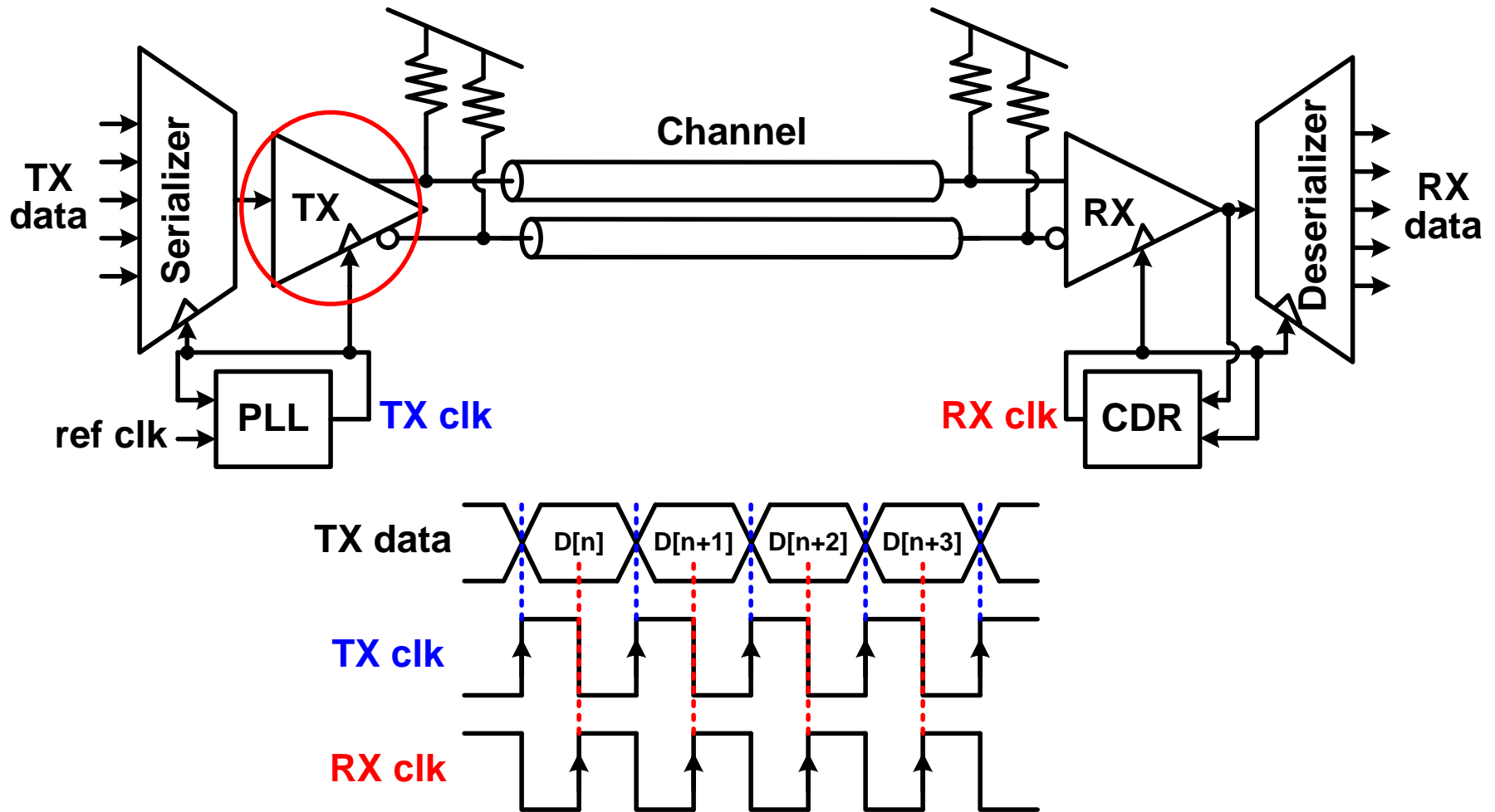


# Transmitter Circuits

---

- Single-ended vs differential signaling
- Current-mode drivers
- Voltage-mode drivers
- Slew-rate control

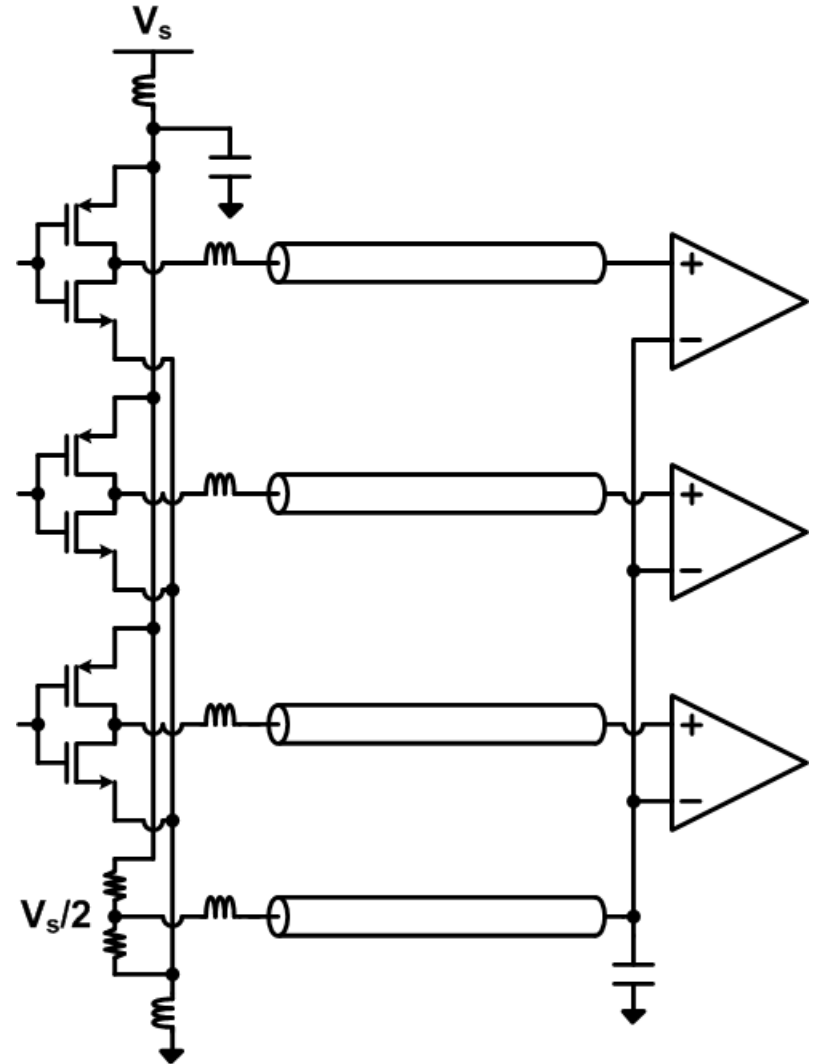
# Single-Ended Signaling

- Finite supply impedance causes significant Simultaneous Switching Output (SSO) noise (xtalk)
- Necessitates large amounts of decoupling capacitance for supplies and reference voltage
  - Decap limits I/O area more than circuitry



# Differential Signaling

---

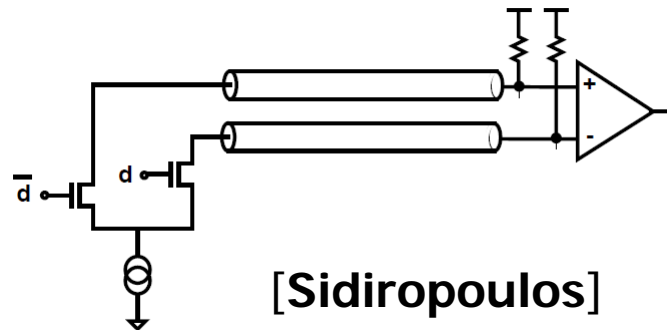

- A difference between voltage or current is sent between two lines
- Requires 2x signal lines relative to single-ended signaling, but less return pins
- Advantages
  - Signal is self-referenced
  - Can achieve twice the signal swing
  - Rejects common-mode noise
  - Return current is ideally only DC



# Next Time

---

- Transmitter Circuits
  - Current-mode drivers
  - Voltage-mode drivers
  - Slew-rate control
- Multiplexing Circuits
- Receiver Circuits