

ECEN720: High-Speed Links Circuits and Systems Spring 2019

Lecture 14: Clock Distribution Techniques




Sam Palermo
Analog & Mixed-Signal Center
Texas A&M University

Agenda

- Clock distribution in serial I/O systems
- Wire scaling
- Clock distribution techniques
 - Inverter Chain
 - CML Chain
 - Transmission Line
 - Inductive Load
 - Capacitively Driven Wires
- CML2CMOS converters

Clock Distribution in Serial I/O Systems

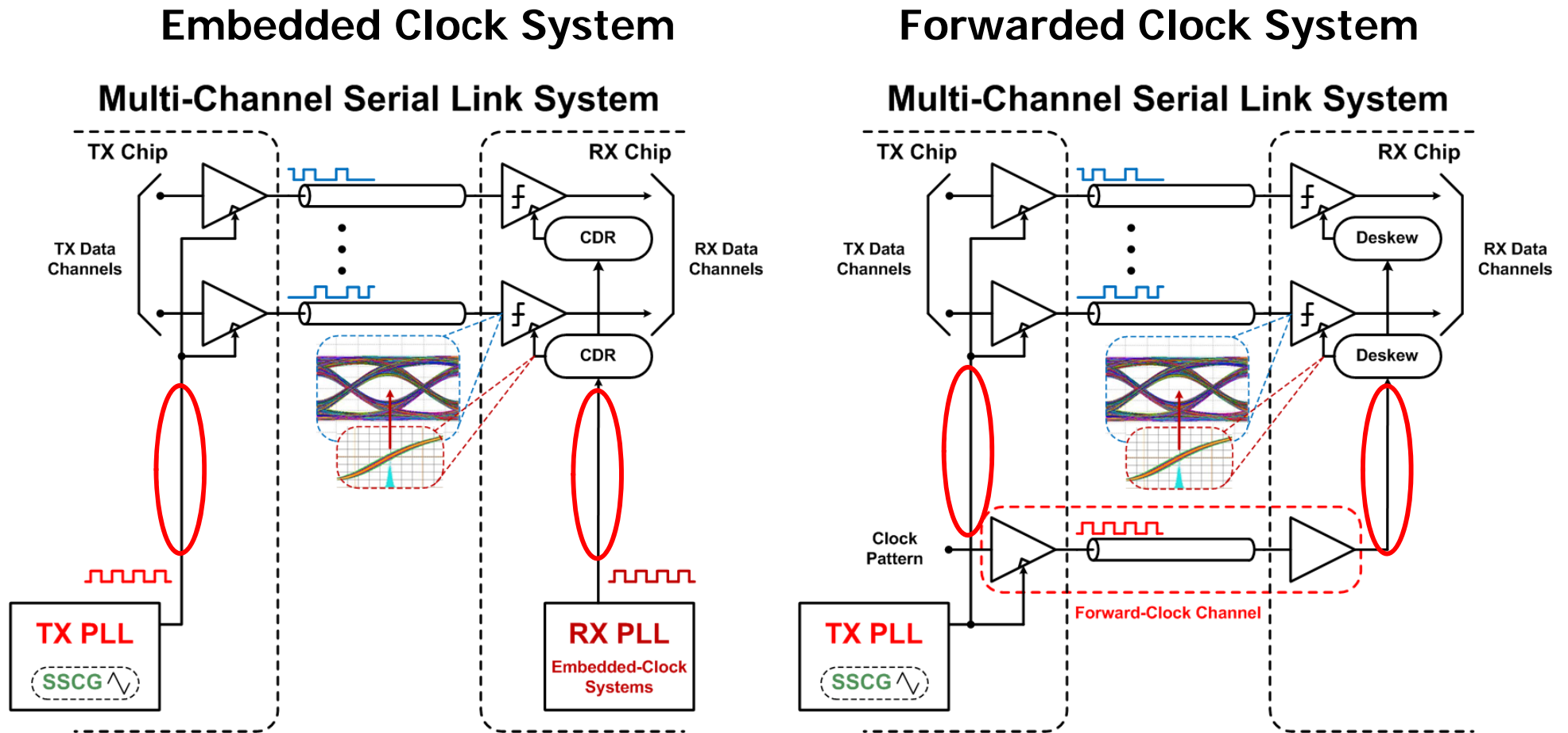

- On-die global clock distribution is necessary in multi-channel embedded and forwarded clock serial link systems

VLSI Interconnect (Wires)

Loose pitch + thick metal
on upper layers


- High speed global wires
- Low resistance power grid

Tight pitch on lower layers

- Maximum density for
local interconnects

[Bohr ISSCC 2009]

45nm CMOS

 

Pitch (nm)

M8 810

M7 560

M6 360

M5 280


M4 240

M3 160

M2 160

M1 160





Wire Scaling

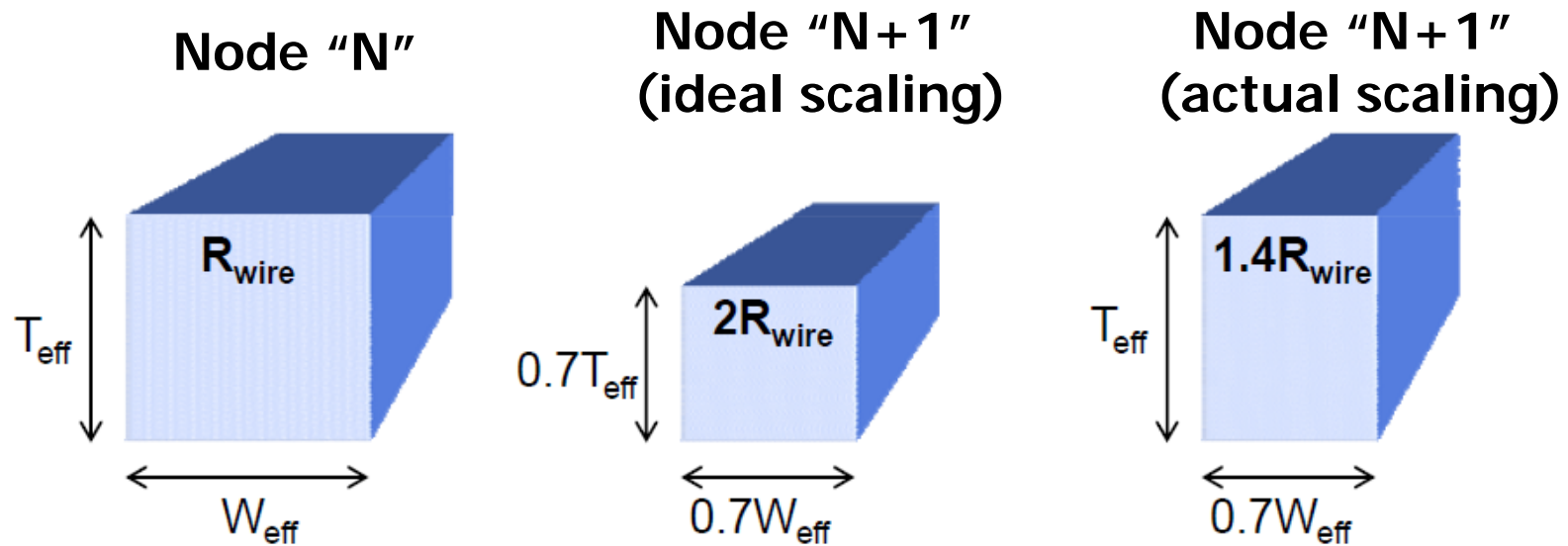

[Ho]

- Ideally, we scale everything by 0.7x when we move to a more advanced technology node for 2x density
- Results in 2x wire resistance, which dramatically increases wire RC delay
 - To compensate resistance wires get taller
- Cap grows at a smaller pace with scaling
 - Taller wires increase sidewall cap
 - Improved (low-k) dielectrics help reduce cap


Wire Scaling - Delay

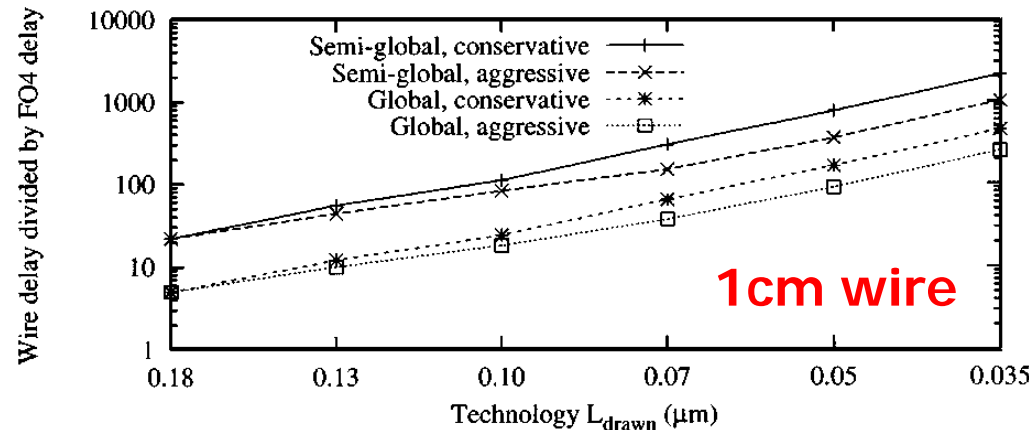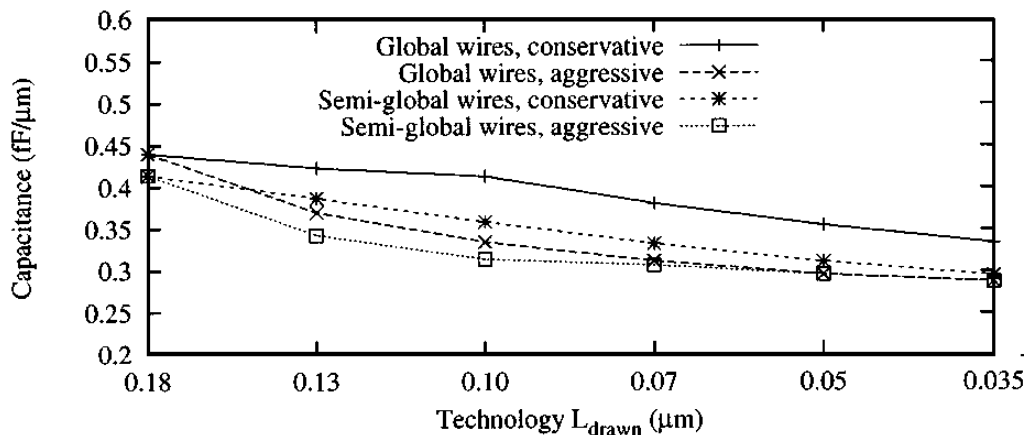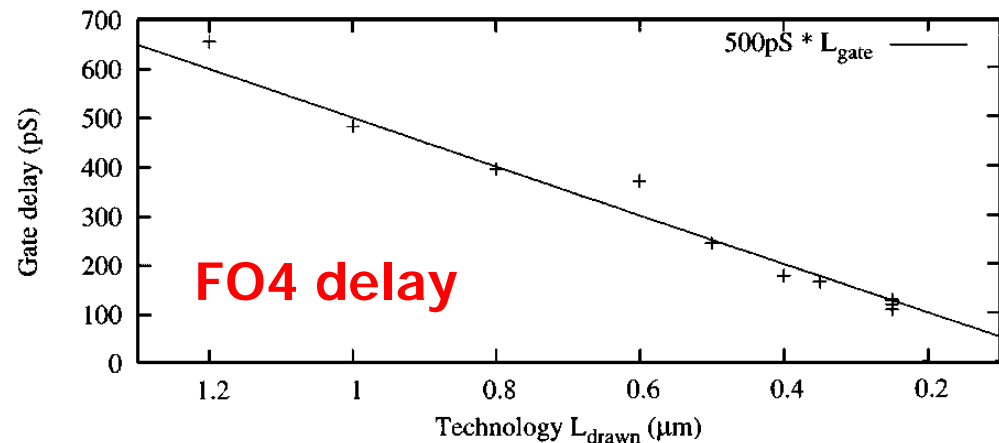 

[Ho Proc. IEEE 2001]

- Global on-chip wire RC delay becomes many (100+) gate delays (if driven w/ one lumped driver)

Limited Wire Bandwidth

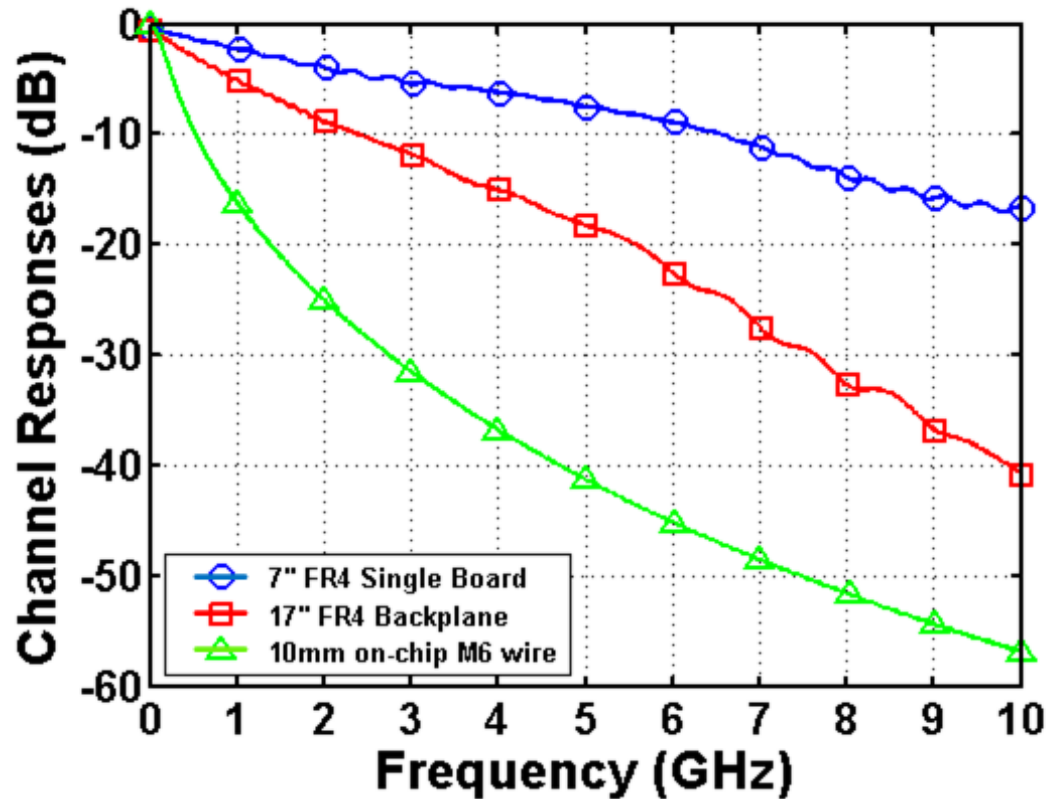


- Global on-chip wire bandwidth is much worse than chip-to-chip channels
- RC-dominated on-chip wires vs (R)LC-dominated off-chip wires

Clock Distribution Techniques

- Clock distribution techniques are typically compared in regards to jitter, delay, and power
- Techniques
 - Inverter Chain
 - CML Chain
 - Transmission Line
 - Inductive Load
 - Capacitively Driven Wires


Inverter Chain Distribution

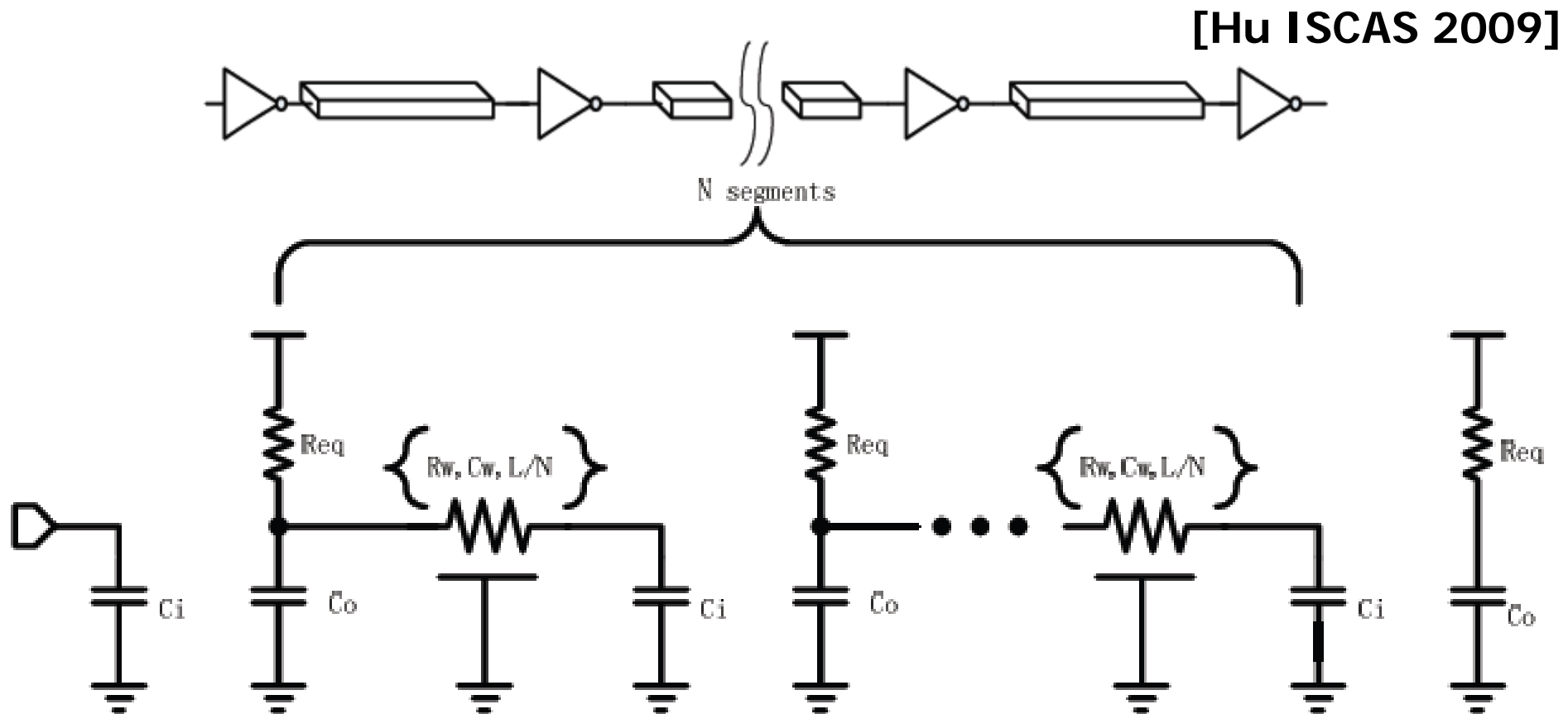

- Instead of driving the long low-bandwidth wire with one huge inverter, break wire up into N segments driven by N inverters

Elmore Delay of Inverter Chain Distribution

[Hu ISCAS 2009]

 

N = segment number

C_i, C_o, R_{eq} = inverter input cap, output cap, equivalent resistance

R_w, C_w = wire unit resistance and capacitance

L = wire length

C_{iu}, C_{ou}, R_{equ} = unit inverter input cap, output cap, equivalent resistance

m = multiple factor of unit inverter

$$t_p = N \left[0.69 R_{eq} c_o + \left(0.69 R_{eq} + 0.38 \frac{R_w L}{N} \right) \frac{C_w L}{N} + 0.69 \left(R_{eq} + \frac{R_w L}{N} \right) c_i \right]$$

$$= N \left[0.69 \frac{R_{equ}}{m} m c_{ou} + \left(0.69 \frac{R_{equ}}{m} + 0.38 \frac{R_w L}{N} \right) \frac{C_w L}{N} + 0.69 \left(\frac{R_{equ}}{m} + \frac{R_w L}{N} \right) m c_{iu} \right]$$

$$= 0.69 N R_{equ} (c_{ou} + c_{iu}) + 0.38 \frac{R_w C_w L^2}{N} + 0.69 \frac{R_{equ} C_w L}{m} + 0.69 m R_w L c_{iu}$$

N FO1 inverter τ_s


Inherent wire delay
divided by N
segments

RC of one inverter
driving total wire cap

RC of wire driving
one inverter

Elmore Delay of Inverter Chain Distribution

[Hu ISCAS 2009]

 

N = segment number

C_i, C_o, R_{eq} = inverter input cap, output cap, equivalent resistance

R_w, C_w = wire unit resistance and capacitance

L = wire length

C_{iu}, C_{ou}, R_{equ} = unit inverter input cap, output cap, equivalent resistance

m = multiple factor of unit inverter

$$t_p = 0.69NR_{equ}(c_{ou} + c_{iu}) + 0.38\frac{R_w C_w L^2}{N} + 0.69\frac{R_{equ} C_w L}{m} + 0.69mR_w Lc_{iu}$$



For Minimum Propagation Delay

$$N = 0.742L\sqrt{\frac{R_w C_w}{R_{equ}(c_{ou} + c_{iu})}} \quad \text{and} \quad m = \sqrt{\frac{R_{equ} C_w}{R_w c_{iu}}}$$

Inverter Chain Distribution


Delay, Jitter, and Power Trade-offs

[Hu ISCAS 2009]

 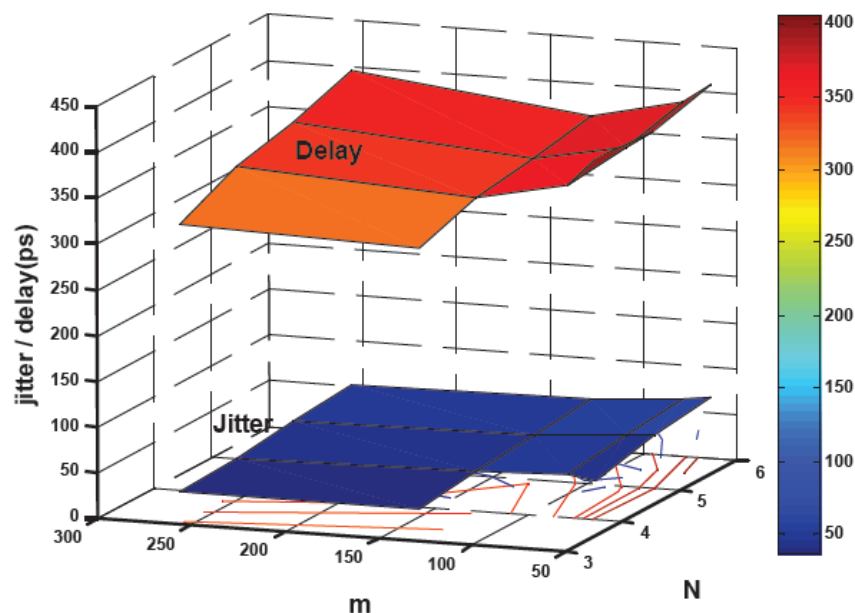


- Delay and jitter are correlated, but don't necessarily share same minimum
- For 5mm wire in 90nm CMOS
 - Minimum jitter (36ps): $N=3$ and $m=256$
 - Minimum delay (321ps): $N=3$ and $m=128$
 - Minimum power: $N=4$ and $m=64$

CML Chain Distribution

 

[Hu ISCAS 2009]


 


- Relative to inverter-based buffers, low-swing CML buffers offer increased bandwidth and PSRR
- Same model used to analyze CML distribution

CML Chain Distribution

Delay, Jitter, and Power Trade-offs


[Hu ISCAS 2009]

 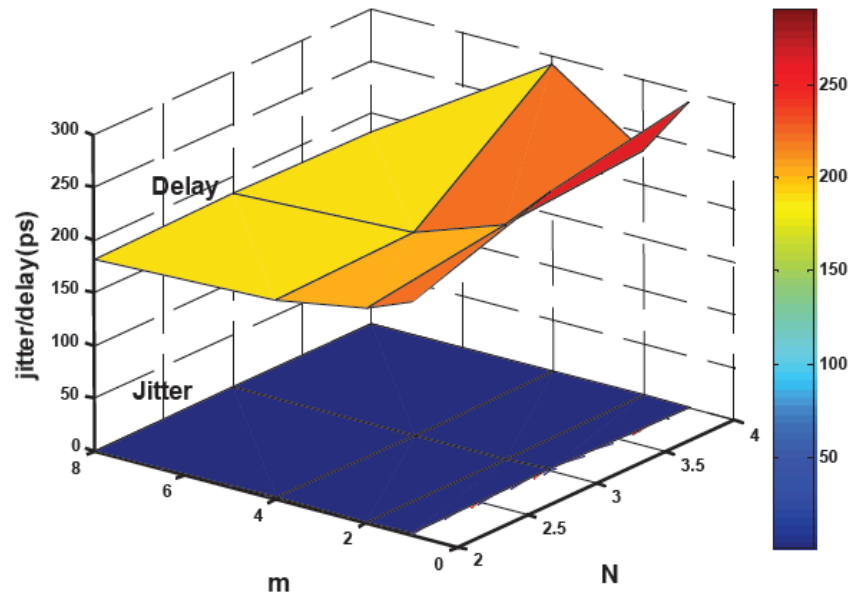

- Analysis with $400\text{mV}_{\text{ppd}}$ swing ($R=200\Omega$, $I_{\text{tail}}=1\text{mA}$)
- For 5mm wire in 90nm CMOS
 - Minimum jitter (0.5ps): $N=2$ and $m=8$
 - Minimum delay (182ps): $N=4$ and $m=8$
 - Minimum power: $N=2$ and $m=1$
- Much better jitter performance than inverter-based distribution
 - However, jitter amplification is not considered in this work
 - CML buffers may be more sensitive to input jitter than inverter-based

Transmission Line Distribution



[Hu ISCAS 2009]

 

- On-die transmission lines can be realized with wider than minimum-width wires
- DC resistance is small relative to characteristic impedance, i.e. distributed wire inductance has strong impact on wire delay
- Allows for “speed-of-light” propagation velocity
- Passive transmission line doesn't introduce any jitter

On-Die Transmission Lines

[Hu ISCAS 2009]

  

- If signaling is strictly on-chip, have more freedom to choose differential impedance
- Larger impedance will allow for lower power, but there are limitations
 - Parasitic capacitance
 - DC resistance
- Because of this, many times the on-die transmission lines will display differential impedance close to the typical off-chip 100Ω value



Clock Swing Along Transmission Line

5mm Transmission Line

$W=6\mu\text{m}$, $d=2.5\mu\text{m}$, $W_{\text{gnd}}=4\mu\text{m}$, $s=4\mu\text{m}$

$Z_0=120\Omega$ and $RDC = 42\Omega$

[Hu ISCAS 2009]

  

- DC-loss of transmission lines causes reduction in the clock swing as it travels down the line
- For 5mm line, delay=43ps and jitter=0.18ps

Inductive Load Distribution

[Hu ISCAS 2009]




- Inductively-loaded wire can boost wire impedance by resonating with the wire capacitance at the clock frequency
 - Reduces power
 - Provides jitter filtering
- Cost is high inductor area, particularly at lower clock frequencies


Inductive Load Distribution

[Song]

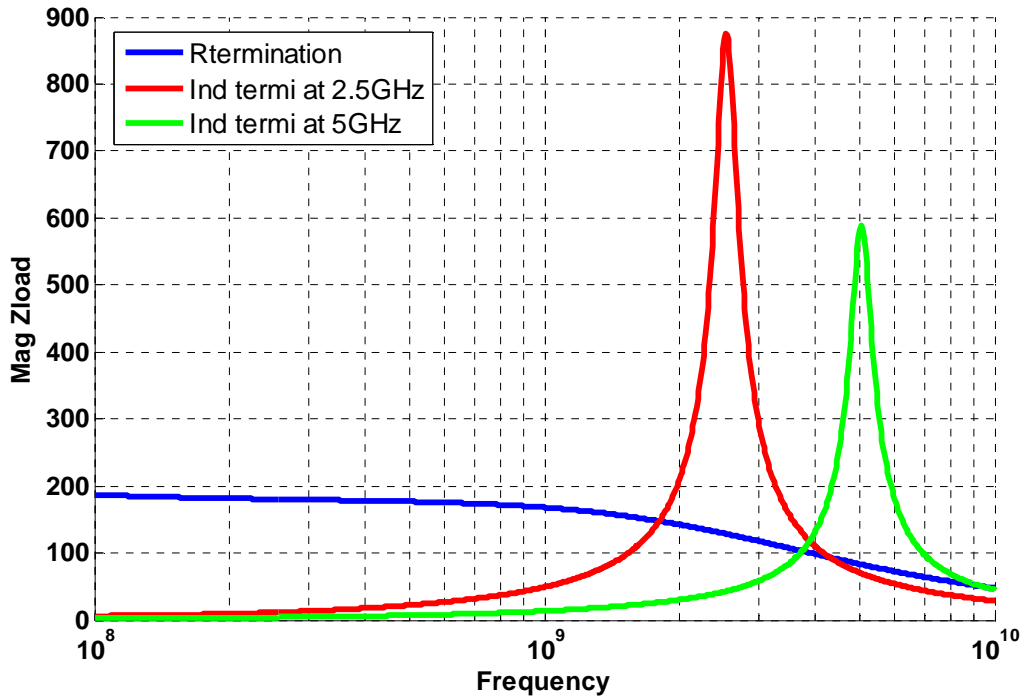2.5GHz and 5GHz Resonant Clock Distribution



5GHz Clock Distribution Eye Diagram

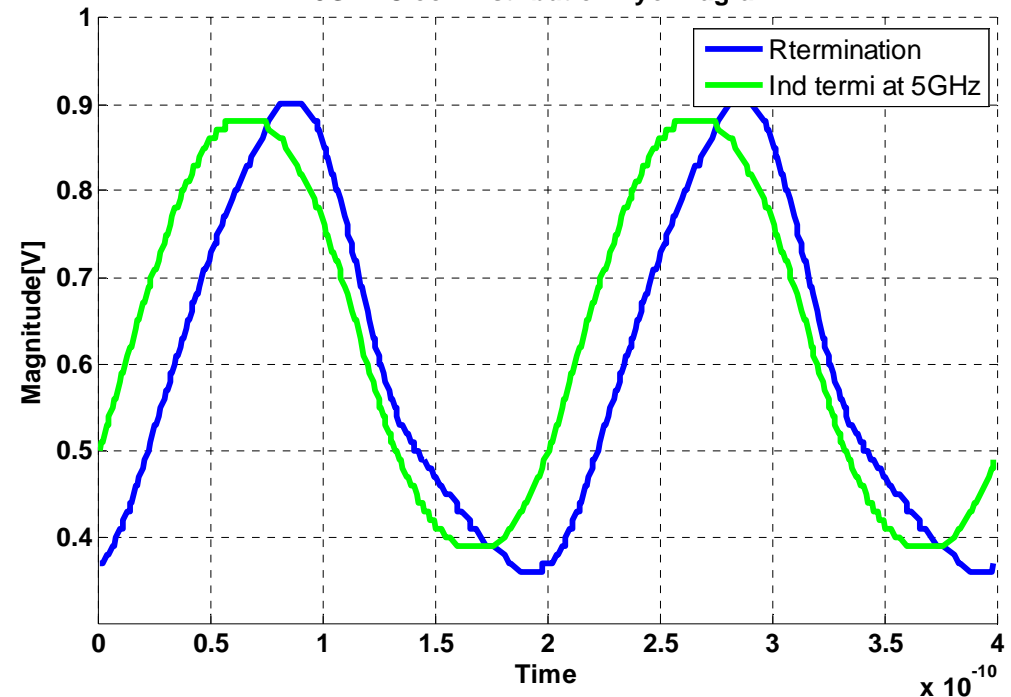


5GHz	Inductor Load	R Load
Vswing	500mV	538mV
Power	1.2mW	7.2mW

- For similar clock swing, inductive termination can offer significant power savings


Capacitively Driven Wires Distribution

[Hu ISCAS 2009]

 


- Adding a capacitor in series to the pseudo-differential inverter-based drivers significantly reduces driver loading

Capacitively Driven Wires Model

 

[Hu ISCAS 2009]

[Ho JSSC 2008]

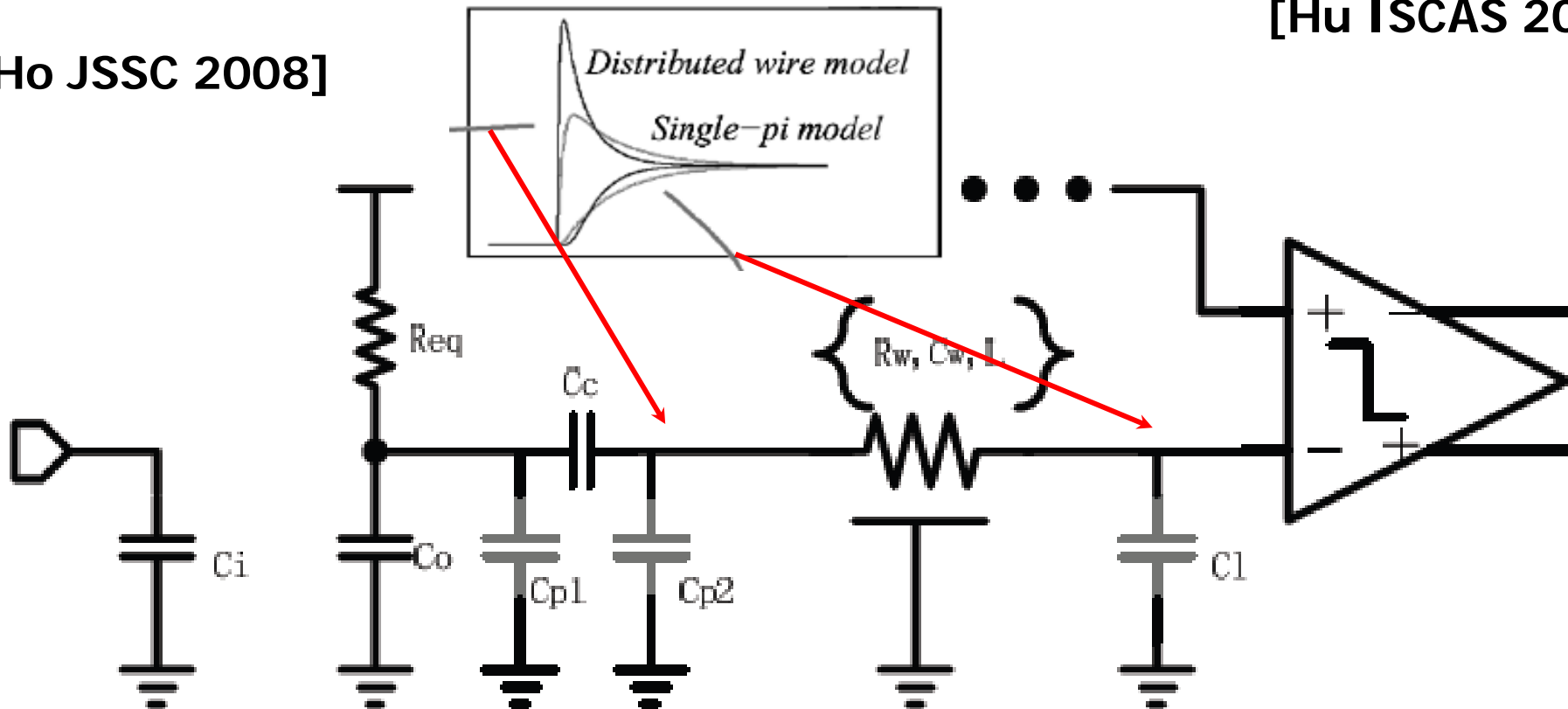


$$t_p = 0.69R_{eq}(c_o + c_{p1} + c_c) + 0.19R_w C_w L^2$$

Capacitively Driven Wires Distribution

$$t_p = 0.69R_{eq}(c_o + c_{p1} + c_c) + 0.19R_w C_w L^2$$

[Hu ISCAS 2009]

 

- Minimum series cap reduces delay and power, but swing also
- If cap is too small, increased jitter is observed


Clock Distribution Performance Comparison

Technology	1.2V 90nm CMOS		
Methods (with optimal tradeoff)	Performance		
	<i>jitter(ps)</i>	<i>delay(ps)</i>	<i>power(mW)</i>
Inverter chain (N=3, m=128)	36	321	11.5
CML chain (N=2, m=1)	1	221	2
Transmission line	0.18	43	4
Inductive load (L=6nH, Q=2)	0.42	55	4
CDW (Cc=50f)	1.98	116	0.62

[Hu ISCAS 2009]

- Transmission-line distribution offers best jitter and delay performance
- CDW offers minimum jitter-power and delay-power product
- Note, everything but inverter-chain distribution is low-swing
- If CML2CMOS converter is not designed well, that can kill your nice distribution network performance


CML2CMOS Converter (1)

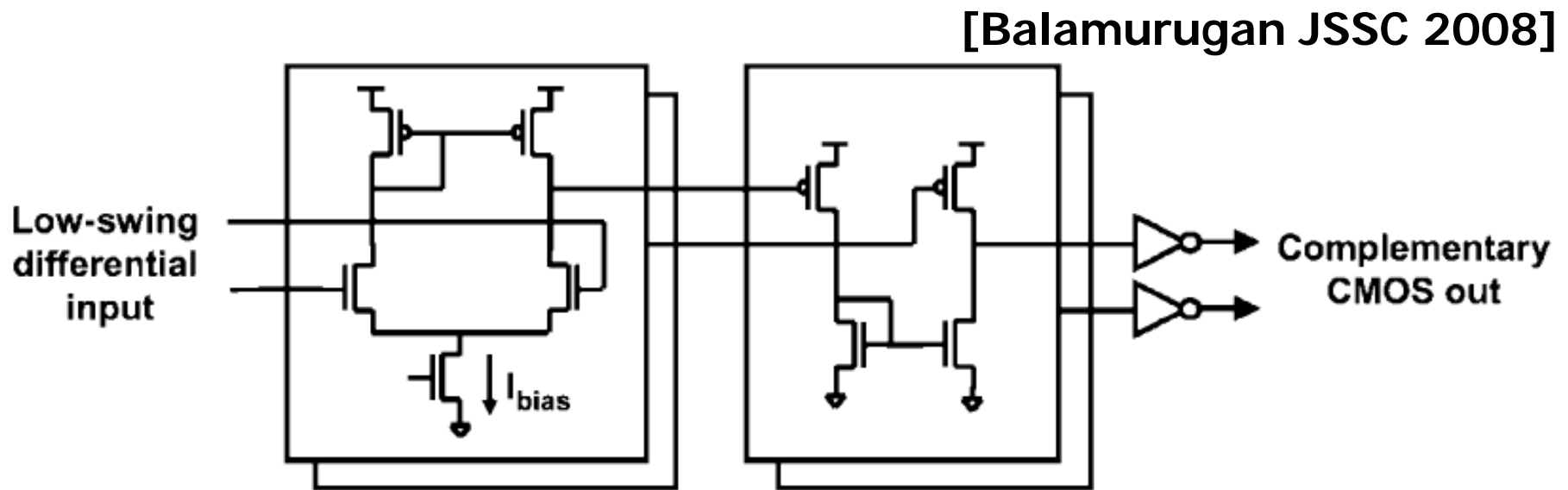

- Differential input stage followed by high-swing output stage
- Can be sensitive to power-supply noise and reduce jitter benefits of low-swing distribution techniques
- Often require some type of duty-cycle control

CML2CMOS Converter (2)

[Kossel JSSC 2008]

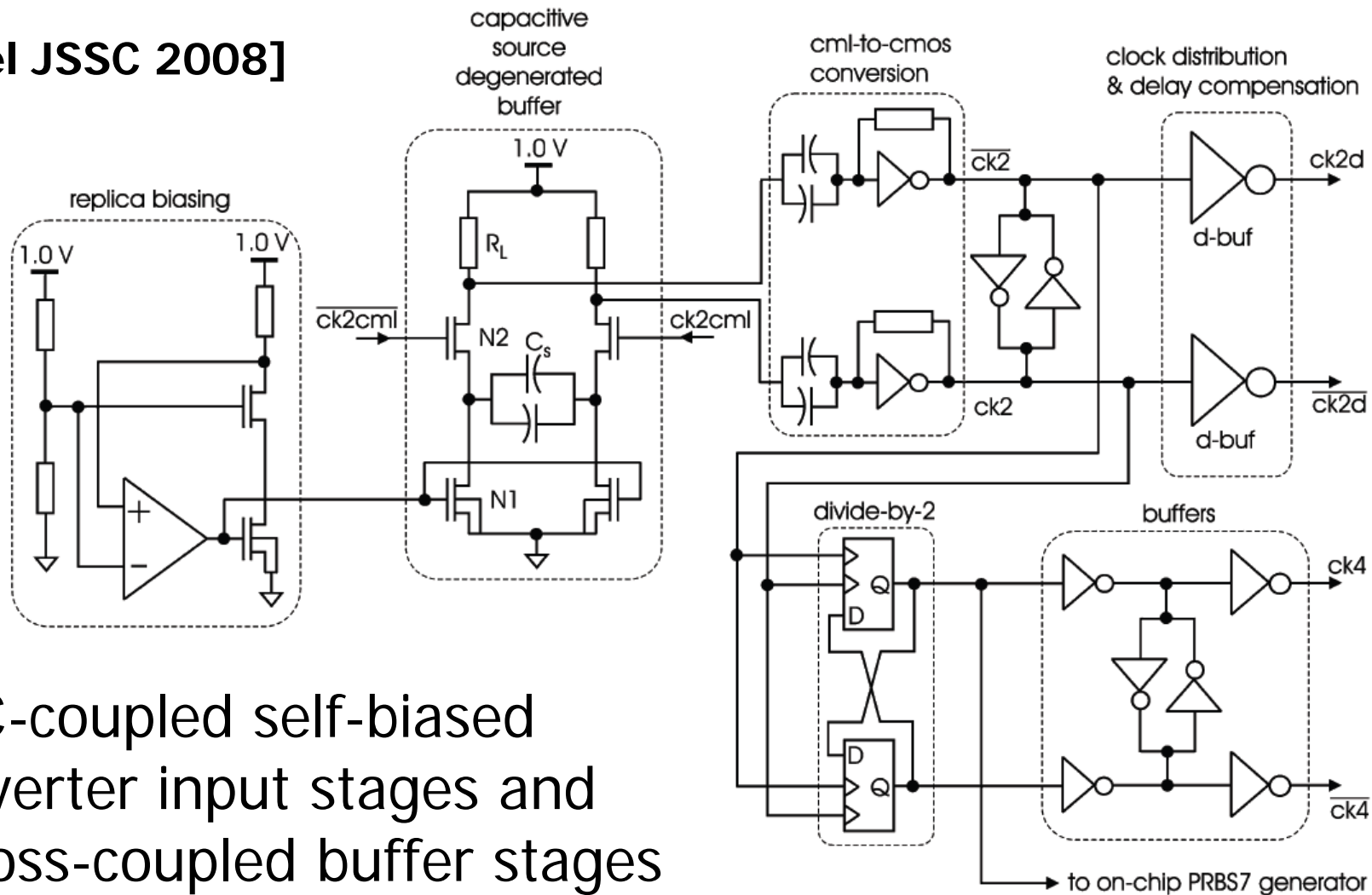

- AC-coupled self-biased inverter input stages and cross-coupled buffer stages can help improve duty cycle performance