

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

Lecture 28: VCOs



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

Announcements


- Project Preliminary Report #2 now due Monday April 26 in class
- Exam 2 is April 30
- Project feedback meetings
 - Today 3:30-5
 - Wednesday 10:30-12

Agenda


- VCOs

Charge-Pump PLL Circuits

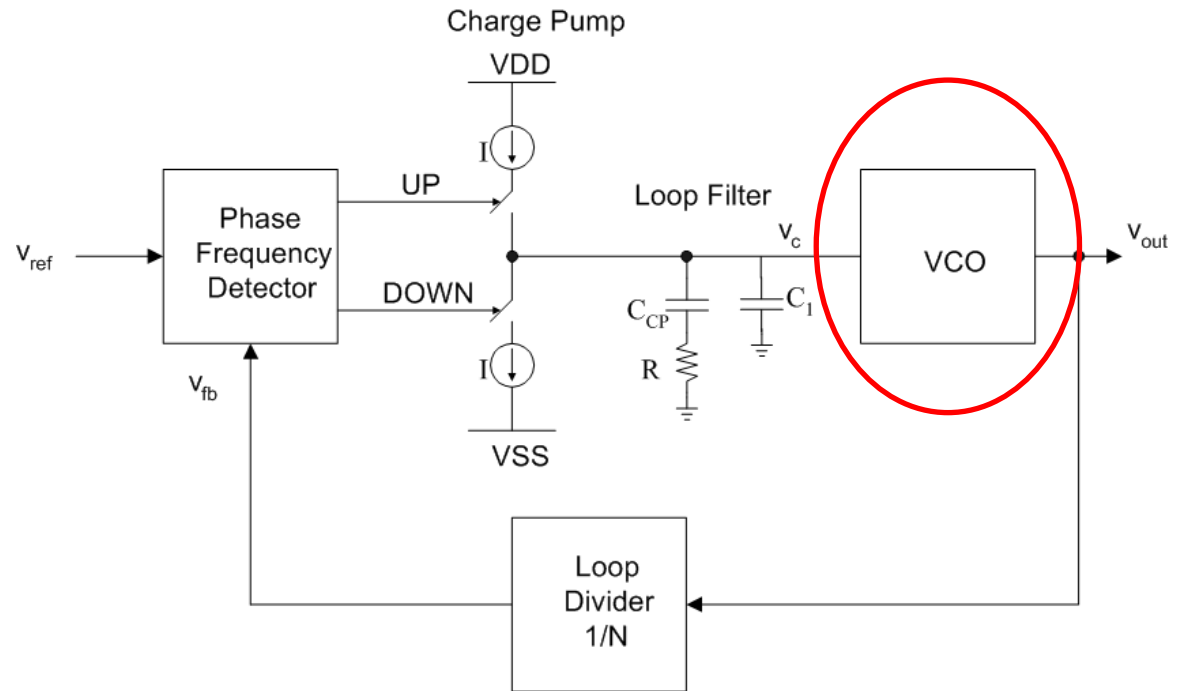- Phase Detector
- Charge-Pump
- Loop Filter
- VCO
- Divider



Voltage-Controlled Oscillator

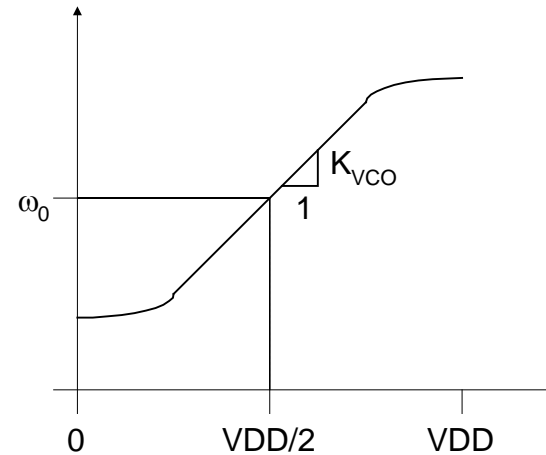


$$\omega_{out}(t) = \omega_0 + \Delta\omega_{out}(t) = \omega_0 + K_{VCO}v_c(t)$$

- Time-domain phase relationship

$$\theta_{out}(t) = \int \Delta\omega_{out}(t)dt = K_{VCO} \int v_c(t)dt$$


Laplace Domain Model

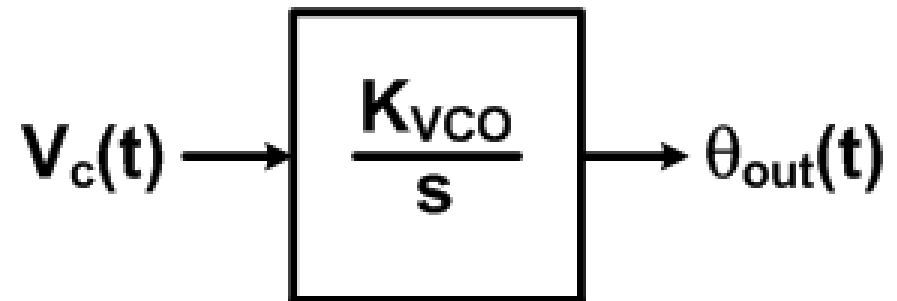

Voltage-Controlled Oscillators (VCO)


- Ring Oscillator

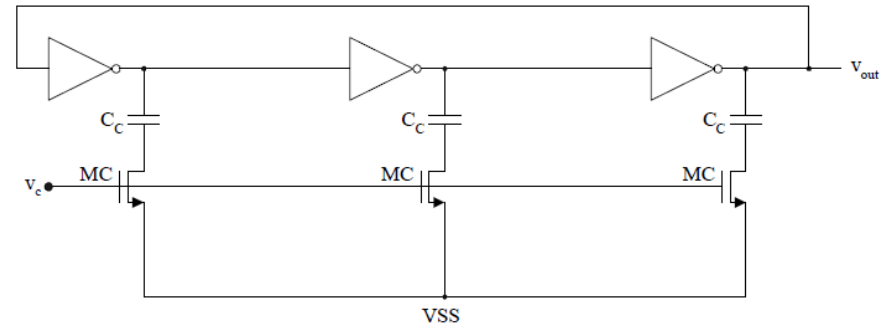- Easy to integrate
- Wide tuning range (5x)
- Higher phase noise




- LC Oscillator

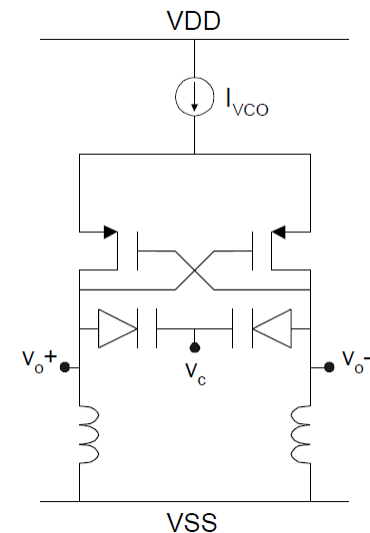- Large area
- Narrow tuning range (20-30%)
- Lower phase noise




Barkhausen's Oscillation Criteria

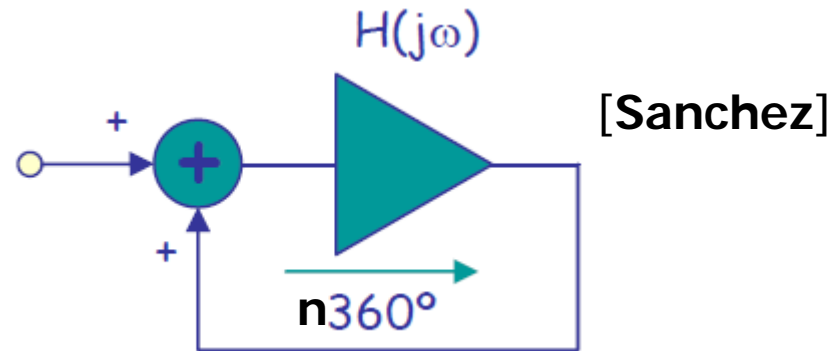

Closed-loop transfer function: $\frac{H(j\omega)}{1-H(j\omega)}$

- Sustained oscillation occurs if $H(j\omega)=1$
- 2 conditions:
 - Gain = 1 at oscillation frequency ω_0
 - Total phase shift around loop is $n360^\circ$ at oscillation frequency ω_0

Ring Oscillator Example

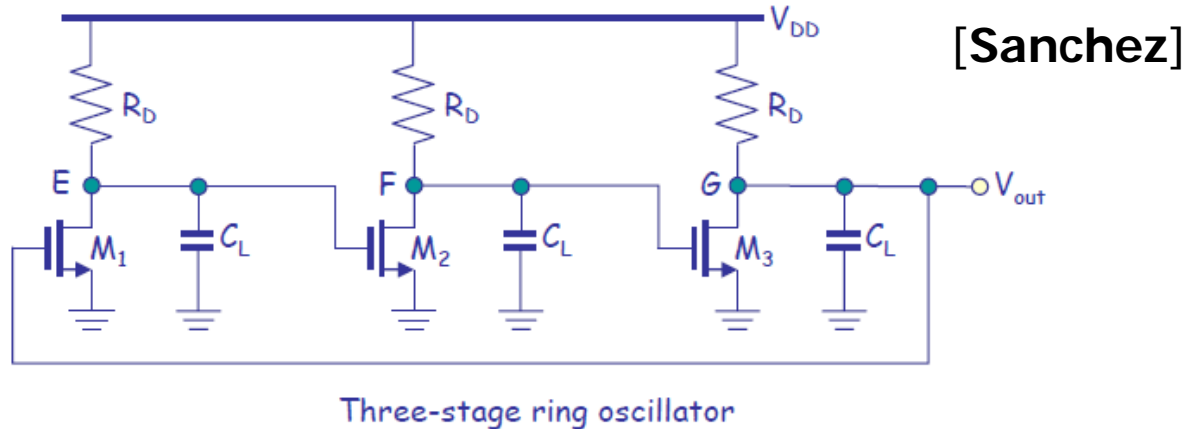

$$H(s) = -\frac{A_0^3}{\left(1 + \frac{s}{\omega_0}\right)^3}$$

$$\omega_{osc} = \sqrt{3}\omega_0$$


$$\tan^{-1} \frac{\omega_{osc}}{\omega_0} = 60^\circ$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-A_0^3}{1 + \frac{A_0^3}{\left(1 + s/\omega_0\right)^3}} = \frac{-A_0^3}{\left(1 + s/\omega_0\right)^3 + A_0^3}$$

$$\frac{A_0^3}{\left[\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}\right]^3} = 1$$

$$A_0 = 2$$

Ring Oscillator Example

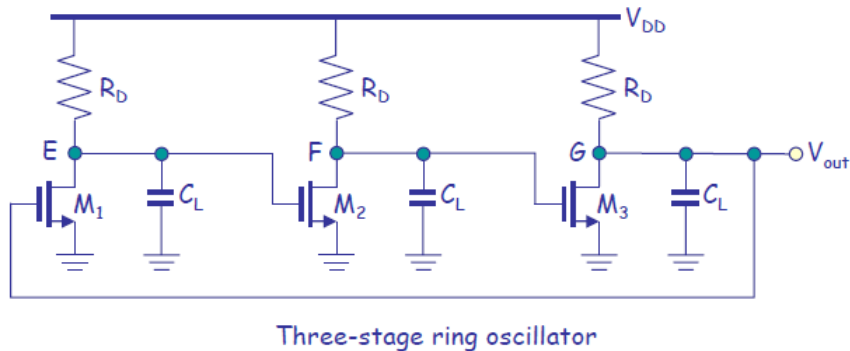

- 4-stage oscillator
 - $A_0 = \sqrt{2}$
 - Phase shift = 45°

$$H(s) = -\frac{A_0^3}{\left(1 + \frac{s}{\omega_0}\right)^3}$$

$$\omega_{osc} = \sqrt{3}\omega_0$$

$$\tan^{-1} \frac{\omega_{osc}}{\omega_0} = 60^\circ$$

- Easier to make a larger-stage oscillator oscillate, as it requires less gain and phase shift per stage


$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-A_0^3}{1 + \frac{A_0^3}{\left(1 + s/\omega_0\right)^3}} = \frac{-A_0^3}{\left(1 + s/\omega_0\right)^3 + A_0^3}$$

$$\frac{A_0^3}{\left[\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}\right]^3} = 1$$

$$A_0 = 2$$


[Sanchez]

LC Oscillator Example

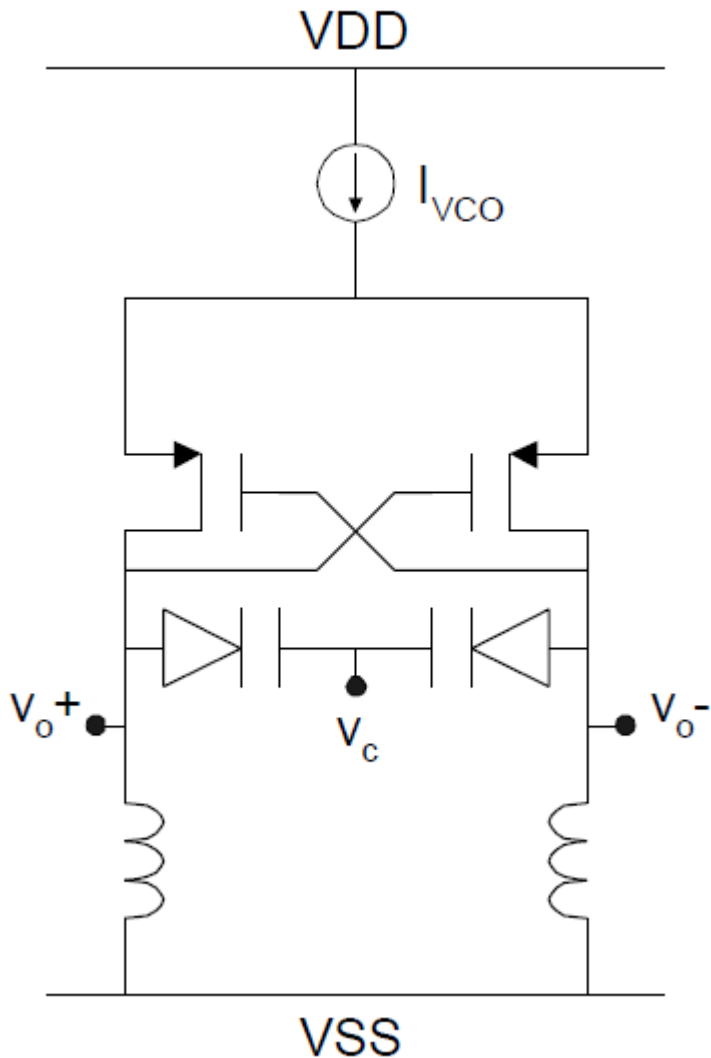


LC tank impedance

$$|Z_{eq}(s = j\omega)|^2 = \frac{R_S^2 + L_1^2 \omega^2}{(1 - L_1 C_1 \omega^2)^2 + R_S^2 C_1^2 \omega^2}$$

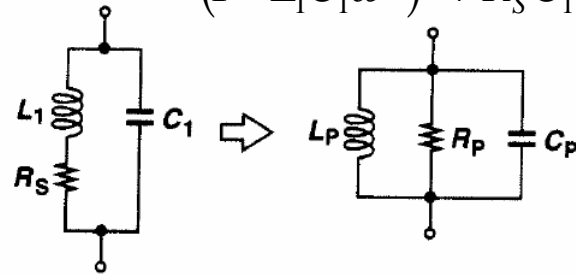


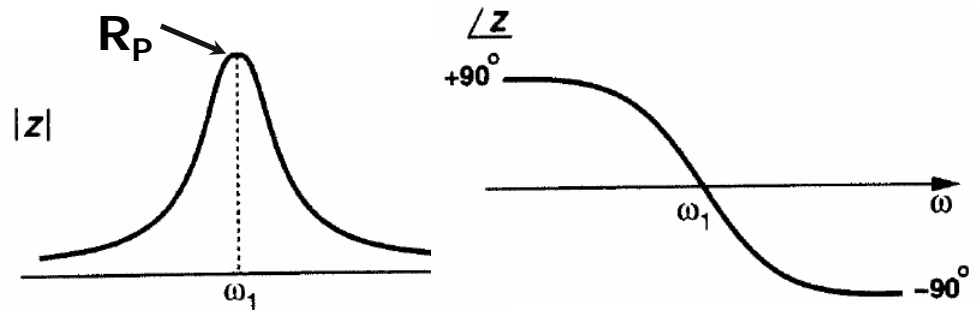
$$L_P = L_1 \left(1 + \frac{R_S^2}{L_1^2 \omega^2} \right), \quad C_P = C_1, \quad R_P \approx \frac{L_1^2 \omega^2}{R_S}$$



$$\omega_1 = \frac{1}{\sqrt{L_P C_P}}$$

[Razavi]

LC Oscillator Example

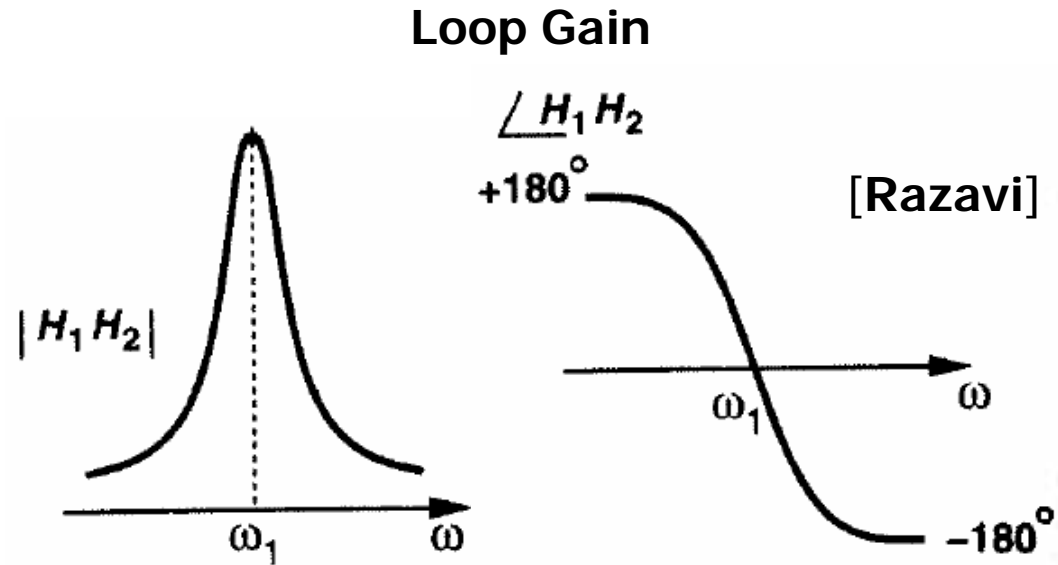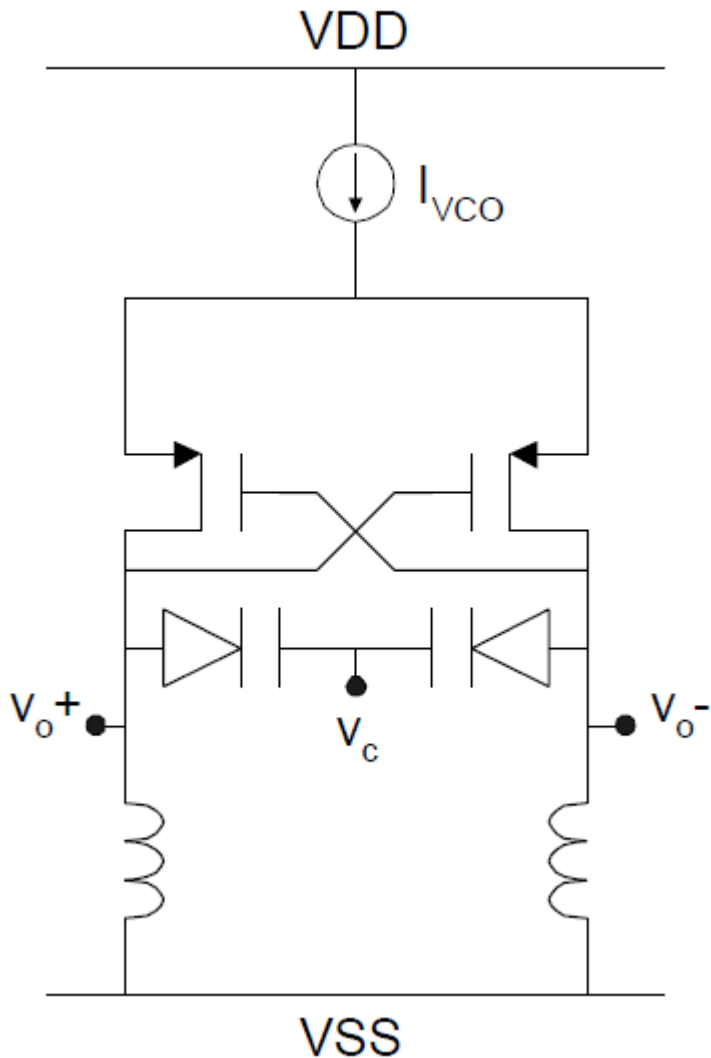


- Phase condition satisfied at

$$\omega_1 = \frac{1}{\sqrt{L_p C_p}}$$
- Gain condition satisfied when

$$(g_m R_p)^2 \geq 1$$

Supply-Tuned Ring Oscillator

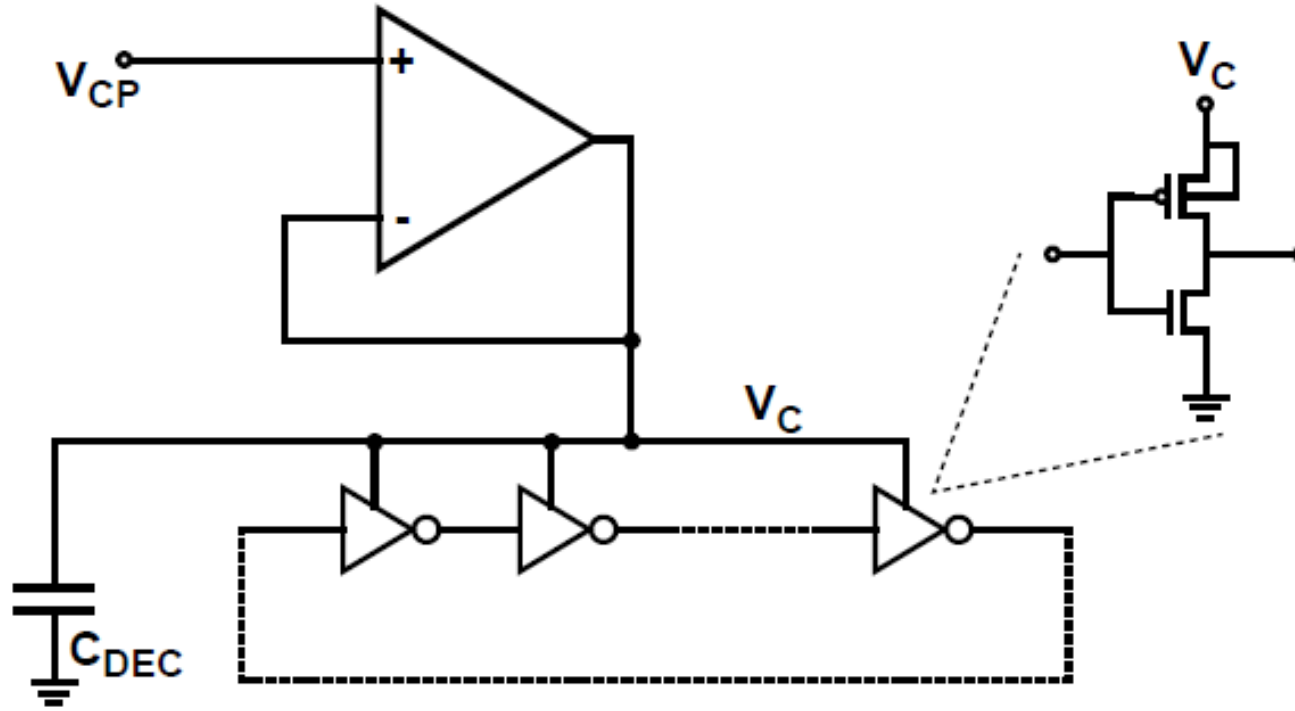


[Sidiropoulos VLSI 2000]

$$T_{VCO} = 2nT_D \approx \frac{2nC_{stage}}{\beta(V_c - V_{th})}$$

$$K_{VCO} = \frac{\partial f_{VCO}}{\partial V_c} = \frac{\beta}{2nC_{stage}}$$



Current-Starved Ring Oscillator

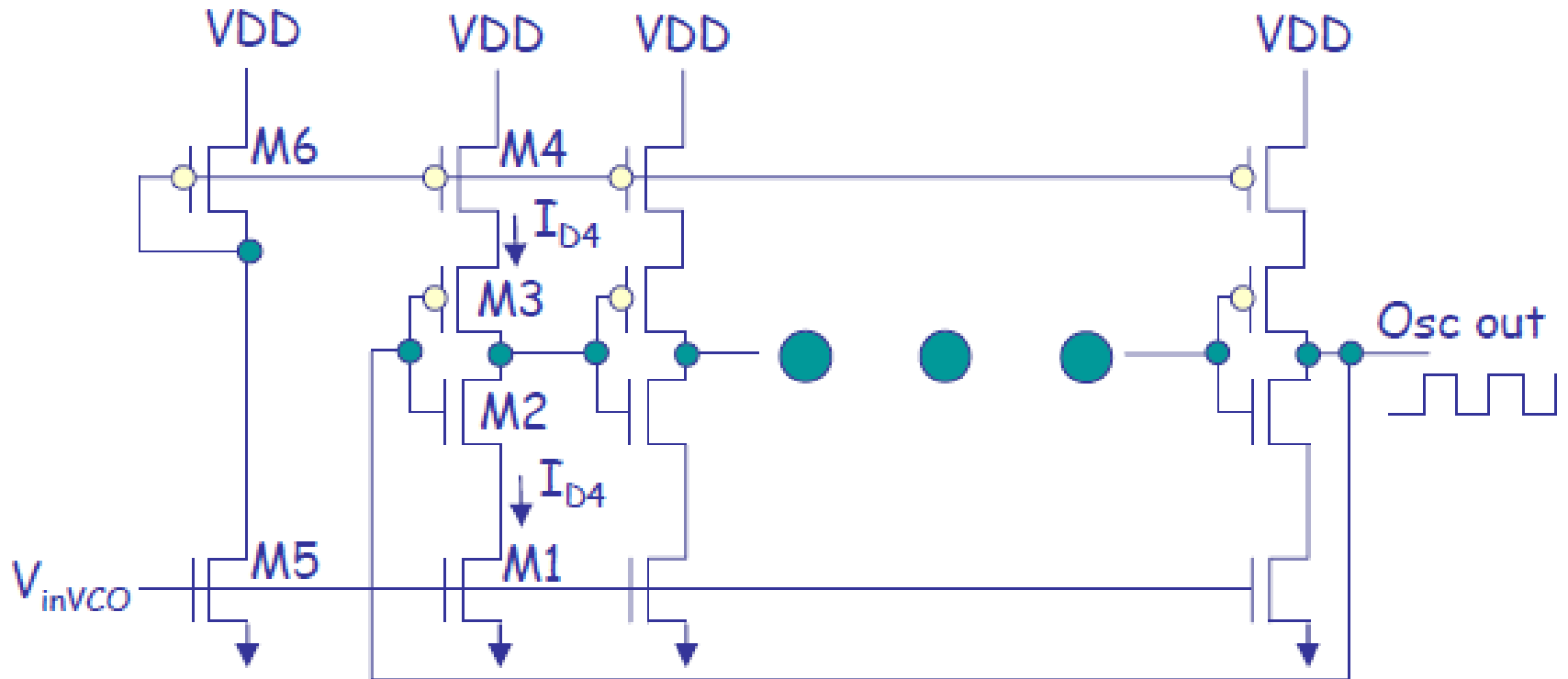

[Sanchez]

Current - starved VCO.


Capacitive-Tuned Ring Oscillator

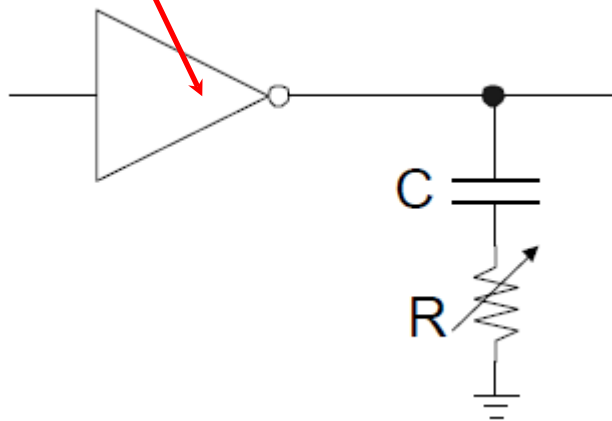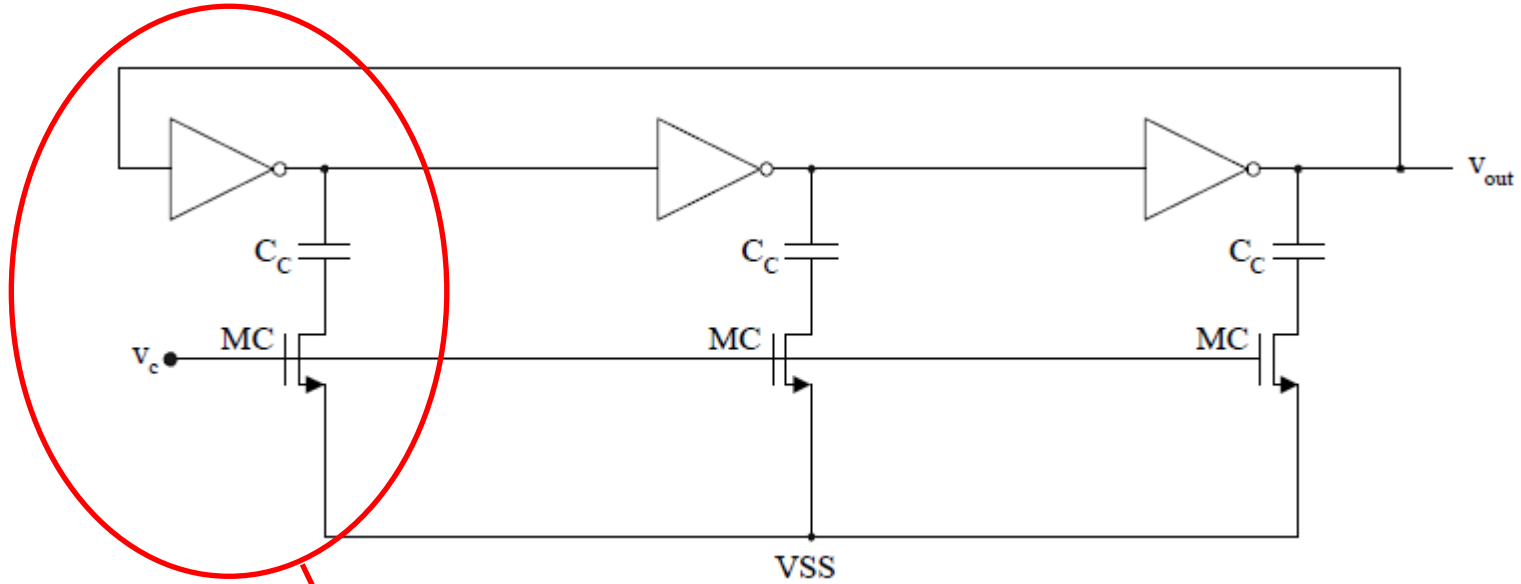

$$C_{eff} = \frac{C}{1 + sCR}$$

Symmetric Load Ring Oscillator

[Maneatis JSSC 1996 & 2003]

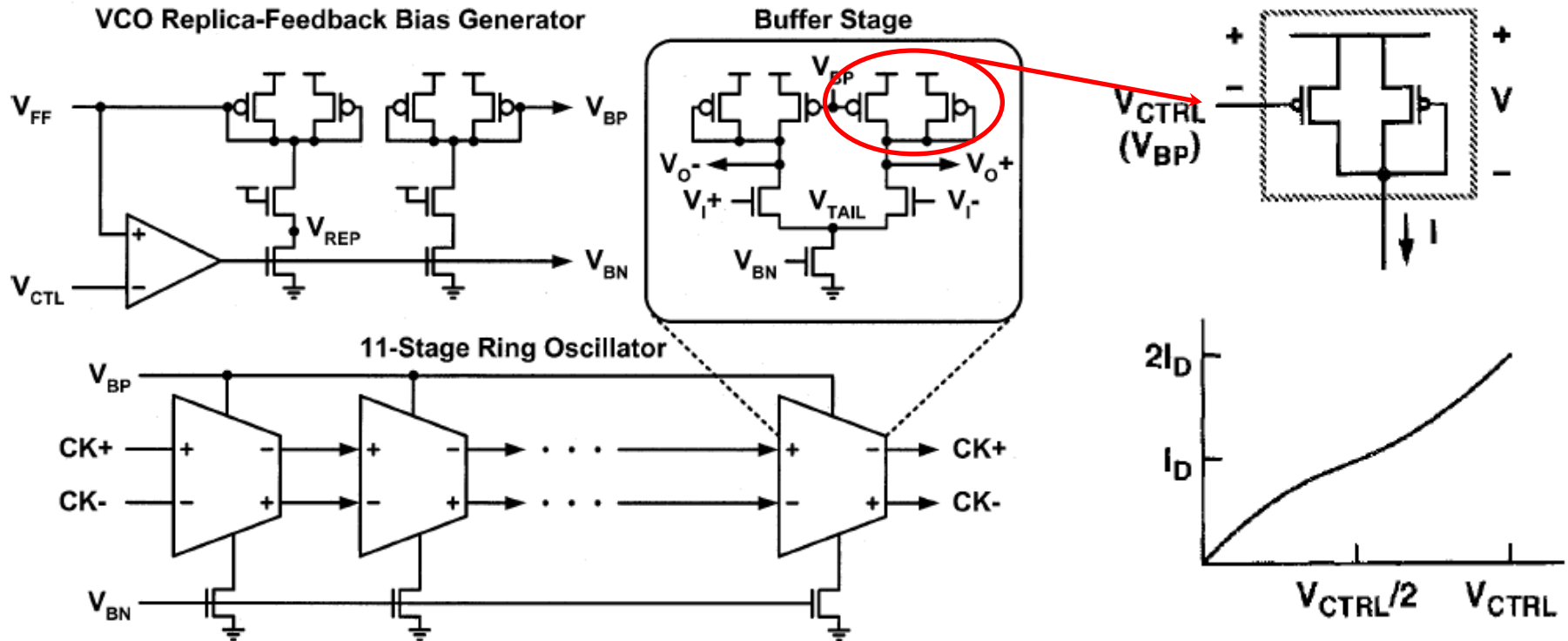


- Symmetric load provides frequency tuning at excellent supply noise rejection
- See Maneatis papers for self-biased techniques to obtain constant damping factor and loop bandwidth (% of ref clk)

LC Oscillator


- A variable capacitor (varactor) is often used to adjust oscillation frequency
- Total capacitance includes both tuning capacitance and fixed capacitances which reduce the tuning range
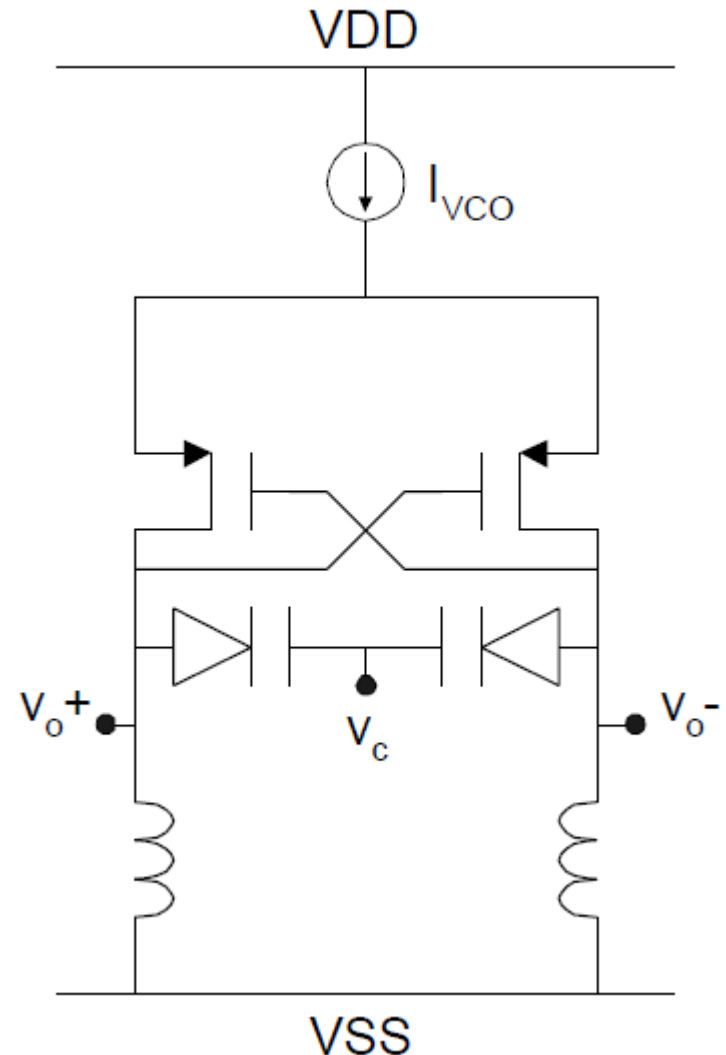
$$\omega_{osc} = \frac{1}{\sqrt{L_P C_P}} = \frac{1}{\sqrt{L_P (C_{tune} + C_{fixed})}}$$




Varactors

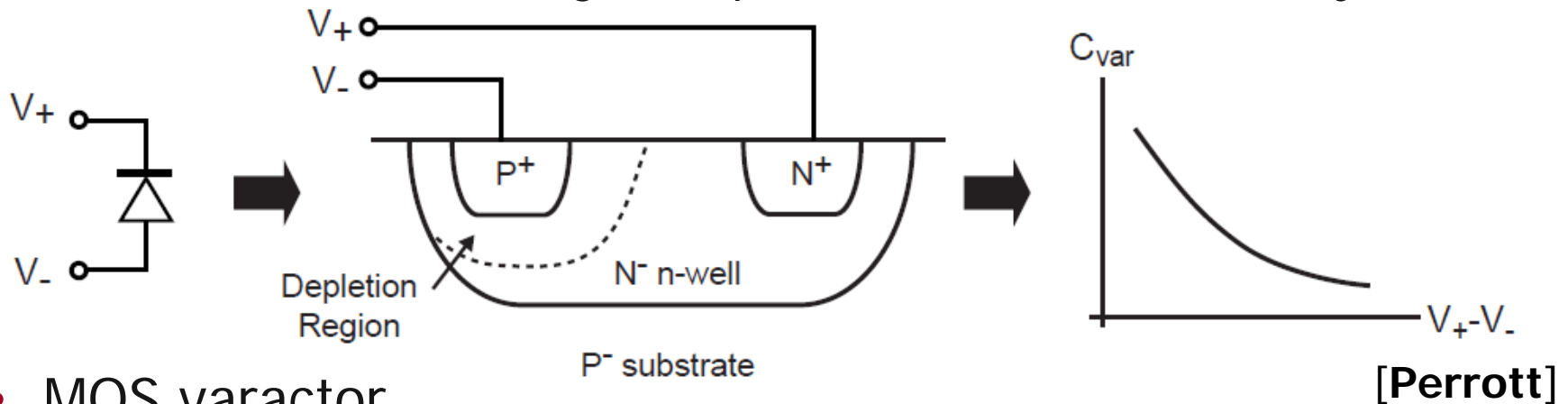
- pn junction varactor
 - Avoid forward bias region to prevent oscillator nonlinearity



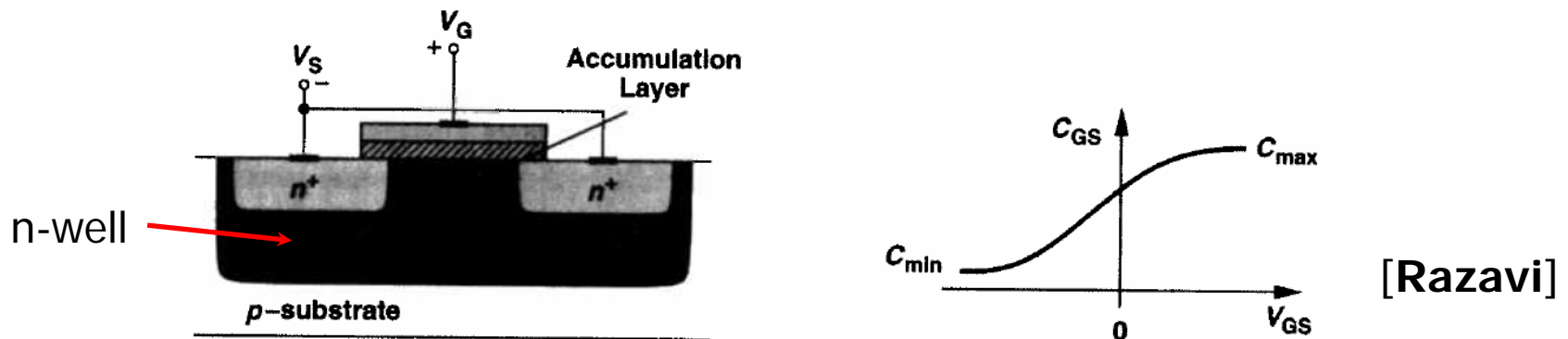- MOS varactor
 - Accumulation-mode devices have better Q




Oscillator Noise

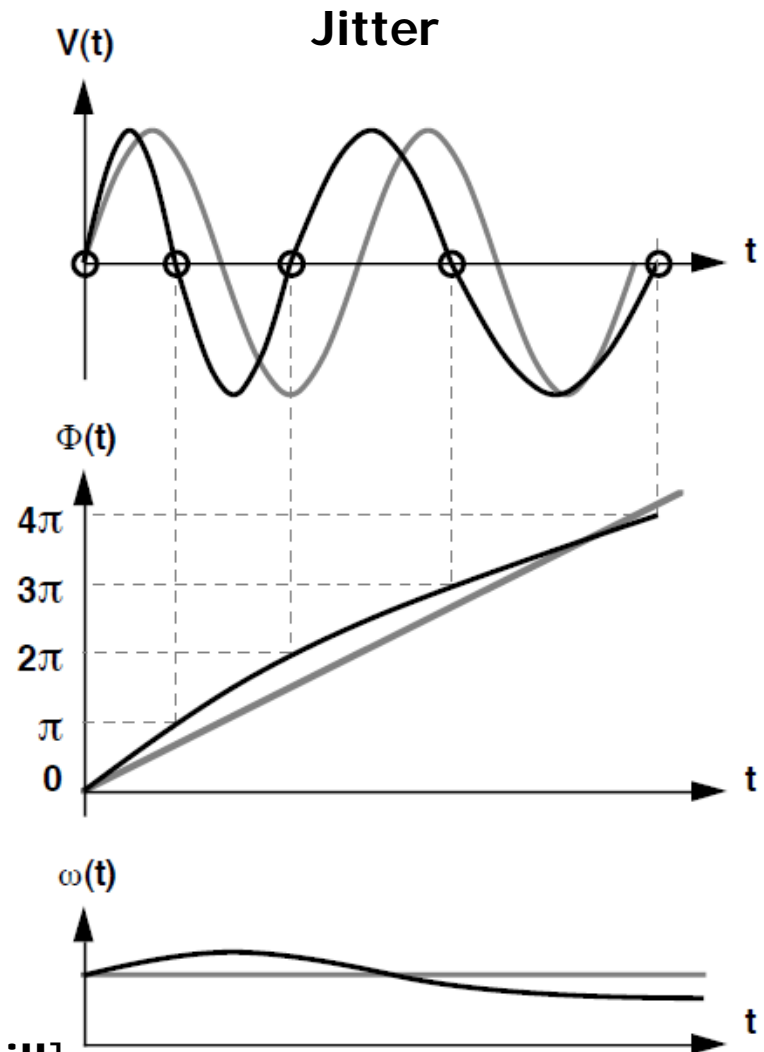


[McNeill]

PHASE NOISE

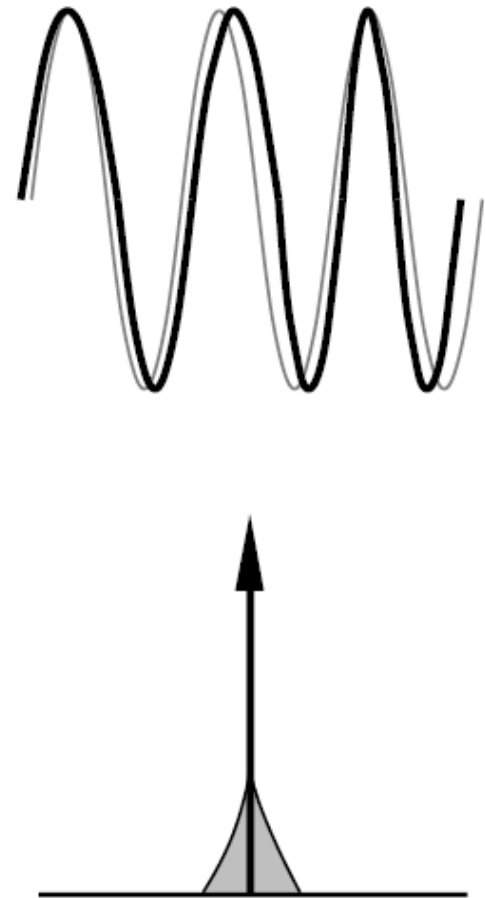

Oscillator Phase Noise Model

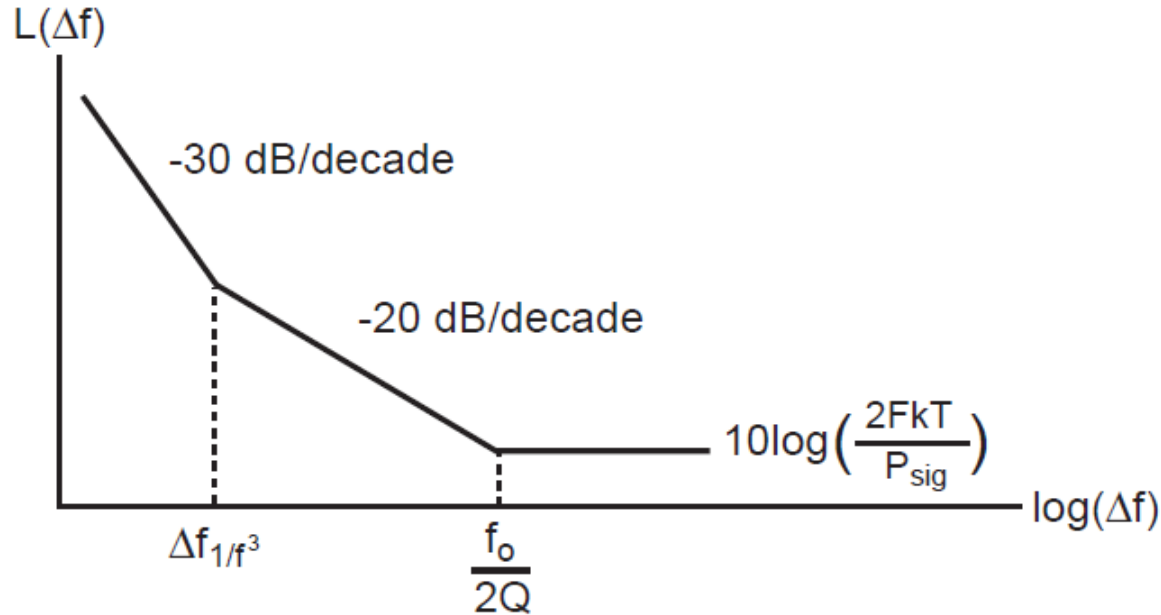


[Perrott]

$$L(f) = 10 \log \left(\frac{\text{Noise Spectral Density}}{\text{Carrier Power}} \right) \text{ (dBc/Hz)}$$

Leeson's Model:
$$L(\Delta f) = 10 \log \left(\frac{2FkT}{P_{sig}} \left(1 + \left(\frac{1}{2Q} \frac{f_o}{\Delta f} \right)^2 \right) \left(1 + \frac{\Delta f_{1/f^3}}{|\Delta f|} \right) \right)$$


- For improved model see Hajimiri papers

Open-Loop VCO Jitter

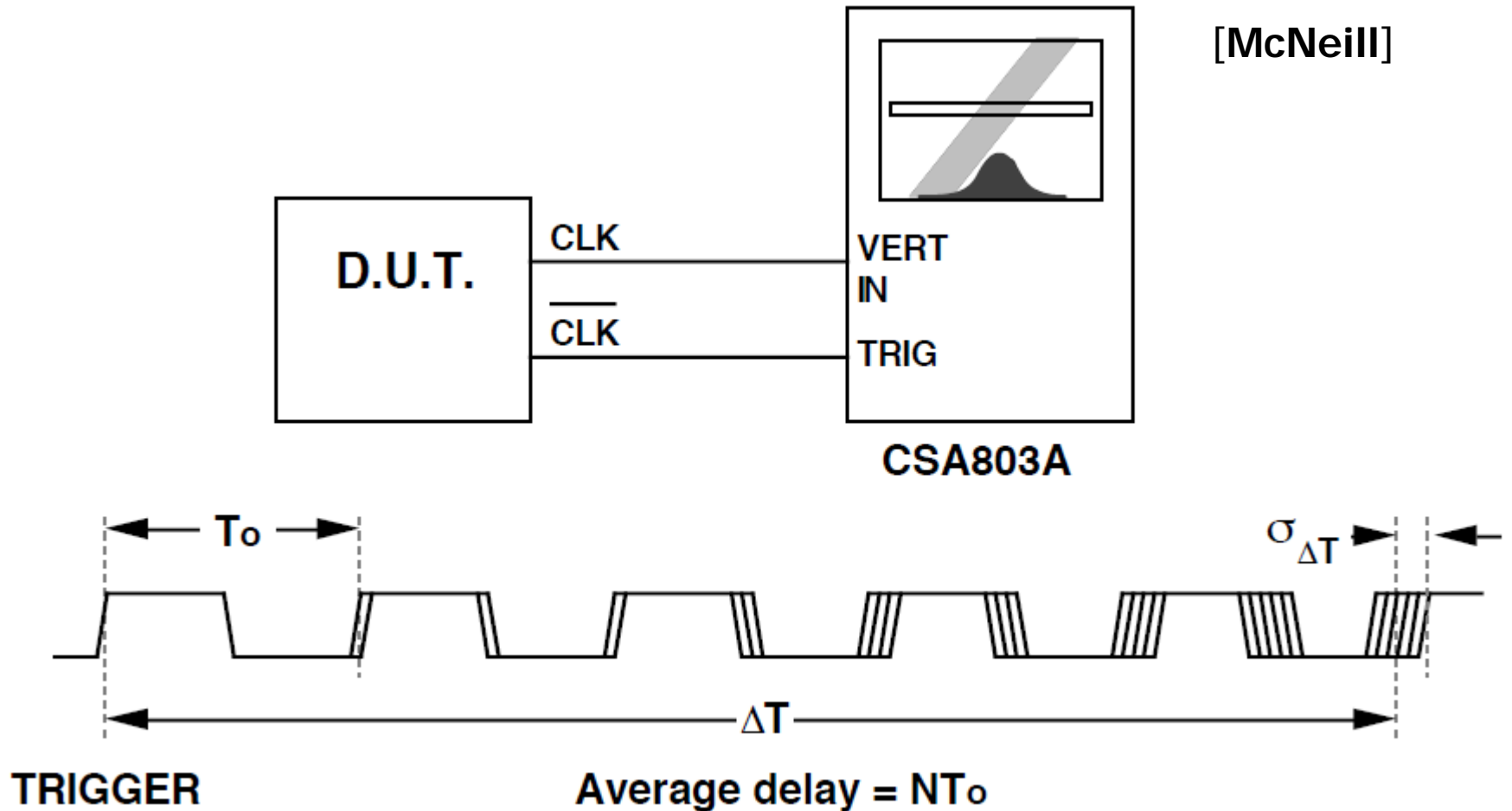

- Measure distribution of clock threshold crossings
- Plot σ as a function of delay ΔT

Open-Loop VCO Jitter

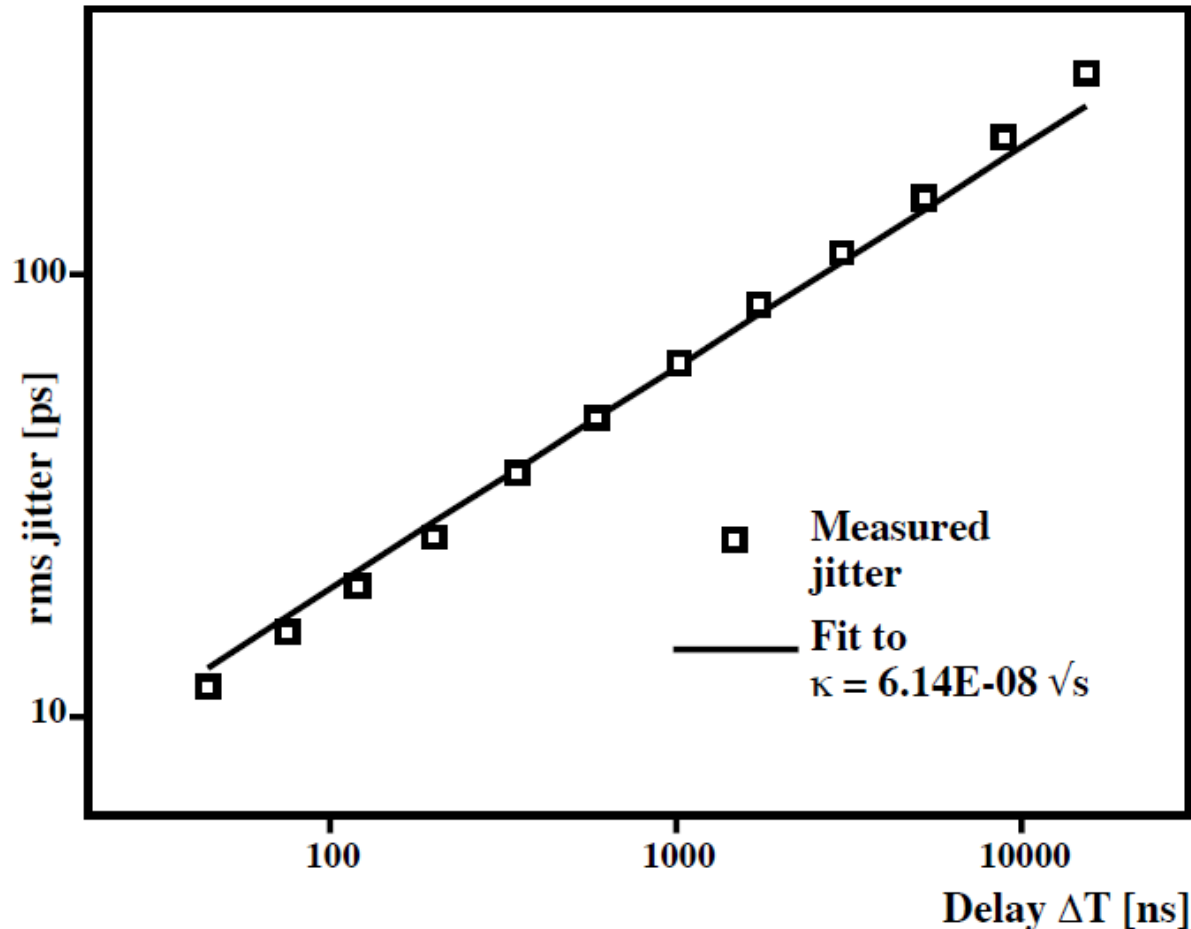


[McNeill]

$$\sigma_{\Delta T(OL)}(\Delta T) \approx \kappa \sqrt{\Delta T}$$

- Jitter σ is proportional to $\sqrt{\Delta T}$
- κ is VCO time domain figure of merit

VCO in Closed-Loop PLL Jitter

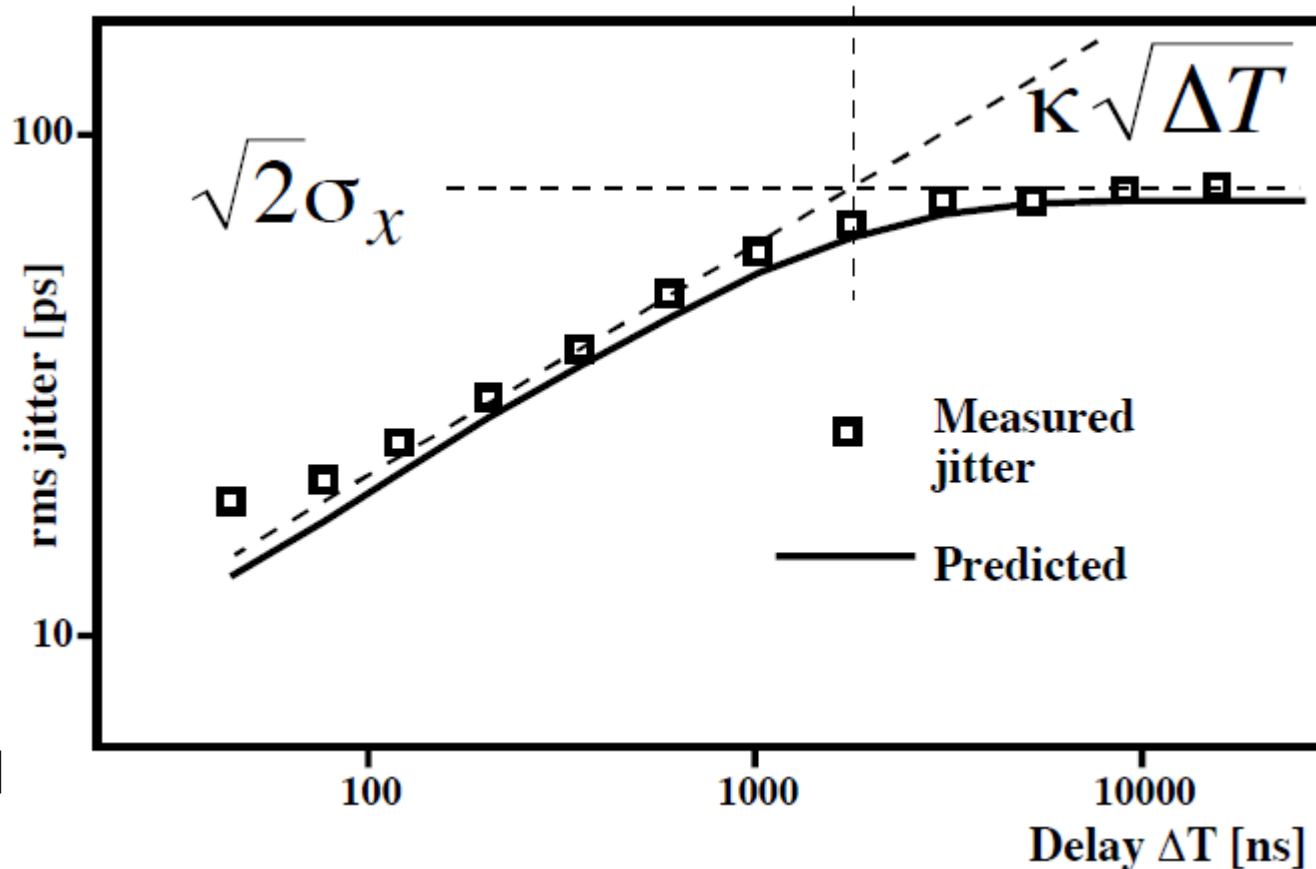

[McNeill]

- PLL limits σ for delays longer than loop bandwidth τ_L

$$\tau_L = 1/2\pi f_L$$

Converting Phase Noise to Jitter

- RMS Phase Jitter

$$J_{phase} = \frac{1}{2\pi f_{vco}} \sqrt{\int S_{\phi}(f) df}$$

- Integration range depends on application
 - f_{min} set by standard
 - Ex. Assumed CDR tracking bandwidth
 - Usually stop integration at $f_0/2$ to avoid capturing carrier and harmonics

Next Time

- PLL wrap-up
- CDRs